
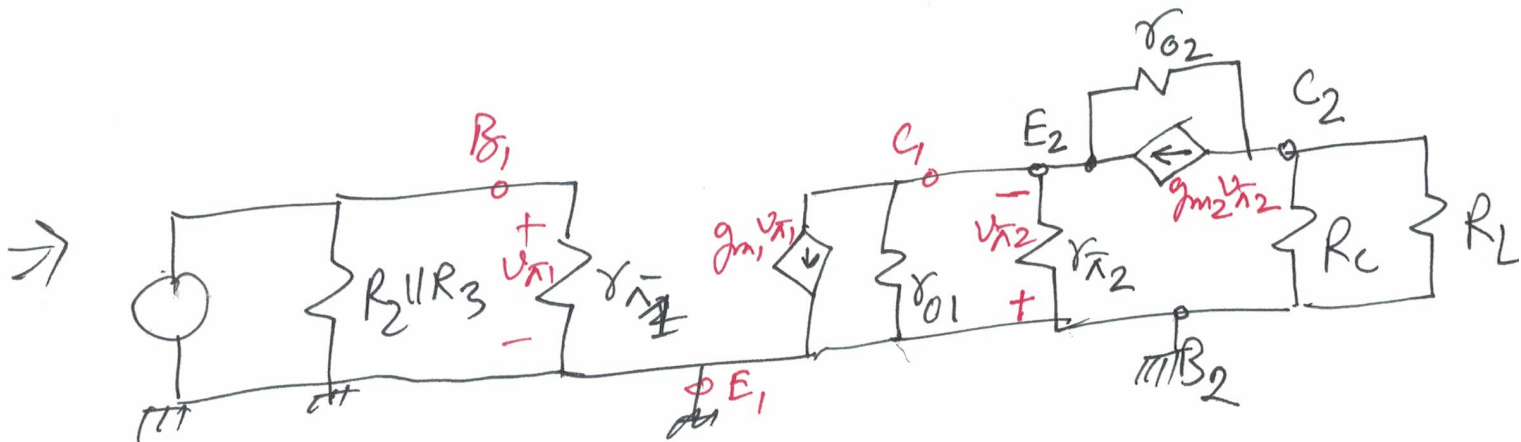
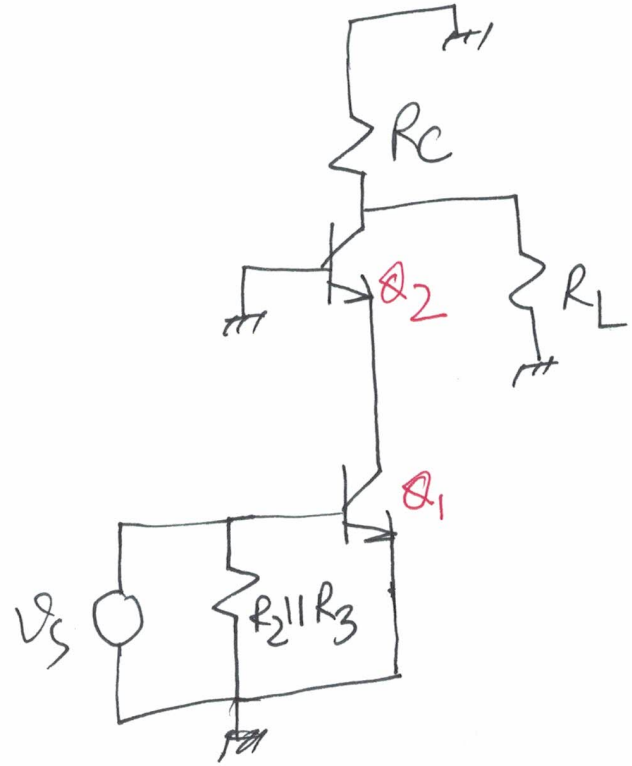


Problem 1 :

(21)

Equivalent AC circuit :

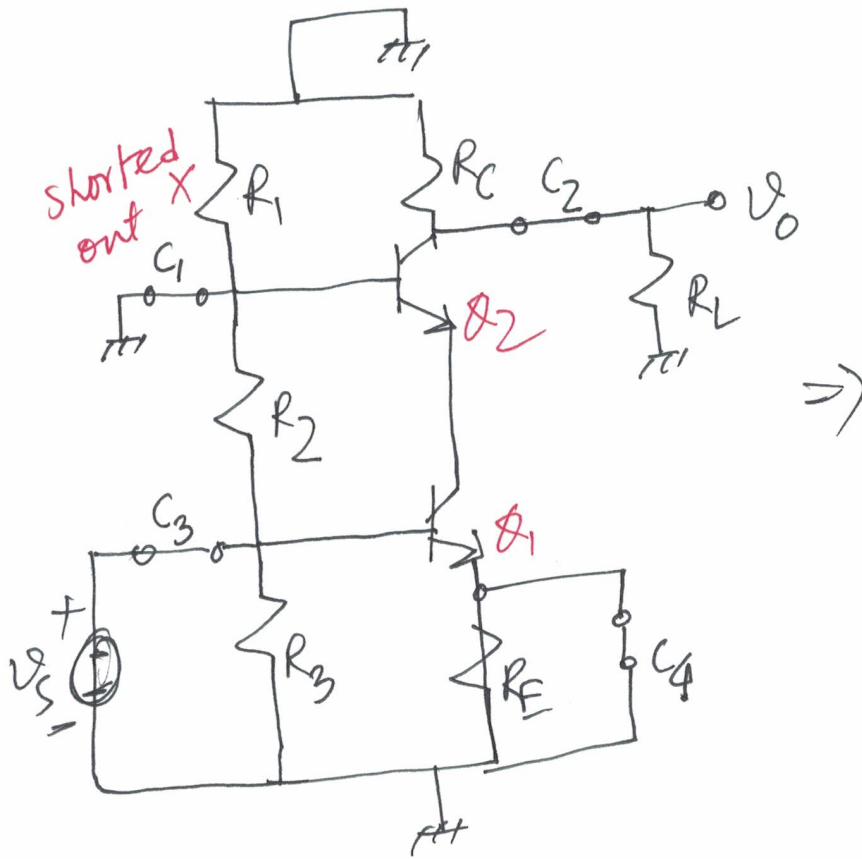

Problem 2 :

(22)

AC Equivalent Circuit :

