

# ENEL 469: Analog Electronic Circuits

## Quiz-2, Fall 2023



Total marks: 20; Time: 11:00 am – 12:00 pm

ID (Optional)	First Name (PRINT)	Last Name (PRINT)

1. [Total 4+1=5] Consider the following circuit where  $I_B = 20 \mu\text{A}$ ,  $\beta = 100$ , and  $V_A = 180 \text{ V}$ . Assume  $I_C = I_E$ , and  $V_{CE(\text{Sat})} = 0\text{V}$  for simplicity.

- a) [4] Draw the load line for the following circuit in the given space. Neatly draw the line at scale. Any ambiguities will be deemed as incorrect answers.

Soln:

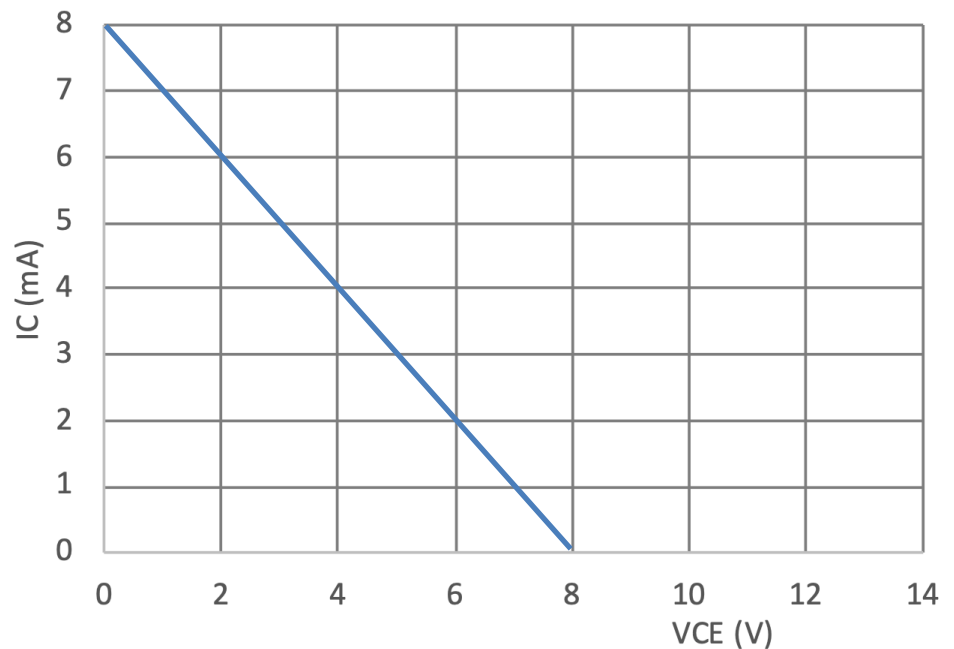
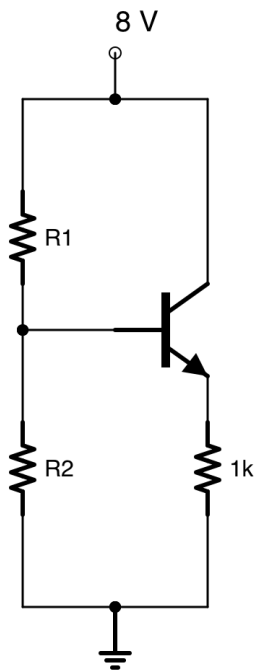


- b) [1] Determine the operating point, i.e.,  $I_{C,Q}$  and  $V_{CE,Q}$ . Here, the subscript Q indicates the respective values at the operating point.

**Ans:**  $I_{C,Q} = 2\text{mA}$

and  $V_{CE,Q} = 6\text{V}$

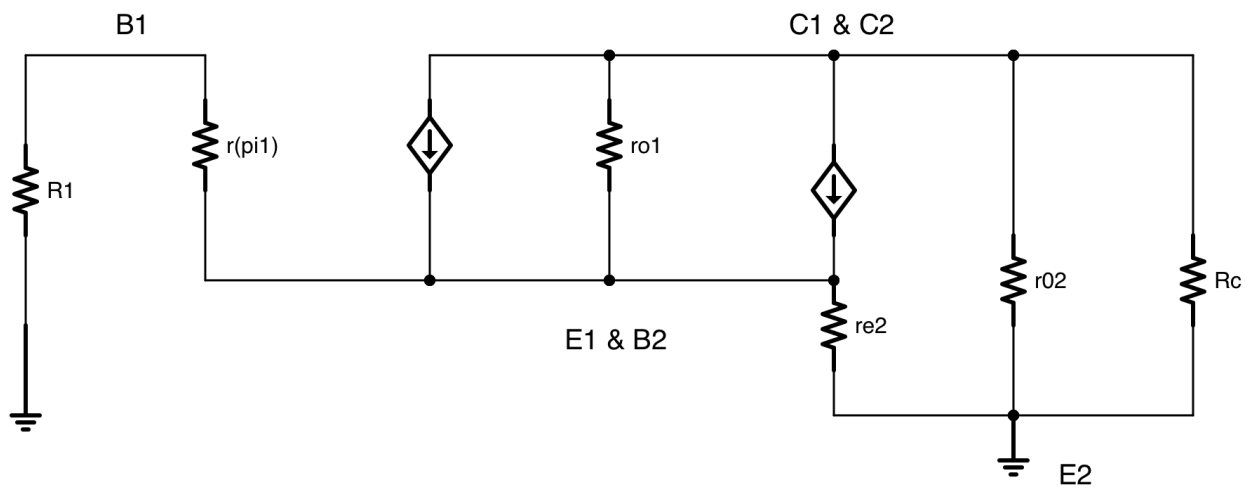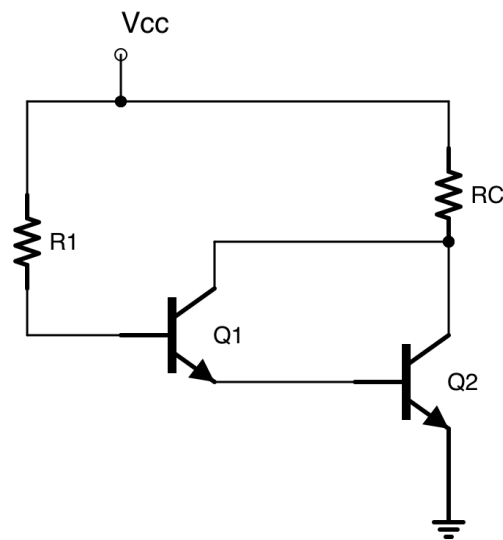2. [Total 4] Draw the small-signal model for the following circuit. Use the  $\pi$ -model for transistor Q1 and T-model for Q2. Note: Indicate the circuit elements using the suffix 1 for Q1 and 2 for Q2, i.e.,  $g_{m1}$  or  $g_{m2}$ . The circuit must be neatly drawn, and all elements must be properly labelled.




3. **[Total 3]** Consider the following circuit, which has a base current of  $I_{B1}$ . Assume the resistor  $R_2$  is changed from 4.7k to 3.0k, which sets a new base current  $I_{B2}$  in the circuit. Assume the transistor operates in the active region in both cases.


Which of the following arguments is correct?

Circle the correct one.

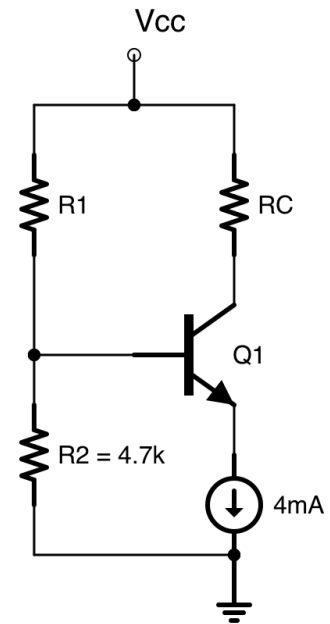- i)  $I_{B1} > I_{B2}$
- ii)  $I_{B1} < I_{B2}$
- ☒ iii)  $I_{B1} = I_{B2}$
- iv) All of the above
- v) None of the above




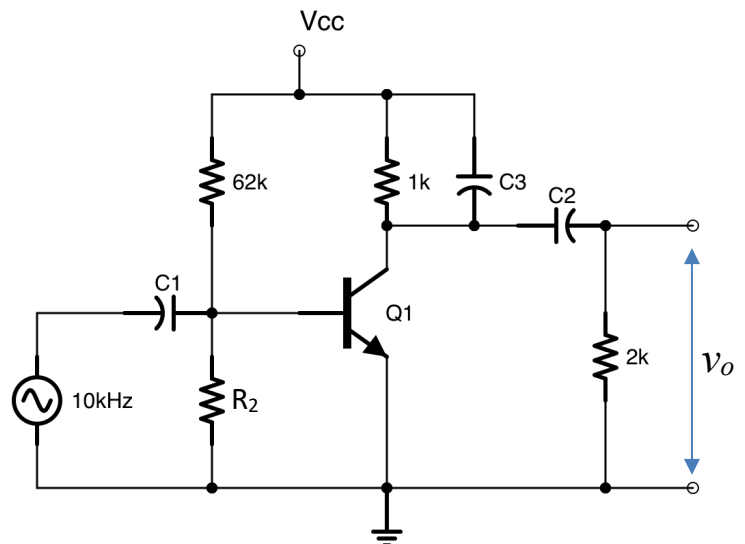4. **[Total 3]** An ENEL469 student wanted to make CE amplifier circuit in his/her lab. The student mistakenly added the third capacitor,  $C_3$ , as shown in the circuit below. The circuit without  $C_3$  gave a voltage gain of 120 and  $V_o = 0.6V$ . What will the new output voltage ( $V_o$ ) be when  $C_3$  is added? The student did not disclose the value of  $R_2$ .



**Ans:  $V_o = 0$**

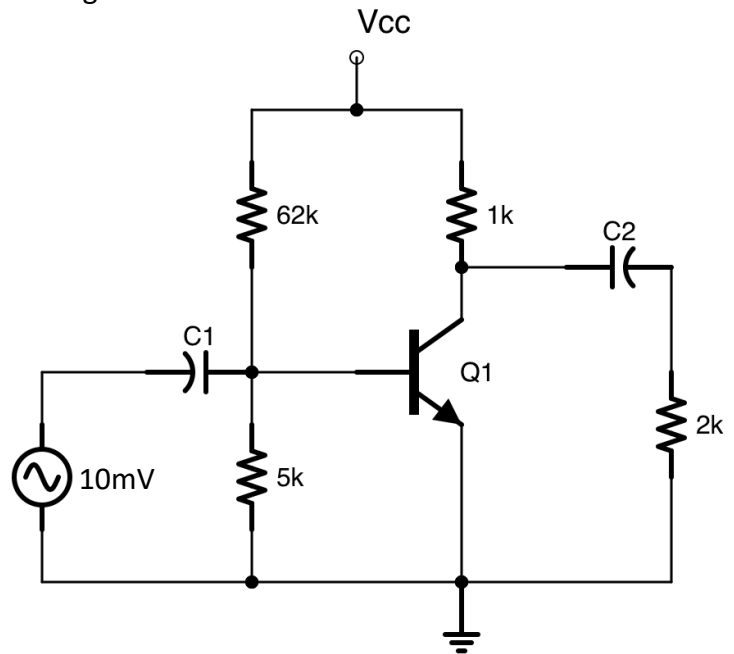5. **[Total 5]** In the following circuit,  $V_{CC} = 10V$ ,  $V_{BE(on)} = 0.7V$ ,  $V_{CE(sat)} = 0.2V$ ,  $V_A = 160V$ , and the internal resistance of the AC source is  $200\Omega$ . The capacitor values are such that they are shorted for the AC signal. Determine the signal voltage that appears at the base, i.e.,  $v_{be}$ . Assume the transistor remains in the active region.



$$I_{(5k)} = \frac{0.7}{5000} = 140\mu A$$

$$\text{and } I_{(62k)} = \frac{12-0.7}{62000} = 150\mu A$$

$$\text{Thus, } I_B = 150 - 140 = 10\mu A$$

$$\text{If so, } r_\pi = (V_T)/(I_B) = 2.5\text{ k}\Omega$$

$$\begin{aligned} \text{The input resistance seen by the source} &= 62\text{k}\Omega // 5\text{k}\Omega // (r_\pi) \\ &= 62\text{k}\Omega // 1.67\text{k}\Omega \\ &= 1.63\text{k}\Omega \end{aligned}$$

Since the internal resistance  $200\Omega$  and the input resistance  $1.63\text{k}\Omega$  are in series, the base voltage can be obtained by voltage division,

$$v_{be} = \frac{10 \times 10^{-3} \cdot 1.63}{(1.63 + 0.2)} = 8.91\text{mV}$$

**Ans:  $v_{be} = 8.91\text{ mV}$**