


IC Biasing

- Integrated Circuits (ICs) have millions or billions of transistors in it
- How can we bias them in a single piece of circuit?

How to bias multiple transistors using a single circuit?

- Higher fabrication area is expensive in terms of area
- Fabricating resistors and capacitors are expensive, but transistors are relatively cheaper.

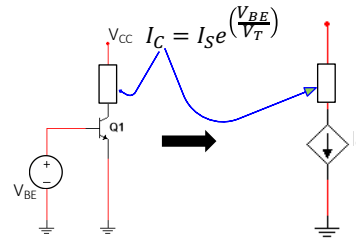- We have already learned that a transistor is a voltage controlled current source.
- How can we use transistors to get a constant current source.



1


1

Two-Transistor Current Source (Current Mirror)

- The two transistors are identical
- $V_{BE1} = V_{BE2} = V_{BE(on)}$ (Same nodes)
- $I_{B1} = I_{B2} = I_B$
- $I_{C1} = I_{C2} = I_o$
- Strictly considering, $I_{Ref} \neq I_{C1}$
- However, for large β values,

$$I_{Ref} \approx I_{C1} = I_o$$

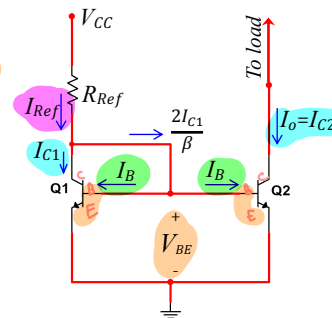This is a **mirror circuit** where the reference current is **mirrored to the load**.



Notice that

$$I_{Ref} \approx I_o = \frac{V_{CC} - V_{BE(on)}}{R_{Ref}}$$

using KVL:

$$V_{CC} - V_{BE(on)} - I_o R_{Ref} = 0$$


current mirror is when 2 identical transistors are connected in this configuration

-B and C are shorted

-there is RRef connected to C

2

2

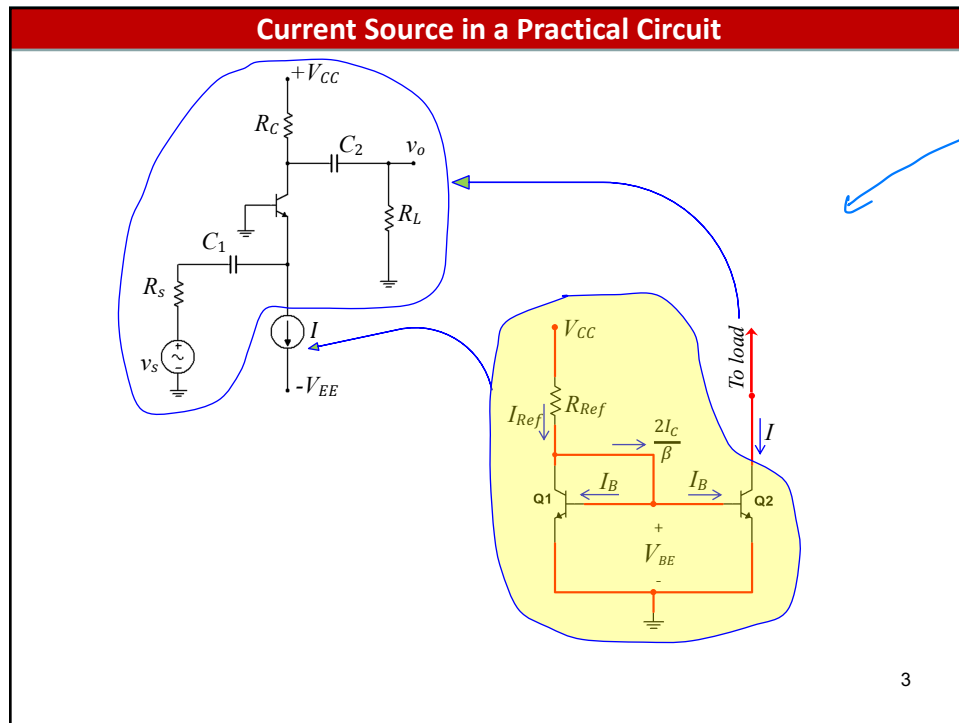

this is how
to connect
a current
source to
Load

current mirror
circuit

3

Current Mirror: Effect of β

- β values are not always very large
- What is the effect of β ?
- Assume that β of Q1 and Q2 are finite, and the base currents cannot be ignored

$$I_{Ref} = I_{C1} + 2I_B = I_{C1} + \frac{2I_{C1}}{\beta}$$

or, $I_{Ref} = I_{C1} \left(1 + \frac{2}{\beta}\right)$

or, $\frac{I_o}{I_{Ref}} = \frac{1}{1 + \frac{2}{\beta}}$ [Since $I_{C1} = I_o$]

V_{CC}

R_{Ref}

I_{Ref}

2I_{C1}

β

Q1

Q2

I_B

I_B

V_{BE}

To load

I_o = I_{C2}

If $\beta = 60$,

$$\frac{I_o}{I_{Ref}} = \frac{1}{1 + \frac{2}{60}} = 0.968 \quad \text{3.2\% error}$$



If $\beta = 160$,

$$\frac{I_o}{I_{Ref}} = \frac{1}{1 + \frac{2}{160}} = 0.988 \quad \text{1.2\% error}$$

4

4

Current Mirror: Effect of V_A

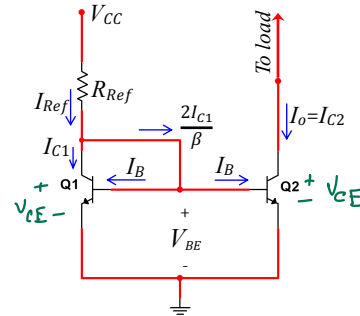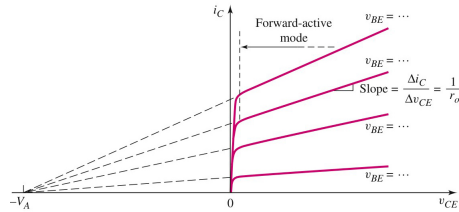

- Recall Early voltage effect
- For lower V_A values, I_C doesn't remain constant with V_{CE}
- For the current mirror, V_{CE1} and V_{CE2} are NOT guaranteed to be the same

Thus, even with $\beta = \infty$, the two collector currents can be different depending on their V_A value.

what determines V_A value

5

5

Current Mirror: Effect of V_A When $\beta = \infty$

- Recall Early voltage effect
- For lower V_A values, I_C doesn't remain constant with V_{CE}


Assume V_A is finite, but $\beta = \infty$. We can write,

$$I_{Ref} = I_{C1} \text{ and}$$

$$I_{C1} = I_s e^{\left(\frac{V_{BE}}{V_T}\right)} \left(1 + \frac{V_{CE1}}{V_A}\right)$$

$$I_{C2} = I_s e^{\left(\frac{V_{BE}}{V_T}\right)} \left(1 + \frac{V_{CE2}}{V_A}\right)$$

Shockley's

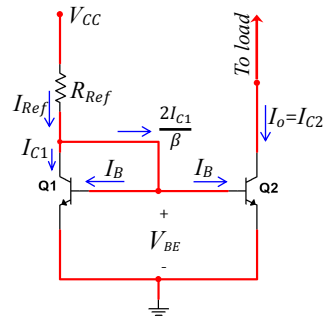


$$\text{or, } \frac{I_{C2}}{I_{C1}} = \frac{I_O}{I_{Ref}} = \frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}}$$

6

6

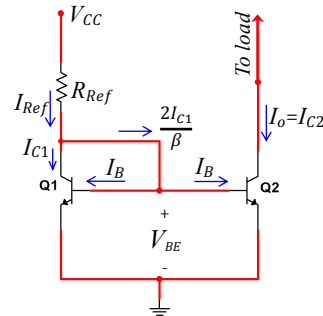Current Mirror: $\beta \neq \infty$ and $V_A \neq \infty$




When β and V_A both are finite, we can write

$$\frac{I_o}{I_{Ref}} = \left[\frac{1}{1 + \frac{2}{\beta}} \right] \times \left[\frac{1 + \frac{V_{CE2}}{V_A}}{1 + \frac{V_{CE1}}{V_A}} \right]$$

7

7

Current Mirror: Output Resistance

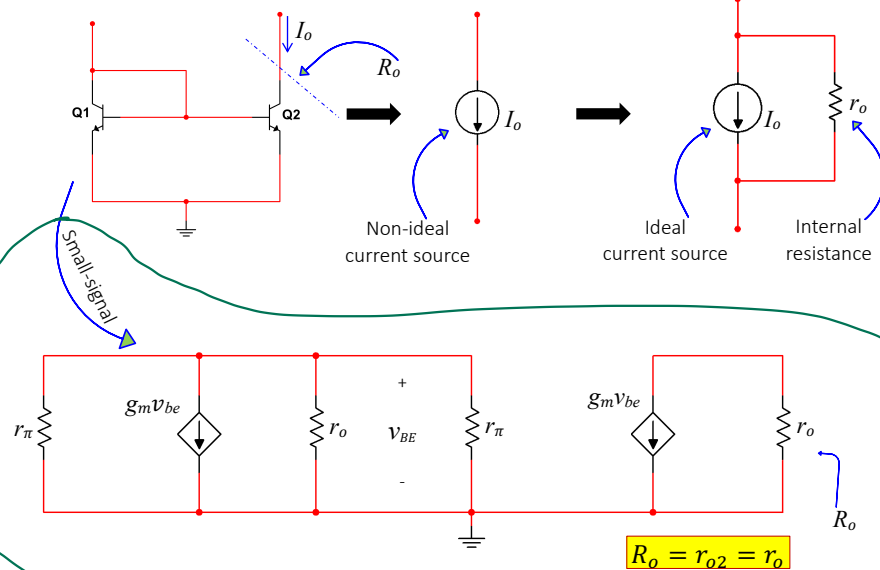



-simply says that a current mirror can be represented by ideal current source and internal resistance

* Parameters
 g_m
 r_{π}
 $r_o = r_{o2} = R_o$
 given in formula sheet

8

8

Ideal Current Source

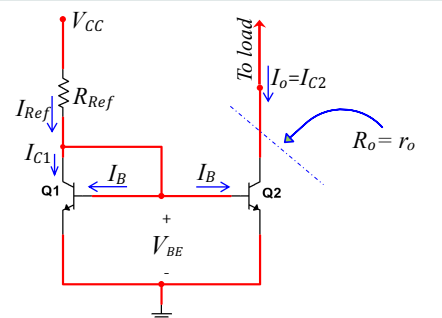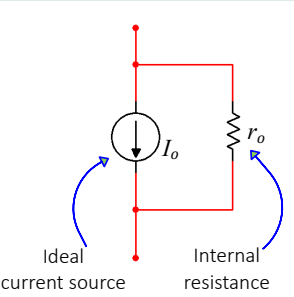For an ideal (good quality) current source, we need to ensure the following two important things


- The output current I_o must be equal to the desired current. For a two-transistor current mirror, I_o must be equal to I_{ref} i.e., $I_o = I_{ref}$
- The output resistance r_o must be infinite. In practice, as high as possible.

Two-transistor current mirror

9

9

Current Mirror With Current Compensation

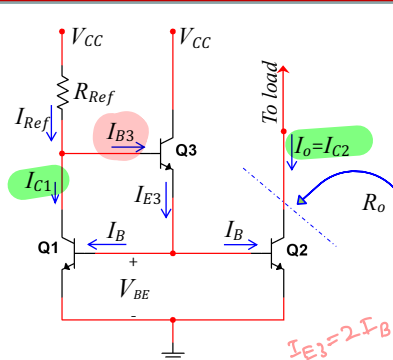

- All transistors are identical
- $I_{C1} = I_{C2} = I_C$
- $\beta_1 = \beta_2 = \beta_3 = \beta$

We have,

$$I_{ref} = I_C + I_{B3} = I_C + \frac{2I_C}{\beta(\beta+1)}$$

Or, $I_{ref} = I_C \left[1 + \frac{2}{\beta(\beta+1)} \right]$

Or, $\frac{I_o}{I_{ref}} = \frac{1}{1 + \frac{2}{\beta(\beta+1)}}$

Or, $\frac{I_o}{I_{ref}} \approx \frac{1}{1 + \frac{2}{\beta^2}}$ 😊


$R_o = r_{o2}$

$R_o = r_o$ 😞

10

10

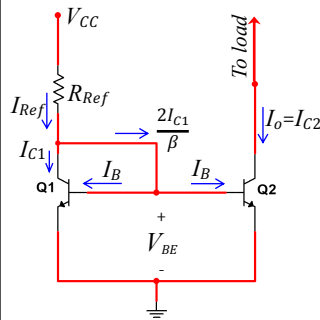Current Mirror With Current Compensation: Example




Recall that for two-transistor current mirror,

$$\frac{I_o}{I_{Ref}} = \frac{1}{1 + \frac{2}{\beta}}$$

For $\beta = 60$, we had 3.2% error

For $\beta = 160$, we had 1.2% error

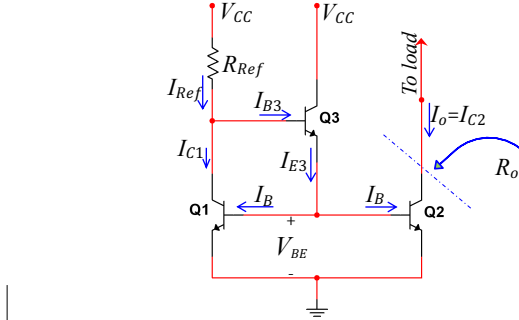

For current mirror with current compensation

If $\beta = 60$,

$$\frac{I_o}{I_{Ref}} = 1 / \left(1 + \frac{2}{60^2} \right) = 0.999 \quad 0.1\% \text{ error}$$

If $\beta = 160$,

$$\frac{I_o}{I_{Ref}} = 1 / \left(1 + \frac{2}{160^2} \right) = 0.9999 \quad 0.01\% \text{ error}$$

* The only diff is β^2

$$\frac{I_o}{I_{Ref}} \approx \frac{1}{1 + \frac{2}{\beta^2}}$$

11

11

Clearly there is much less error with current compensation

Wilson Current Mirror

- Wilson current mirror also uses current compensation with a slight difference for increasing the output resistance.
- All transistors are identical

It can be shown that

$$\frac{I_o}{I_{Ref}} = \frac{1}{1 + \frac{2}{\beta^2}}$$

$$R_o = \beta \frac{r_o}{2}$$

If
 $I_o = 4 \text{ mA}$
 $V_A = 100 \text{ V}$
 $\beta = 140$

For a two-transistor current mirror,

$$R_o = r_o = \frac{V_A}{I_C} = \frac{100}{4 \times 10^{-3}} = 25 \text{ k}\Omega$$

For Wilson current mirror,


$$R_o = \frac{\beta r_o}{2} = \frac{140 \times 100}{2 \times 4 \times 10^{-3}} = 1.75 \text{ M}\Omega$$

12


12

much greater output resistance

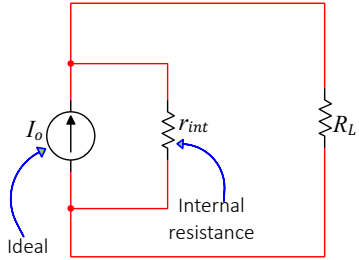Effect of Current Source Internal Resistance



current source

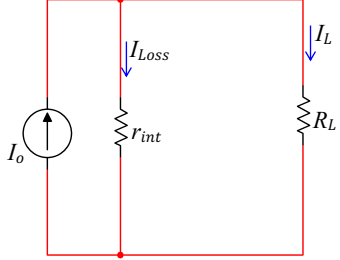

For, $r_{int} = 25 \text{ k}\Omega$
 If $R_L = 10 \text{ k}\Omega$,
 $I_L = 71\% \text{ of } I_o$ and $I_{Loss} = 29\% \text{ of } I_o$

If $R_L = 100 \text{ k}\Omega$,
 $I_L = 20\% \text{ of } I_o$ and $I_{Loss} = 80\% \text{ of } I_o$

For, $r_{int} = 1.75 \text{ M}\Omega$ (Wilson mirror)
 If $R_L = 10 \text{ k}\Omega$,
 $I_L = 99.4\% \text{ of } I_o$ and $I_{Loss} = 0.6\% \text{ of } I_o$

If $R_L = 100 \text{ k}\Omega$,
 $I_L = 94.6\% \text{ of } I_o$ and $I_{Loss} = 5.4\% \text{ of } I_o$

- most of the current goes to load and there is barely any I_o

as $R_L \uparrow$ it becomes worse

13

Mon Oct 23rd

• for all previous:
 $I_{C1} = I_{C2}$
 $V_{BE1} = V_{BE2}$
 • not case here due to resistor in emitter of Q_2

Wilson vs Widlar

Widlar Current Source

- The two transistors are identical
- $V_{BE1} \neq V_{BE2}$, $I_{B1} \neq I_{B2}$ and $I_{C1} \neq I_{C2}$

We can write for Q_1 and Q_2


$$V_{BE1} = V_T \ln \left(\frac{I_{Ref}}{I_S} \right)$$

$$\text{and, } V_{BE2} = V_T \ln \left(\frac{I_o}{I_S} \right)$$

Subtracting the two equations,

$$V_{BE1} - V_{BE2} = V_T \ln \left(\frac{I_{Ref}}{I_o} \right)$$
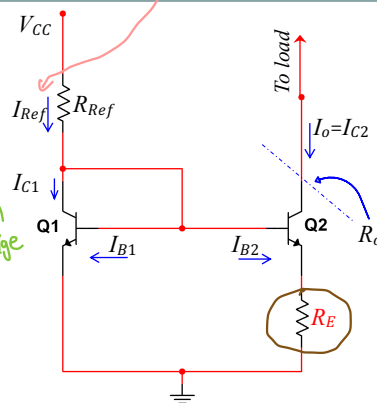
$$\text{Or, } I_o R_E = V_T \ln \left(\frac{I_{Ref}}{I_o} \right)$$



One can also show that

$$R_o = [1 + g_m(R_E // r_{\pi 2})] r_{o2}$$

(no need to know derivation)¹⁴

input resistance


14

$$V_{BE1} = 0.7$$

If $\alpha \approx 1$
 $I_{C2} = I_{E2} = I_o$
 $= \frac{V_T}{R_E} \ln \left(\frac{I_{Ref}}{I_o} \right)$

Widlar Current Source (Continued ...)

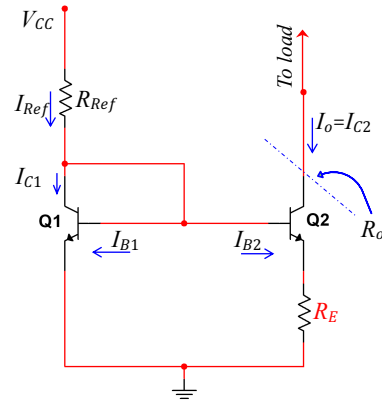
- Both transistors must operate in active region
- The reference current is still $I_{Ref} = \frac{V_{CC} - V_{BE1}}{R_{Ref}}$ *last slide*
- The output current cannot be higher than the reference current I_{ref}
- The output current can be set to any fraction by changing R_E
- The output resistance is very high, particularly for low output currents



15

15

Current Steering

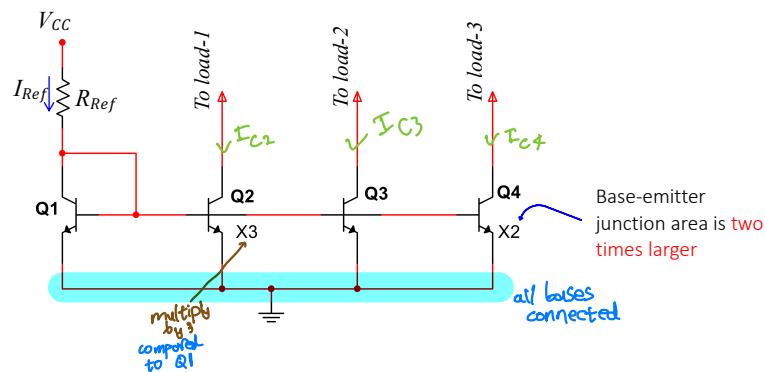

Assume β and V_A are infinite

Thus,

- $I_{C3} = I_{Ref}$
- $I_{C2} = 3I_{Ref}$
- $I_{C4} = 2I_{Ref}$

$$I_{Ref} = \frac{I_{C2}}{3} = I_{C3} = \frac{I_{C4}}{2}$$

16

16

hardest part:
- identify reference
transistor

will be one
where B and
C are shorted

Current Steering: Example-1

Here,

$$I_{Ref} = \frac{V_{CC} - V_{BE1}}{R_{Ref}} = \frac{10 - 0.7}{16 \times 10^3}$$

$$I_{Ref} = 0.581 \text{ mA}$$

$$I_{C2} = 2 \times I_{Ref} = 1.162 \text{ mA}$$

$$I_{C3} = 3 \times I_{Ref} = 1.743 \text{ mA}$$

$$I_{C4} = I_{Ref} = 0.581 \text{ mA}$$

17

find all currents
 $I_{Ref}, I_{C2}, I_{C3}, I_{C4}$

17

Current Steering: Example with Saturation

Same circuit as given in the previous slide, except this resistor value is high.

The currents are exactly same as before, i.e.,

$$I_{Ref} = \frac{10 - 0.7}{16 \times 10^3} = 0.581 \text{ mA}$$

$$I_{C2} = 2 \times I_{Ref} = 1.162 \text{ mA}$$

$$I_{C3} = 3 \times I_{Ref} = 1.743 \text{ mA}$$

$$I_{C4} = I_{Ref} = 0.581 \text{ mA}$$

Notice that

$$I_{C3(max)} = \frac{(10 - 0.2)}{6 \times 10^3} = 1.633 \text{ mA}$$

- Thus, Q3 is in saturation
- I_{C3} will be $I_{C3} = I_{C3(max)} = 1.633 \text{ mA}$
- Q3 doesn't work as a current mirror

18

one of resistor values too high, so that transistor doesn't act as current mirror

$$I_{C3(max)} = \frac{V_{CC} - V_{SAT}}{R_3}$$

18

the rest of transistors work fine

* Q_1 is reference, can write clear KVL

Current Steering: Example-2

Example: Consider the given current steering circuit where β and V_A are infinite. Determine:
a) I_C of all transistors and
b) $|V_{CE}|$ of all transistors

$$I_{Ref} = \frac{7 - 0.7 - 0.7 - 0.7 - (-5)}{19.8 \times 10^3} = 0.5 \text{ mA}$$

Here, all transistor have equal collector current which is 0.5 mA

DC analysis


$$V_{CE1} = |V_{CE10}| = |V_{CE6}| = 0.7 \text{ V}$$

$$V_{CE2} = 0 - 2 \times 0.5 - (-5) = 4 \text{ V}$$

$$V_{CE3} = V_{CE4} = V_{CE5} = -1 \times 1.5 + 5 = 3.5 \text{ V}$$

$$V_{CE7} = 7 - 4 \times 0.5 = 5 \text{ V}$$
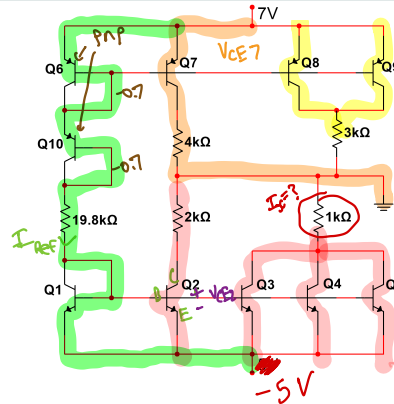
$$V_{CE8} = V_{CE9} = 7 - 3 \times 1 = 4 \text{ V}$$



* There must be clear current that doesn't depend on other parameters in circuit

$$7 - (3 \times 0.5) - 0$$

* they are connected

$$7 - (3 \times 1) - 0 = 4 \text{ V}$$


$$= (1.5 \text{ mA} \times 1 \text{ k}) - (-5) = 3.5 \text{ V}$$

19

* 2 criteria to identify reference:
① B and C are shorted
② can write KVL with no unknowns, i.e. independent of other components

$$I_{REF} = \frac{12 - 0.7 - 0.7 - (-10)}{20.6 \times 10^3} \approx 1 \text{ mA}$$

Current Steering: Example-3

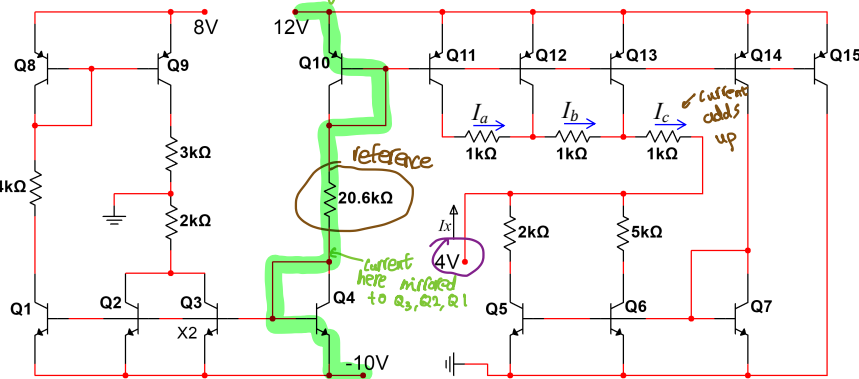

Determine the power in 4V source

$$I_{Ref} = I_{C4} = I_{C10} = 1 \text{ mA}$$

$$I_a = I_{C11} = 1 \text{ mA}$$

$$I_b = I_{C11} + I_{C12} = 2 \text{ mA}$$

$$I_c = I_b + I_{C13} = 3 \text{ mA}$$

By KCL,

$$I_{C5} + I_{C6} - I_c - I_x = 0 \quad \text{Why?}$$

$$I_x = 1 + 0.76 - 3 = -1.24 \text{ mA}$$

The power in 4V source is,

$$P_{4V} = 4 \times (-I_x) = 4.96 \text{ W (absorbed)}$$

Q6 is saturated


$$I_{C5} + I_{C6} = I_c + I_x$$

$$I_x = I_{C5} + I_{C6} - I_c$$

20

$$I_{REF} = \frac{12 - 0.7 - 0.7 - (-10)}{20.6 \times 10^3} \approx 1 \text{ mA}$$

same as
ex 3

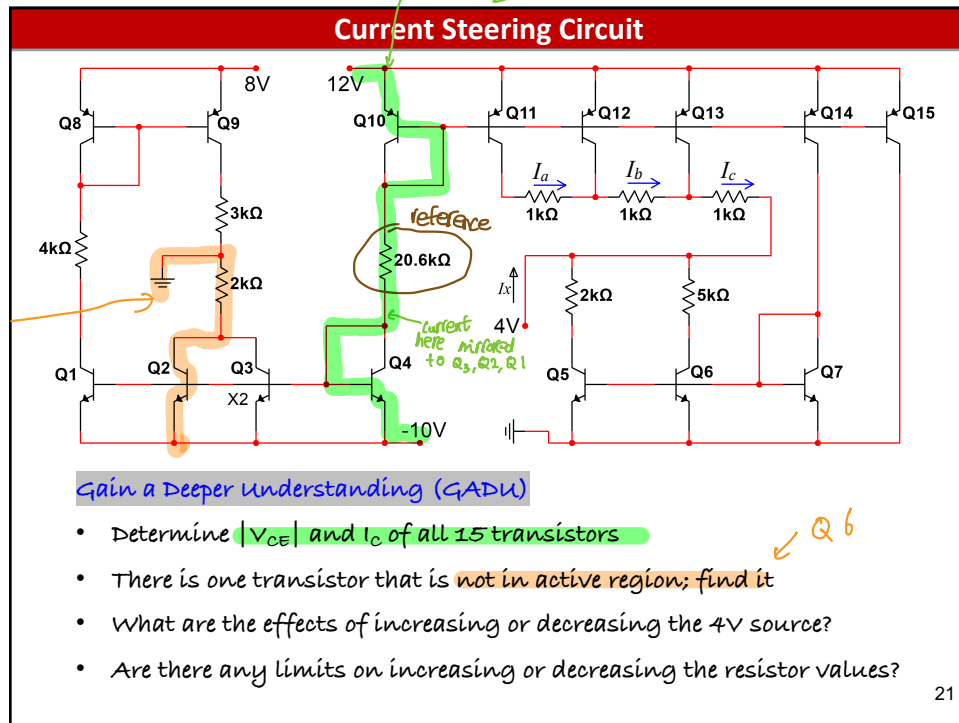

$$I_{C6(max)} = \frac{4 - 0.2}{5 \times 10^3} = 0.76 \text{ mA}$$

21

$$I_{REF} = I_{C4} = I_{C10} = 1 \text{ mA}$$

= all others except I_{C3} and I_{C6}

$$I_{C3} = 2 \text{ mA}$$

$$I_{C6} = 0.76 \text{ mA}$$