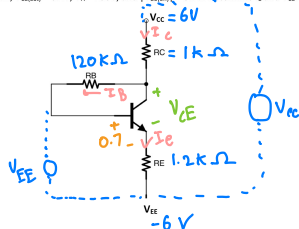


Assignment 1

1. Consider the following circuit where $V_{CC} = 6V$, $V_{EE} = -6V$, $\alpha = 0.9917356$, $R_C = 1k\Omega$, $R_B = 120k\Omega$, $R_E = 1.2k\Omega$, $V_{CE(sat)} = 0.2V$, $V_A = 150V$, and $|V_{BE(on)}| = 0.7V$. Determine I_C and V_{CE} .



$$\alpha = \frac{I_C}{I_E} \quad \beta = \frac{\alpha}{1-\alpha} = 120.0009196 = \frac{I_C}{I_B}$$

$$V_{CC} - (\beta+1)I_B R_C - I_B R_B - V_{BE} - (\beta+1)I_B R_E - V_{EE} = 0$$

$$V_{CC} - I_B [(\beta+1)(R_C + R_E) + R_B] - V_{BE} - V_{EE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE} - V_{EE}}{R_B + (\beta+1)(R_C + R_E)} = \frac{6 - 0.7 - (-6)}{120k + (121)(1.2k + 1k)} = 29.2 \mu A$$

$$I_C = \beta I_B = 3.5 mA$$

KVL in output loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E - V_{EE} = 0$$


$$V_{CC} - I_C (R_C + R_E) - V_{CE} - V_{EE} = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E) - V_{EE}$$

$$= 6 - 3.5mA(1k + 1.2k) - (-6)$$

$$V_{CE} = 4.3 V$$

2. Consider the following circuit where $V_{CC} = 10V$, $\beta = 140$, $R_C = 1k\Omega$, $R_B = 80k\Omega$, and $R_E = 1k\Omega$, $R_L = 2k\Omega$, $V_{CE(sat)} = 0.2V$, $V_A = 150V$, and $|V_{BE(on)}| = 0.7V$. Determine I_C and V_{CE} .

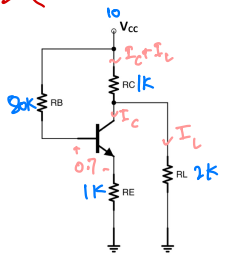

Emitter-bias config

$$\beta = \frac{I_C}{I_B}$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{140}{141} = 0.9929078014$$

$$\alpha = \frac{I_C}{I_E}$$

$$I_C = \alpha I_E$$

$$\beta = \frac{\alpha I_E}{I_B} \Rightarrow I_B = \frac{\alpha I_E}{\beta}$$

KVL:

$$V_{CC} - I_B R_B - V_{BE(on)} - I_E R_E = 0$$

$$V_{CC} - V_{BE} - I_B (R_B + R_E (\beta+1)) = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + R_E (\beta+1)} = \frac{10 - 0.7}{80k + 1k(141)} = 42.1 \mu A$$

$$I_C = (\beta+1)(I_B)$$

$$= 5.94 mA$$

KVL

$$10 - 1000I_1 + 2000I_2 = 0$$

$$10 = 2000I_1 + 2000(I_1 - (5.9 \text{ mA}))$$

$$10 = 1000I_1 + 2000I_1 - 11.8$$

$$I_1 = 7.27 \text{ mA}$$

wrong
saturation

finding V_C, V_B

$$10 - 1000I_C = V_C$$

$$V_C = 4.1 \text{ V}$$

$$V_B = 10 - 80 \mu A I_B$$

$$= 6.6$$

forward biased

KVL inner

$$10 - 1000I_1 - V_{CE} - 1000I_E = 0$$

$$V_{CE} = -3.2 \text{ V}$$

can't
be -ve

$$\text{so } V_E = 5.9 \text{ V}$$

$$\therefore V_{CE} = 0.2 \text{ V}$$

$$V_{CC} - I_1 R_1 - 2 \mu A I_2 = 0 \Rightarrow 10 \mu A I_1 + 2 \mu A I_2$$


$$I_2 = 5 \text{ mA} - 0.5 I_1 \quad \therefore I_2 = I_1 - I_C$$

$$5 \text{ mA} - 0.5 I_1 = I_1 - I_C \Rightarrow I_C = 1.5 I_1 - 5 \text{ mA}$$


$$I_C = 0.79 \text{ mA}$$

3. Consider the following circuit where $V_{CC} = 14 \text{ V}$, $\beta = 60$, $R_C = 1 \text{ k}\Omega$, $R_1 = 60 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_E = 0.5 \text{ k}\Omega$, $V_{CE(\text{sat})} = 0.2 \text{ V}$, $V_A = 150 \text{ V}$, and $|V_{BE(\text{on})}| = 0.7 \text{ V}$. Determine I_C and V_{CE} .

voltage
divider
w/ Emitter
resistor

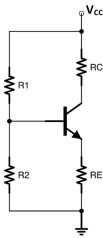

Thevenin Equivalent

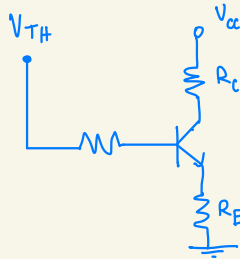

$$R_B = R_1 // R_2$$

$$= 4615.3846 \Omega$$

$$I = \frac{V_{CC}}{R_1 + R_2}$$

$$V_{TH} = I_2 R = \frac{R_1 V_{CC}}{R_1 + R_2}$$

$$I = \frac{5 \text{ k} \cdot 14}{65 \text{ k}} = 1.077$$

$$\approx 1.1 \text{ V}$$

KVL input

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + R_C(\beta + 1)} = \frac{1.1 - 0.7}{4615 + 500(61)} = 11.4 \mu A$$

$$I_C = \beta I_B = 60 \cdot 11.4 \mu A = 0.68 \text{ mA}$$


output KVL

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 12.98 \text{ V}$$

4. Consider the following circuit where $V_{CC} = 8V$, $\beta = 150$, $R_C = 4k\Omega$, $R_1 = 68k\Omega$, $R_2 = 8k\Omega$, $V_{CE(sat)} = 0.2V$, $V_A = 200V$, and $|V_{BE(on)}| = 0.7V$. Determine I_C and V_{CE} .

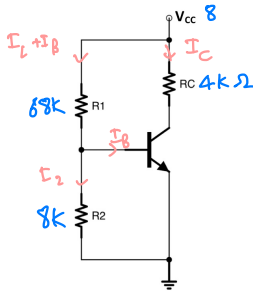

By KVL:

$$8 - (I_2 + I_B)R_1 - I_C R_C = 0$$

$$V_2 = 0.7 \quad \therefore V_2 = I_2 R_2$$

$$I_2 = \frac{V_2}{R_2} = \frac{0.7}{8000} = 8.75 \times 10^{-5} A$$

$$8 - I_2 R_1 - I_B R_1 - I_C R_C = 0$$

$$\hookrightarrow I_B = (8 - I_2 R_1 - I_C R_C) / R_1$$

$$= 1.985 \times 10^{-5} A$$

$$I_C = \beta I_B = 2.978 \times 10^{-3} A$$

$$V_C = 8 - I_C R_C = 8 - (2.978 \times 10^{-3}) 4000 = -3.912V \quad \text{not possible}$$

$$\therefore V_{CE(sat)} = 0.2V$$


By KVL:

$$8 - I_C R_C - 0.2 = 0 \quad \rightarrow \quad I_C = \frac{7.8}{R_C}$$

$$I_C = 1.95 \times 10^{-3} A$$

5. Consider the following circuit where $V_{CC} = 12V$, $\beta = 60$, $R_C = 2k\Omega$, $R_1 = 45k\Omega$, $R_2 = 4k\Omega$, $V_{CE(sat)} = 0.2V$, $V_A = 200V$, and $|V_{BE(on)}| = 0.7V$. Assume that the maximum and minimum base currents are $I_{B(max)} = 150\mu A$ and $I_{B(min)} = 5\mu A$. Determine:

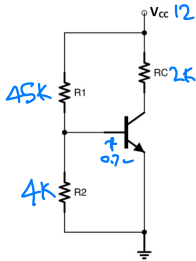- The maximum and minimum values of R_2 , which satisfies the base current limits. Assume all other values remain unchanged
- The maximum and minimum values of R_1 , which satisfies the base current limits. Assume all other values remain unchanged
- The maximum and minimum values of R_1 , which satisfies the base current limits. Assume all other values remain unchanged



$$I_B = (V_{CE} - 0.7) / R_1 - (0.7 / R_2)$$

$$= 7.611 \times 10^{-5} A$$

$$I_C = \beta I_B = 4.567 \times 10^{-3} A$$

$$I_2 = \frac{0.7}{4000} = 1.75 \times 10^{-4} A$$

$$I_1 = \frac{(12 - 0.7)}{4500} = 2.511 \times 10^{-4} A$$

$$V_{CE} = V_{CE} - \beta I_B \times R_C = 12 - (60)(7.611 \times 10^{-5})(2000)$$

$$= 2.867V$$

$$V_1 = I_1 R_1 = (2.511 \times 10^{-4}) / (45000) = 11.2995V$$

(a)

$$I_C = \beta I_B \quad \therefore I_{C(min)} = 60 (5 \times 10^{-6}) = 3 \times 10^{-4} A$$

$$I_{C(max)} = 60 (150 \times 10^{-6}) = 9 \times 10^{-3} A$$

By KVL:

$$V_{CC} - I_C R_C - V_{CE} = 0 \rightarrow R_C = \frac{V_{CC} - V_{CE}}{I_C} = R_C$$

$$\therefore R_{C(max)} = \frac{12 - 2.867}{9 \times 10^{-3}} = 13,014.56 \, \Omega$$

$$R_{C(min)} = \frac{12 - 2.867}{3 \times 10^{-4}} = 390,436.67 \, \Omega$$

b) $R_2 = \frac{V_2}{I_2}$

$$I_2 = I_1 - I_B$$

$$I_{2(max)} = (2.511 \times 10^{-4}) - (5 \times 10^{-6}) = 2.46 \times 10^{-4} \, A$$

$$I_{2(min)} = (2.511 \times 10^{-4}) - (150 \times 10^{-6}) = 1.011 \times 10^{-4} \, A$$

$$R_{2(min)} = \frac{0.7}{2.461 \times 10^{-4}} = 2844.372 \, \Omega$$

$$R_{2(max)} = \frac{0.7}{1.011 \times 10^{-4}} = 6923.838 \, \Omega$$

c) $I_1 = I_2 + I_B$



$$I_{1(max)} = 1.75 \times 10^{-4} + 9 \times 10^{-3} = 9.175 \times 10^{-3}$$

$$I_{2(min)} = 1.75 \times 10^{-4} + 3 \times 10^{-4} = 4.75 \times 10^{-4}$$

$$R_1 = \frac{V_1}{I_1} \rightarrow R_{1(max)} = \frac{11.2995}{9.175 \times 10^{-3}} = 1231.55 \, \Omega$$

$$R_{1(min)} = \frac{11.2995}{4.75 \times 10^{-4}} = 23,788.42 \, \Omega$$

6. Consider the following circuit where $V_{CC} = 20V$, $\beta = 100$, $V_{CE(sat)} = 0.2V$, $V_A = 230V$, $|V_{BE(on)}| = 0.7V$. Design the circuit (Determine R_1 , R_2 , R_C , and R_E) so that the transistor operates at $V_{CE} = 6V$ and $I_C = 2.5mA$. Given that $R_C = R_E$ and $I_{B2} = 2I_{B1}$.

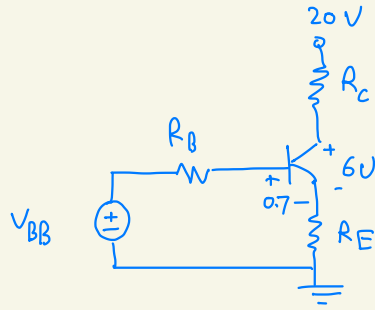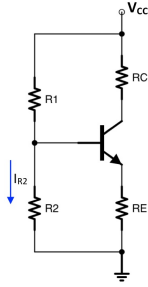

$$V_{BB} = \frac{V_{CC} R_2}{R_1 + R_2} = \frac{20 R_2}{R_1 + R_2}$$

$$R_B = \frac{R_1 + R_2}{R_1 \times R_2}$$

$$\beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.5 \times 10^{-3}}{100} = 2.5 \times 10^{-5} A$$

$$I_E = \frac{I_C (1 + \beta)}{\beta} = 2.525 \times 10^{-3} A$$

By KVL:

$$20 - I_C R_C - 6 - I_E R_E = 0$$

$$R_C = R_E$$

$$\therefore 14 = R_E (I_C + I_E)$$

$$R_E = \frac{14}{I_C + I_E} = R_C = 2786.07 \Omega$$

$$I_1 = I_2 + I_B$$

$$I_1 = 5 \times 10^{-5} + 2.5 \times 10^{-5}$$

$$I_2 = 2I_B = 5 \times 10^{-5}$$

$$= 7.5 \times 10^{-5} A$$

$$V_2 = 0.7 + V_E = 0.7 + (2.525 \times 10^{-3}) (2786.07) = 7.735 V$$


$$R_2 = \frac{V_2}{I_2} = \frac{7.735}{5 \times 10^{-5}} = 154.7 k\Omega$$

$$R_1 = \frac{V_1}{I_1} = \frac{12.265}{7.5 \times 10^{-5}} = 163.5 k\Omega$$

by KVL:

$$V_{CC} - V_1 - V_2 = 0 \rightarrow V_1 = V_{CC} - V_2 = 20 - 7.735 = 12.265$$

7. Design the following circuit so that the transistors operate at $I_{C1} = 2\text{mA}$, $I_{C2} = 2\text{mA}$, $I_{C3} = 4\text{mA}$, $V_1 = 2\text{V}$, $V_2 = -3\text{V}$, and $V_3 = 0\text{V}$. Also given that $V_{CC} = 10\text{V}$, $V_{EE} = -10\text{V}$, $\beta = \infty$ (i.e., ignore base current), $V_{CE(\text{sat})} = 0.2\text{V}$, $V_A = 300\text{V}$, and $|V_{BE(\text{on})}| = 0.7\text{V}$.

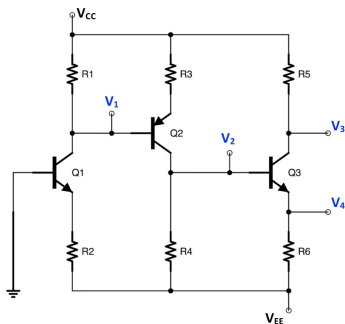

$$R_5 = \frac{V_{CC} - V_3}{I_{C3}} = \frac{10}{4\text{mA}} = 2500\Omega$$

$$R_4 = \frac{V_2 - V_{EE}}{I_{C2}} = \frac{-3 - (-10)}{2\text{mA}} = 3500\Omega$$

$$\beta = \infty, \text{ so } I_C = I_E$$

$$R_1 = \frac{V_{CC} - V_1}{I_{C1}} = \frac{10 - 2}{2\text{mA}} = 4000\Omega$$

$$-V_{BE} - I_E R_2 - (-10\text{V}) = 0$$

$$R_2 = \frac{10 - 0.7}{2\text{mA}} = 4650\Omega$$

$$V_{B2} = 2\text{V}, V_{C2} = -3\text{V} \Rightarrow V_{BC2} = 5\text{V}$$

F.B

$$V_{E2} = 0.7 + 5 = 5.7\text{V}$$

$$\text{So, } 10 - I_{C2} R_3 - 5.7 - (-10) = 0$$

$$R_3 = \frac{7.3}{2\text{mA}} = 3650\Omega$$

$$V_2 = -3, V_4 = -3.7\text{V}$$

$$R_6 = \frac{V_4 - V_{EE}}{I_{E3}} = \frac{-3.7 - (-10)}{4\text{mA}} = 1575\Omega$$