

Practice Problem Set #1
Transistor Biasing Basic
ENEL469: Analog Electronics

1. For a BJT, we know that $I_E = I_C + I_B$, $\beta = I_C/I_B$, and $\alpha = I_C/I_E$. Using these three equations, show that


$$\alpha = \beta/(\beta + 1) \text{ and } \beta = \alpha/(1 - \alpha)$$

Note: these equations will be frequently used for problem solving in this course

2. Consider the following BJT circuit where two separate sources are used for simplicity.

Given, $\beta = 80$, $V_{BE(on)} = 0.7V$, $V_{BB} = 1.5V$, $V_{CC} = 8V$, $R_B = 80k$, and $R_C = 5k$.


Determine α , I_B , I_C , and V_{CE} .

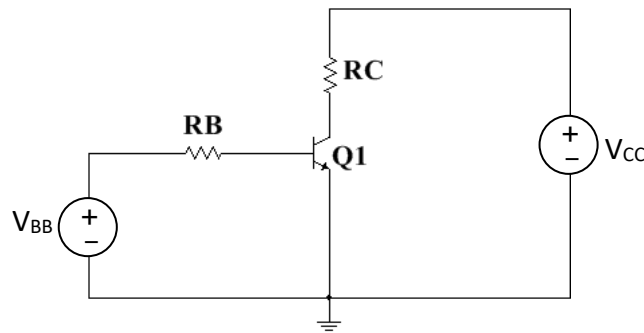

3. Consider the following BJT circuit where two separate sources are used for simplicity.

Given, $\alpha = 0.9836$, $V_{BE(on)} = 0.7V$, $V_{BB} = 5.2V$, $V_{CC} = 3V$, $R_B = 90k$, and $R_C = 0.5k$.

Determine I_B , I_C , and V_{CE} .

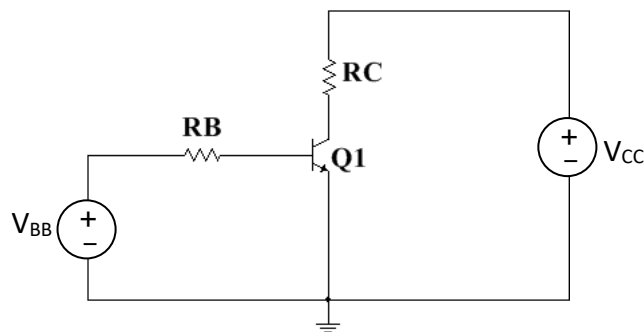

Additional thoughts

- In this example, V_{CC} is less than V_{BB} . Is the transistor properly biased?

1. For a BJT, we know that $I_E = I_C + I_B$, $\beta = I_C/I_B$, and $\alpha = I_C/I_E$. Using these three equations, show that

$$\alpha = \beta/(\beta + 1) \text{ and } \beta = \alpha/(1 - \alpha)$$

Note: these equations will be frequently used for problem solving in this course

$$I_E = I_C + I_B$$

$$I_B = I_E - I_C$$

$$\alpha = \frac{I_C}{I_E}$$

$$\div \text{ by } I_B$$

$$\alpha = I_C/I_B$$

$$\rightarrow I_E/I_B$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{I_C}{I_B}$$

$$= \frac{I_C}{I_E - I_C}$$

$$\div \text{ by } I_E$$

$$= \frac{I_C/I_E}{I_E/I_E - I_C/I_E}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

\div all by I_B

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + 1$$

$$I_E = I_B (\beta + 1)$$

$$\frac{I_E}{I_B} = \beta + 1$$


2. Consider the following BJT circuit where two separate sources are used for simplicity.

Given, $\beta = 80$, $V_{BE(on)} = 0.7V$, $V_{BB} = 1.5V$, $V_{CC} = 8V$, $R_B = 80k$, and $R_C = 5k$.

Determine α , I_B , I_C , and V_{CE} .

npn

common-emitter

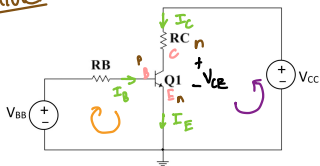

why - and not +?

$$V_{BB} - I_B R_B - V_{BE(on)} = 0$$

$$V_{BB} = I_B R_B + V_{BE(on)}$$

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$

$$= \frac{1.5 - 0.7}{80,000} = 10 \mu A$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$


$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 8 - (0.8 \times 10^{-3} \times 5000) \\ &= 4V \end{aligned}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{80}{80 + 1} = 0.987654321$$

$$\text{using } \beta = \frac{I_C}{I_B}$$

$$\begin{aligned} I_C &= \beta I_B \\ &= 0.8 \text{ mA} \end{aligned}$$

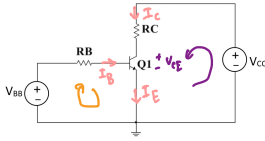3. Consider the following BJT circuit where two separate sources are used for simplicity.
 Given, $\alpha = 0.9836$, $V_{BE(on)} = 0.7V$, $V_{BB} = 5.2V$, $V_{CC} = 3V$, $R_B = 90k$, and $R_C = 0.5k$.
 Determine I_B , I_C , and V_{CE} .



Additional thoughts

- In this example, V_{CC} is less than V_{BB} . Is the transistor properly biased?

$$\beta = \frac{\alpha}{1-\alpha} = 59.97560976$$

$$\beta = \frac{I_C}{I_B}$$

yes it's 'properly' biased
 since BE is fwd biased
 while CB is rev biased

$$V_{BB} - I_B R_B - V_{BE(on)} = 0$$

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$


$$= \frac{5.2 - 0.7}{90,000} = 50 \mu A$$

$$\begin{aligned} \text{using } I_C &= \beta I_B \\ &= 59.97560975 \times 50 \mu A \\ &= 3 \text{ mA} \end{aligned}$$


$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 3 - (3 \times 10^{-3} \cdot 0.5k) \\ &= 1.5 \text{ V} \end{aligned}$$

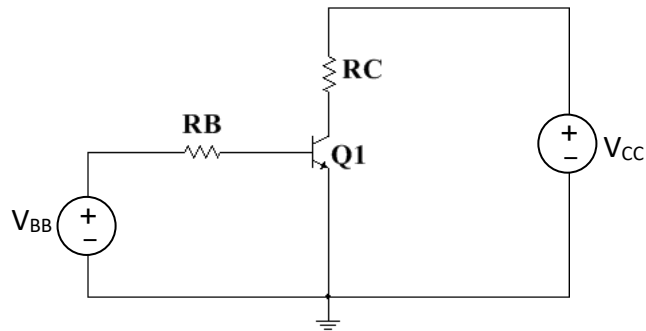4. Consider the following BJT circuit where two separate sources are used for simplicity. Design a BJT biasing circuit for which I_C should be set to 6mA. The collector-base junction is reverse biased by 7.8V. Also, given that $\beta = 150$, $V_{BE(on)} = 0.7V$, $V_{BB} = 2.3V$, and $R_C = 1.5k$. (Hint: determine R_B and V_{CC})



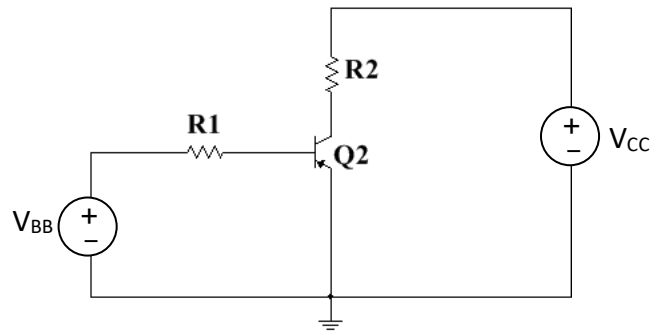
5. Consider the following BJT circuit where two separate sources are used for simplicity.
 Given, $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_{BB} = 3.5V$, $V_{CC} = 10V$, $R_B = 50k$, and $R_C = 3k$.
 Determine I_B , I_C , and V_{CE} .



Additional thoughts

- Have you noticed anything strange in biasing?
- What type of biasing the emitter-base junction has?
- What type of biasing the base-collector junction has?

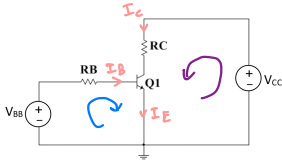4. Consider the following BJT circuit where two separate sources are used for simplicity. Design a BJT biasing circuit for which I_C should be set to 6mA. The collector-base junction is reverse biased by 7.8V. Also, given that $\beta = 150$, $V_{BE(on)} = 0.7V$, $V_{BB} = 2.3V$, and $R_C = 1.5k$. (Hint: determine R_B and V_{CC})



$$V_B = 0.7$$

$$V_C = 0.7 + 7.8 = 8.5V$$

$$\text{since } V_E = 0$$

$$V_{CE} = 8.5V$$

$$\beta = 150 = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{6 \times 10^{-3}}{150} = 40 \mu A$$

$$V_{CC} - I_C R_C - V_{CE} = 0$$


$$V_{CC} = (6 \times 10^{-3} \cdot 1.5 \times 10^3) + 8.5V = 9 + 8.5 = 17.5$$

$$V_{BB} - I_B R_B - V_{BE(on)} = 0$$

$$R_B = \frac{V_{BB} - V_{BE(on)}}{I_B}$$

$$= \frac{2.3 - 0.7}{40 \times 10^{-6}} = 40k$$

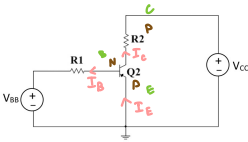5. Consider the following BJT circuit where two separate sources are used for simplicity. Given, $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_{BB} = 3.5V$, $V_{CC} = 10V$, $R_B = 50k$, and $R_C = 3k$. Determine I_B , I_C , and V_{CE} .



Additional thoughts

- Have you noticed anything strange in biasing?
- What type of biasing the emitter-base junction has?
- What type of biasing the base-collector junction has?

* idk *


BE junction is reverse biased
therefore $I_B = 0$

$$\therefore \beta = \frac{I_C}{I_B} \Rightarrow I_C = \beta I_B = 0$$

$$V_{CE} = V_{CC} = 10V$$

↑
cuz no voltage drop across R_C

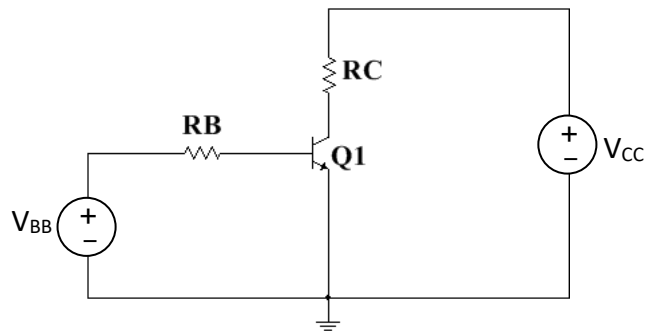
6. Consider the following BJT circuit where two separate sources are used for simplicity.
 Given, $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_{BB} = 2.3V$, $V_{CC} = 10V$, $R_B = 20k$, and $R_C = 2k$.
 Determine I_B , I_C , and V_{CE} .




Additional thoughts

- Have you noticed anything that does not make sense?
- Apply KVL at the output (i.e., R_C , V_{CE} , and V_{CC}) circuit. Have you noticed now?

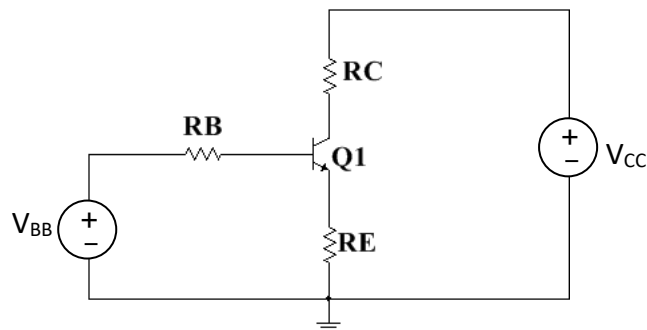7. Consider the following BJT circuit where two separate sources are used for simplicity. Given, $\beta = 80$, $V_{BE(on)} = 0.7V$, $V_{BB} = 1.5V$, $V_{CC} = 6V$, $R_E = 500\Omega$, $R_B = 80k$, and $R_C = 5k$. Determine I_B , I_C , and V_{CE} .



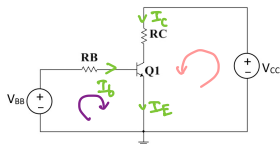6. Consider the following BJT circuit where two separate sources are used for simplicity. Given, $\beta = 100$, $V_{BE(on)} = 0.7V$, $V_{BB} = 2.3V$, $V_{CC} = 10V$, $R_B = 20k$, and $R_C = 2k$. Determine I_B , I_C , and V_{CE} .



Additional thoughts

- Have you noticed anything that does not make sense?
- Apply KVL at the output (i.e., R_C , V_{CE} , and V_{CC}) circuit. Have you noticed now?

$$V_{CC} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - (8 \times 10^{-3} \cdot 2000)$$

$$= 10 - 16$$


$= -6$ not possible, the transistor will be saturated

$$V_{CE} \approx V_{CE(sat)} \approx 0.3V$$

$$I_C R_C = V_{CC} - V_{CE(sat)} \text{ and so on}$$

what does this mean?

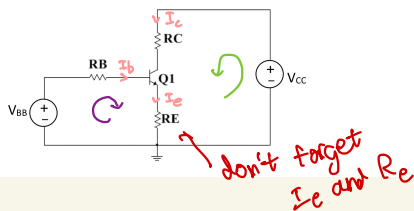7. Consider the following BJT circuit where two separate sources are used for simplicity. Given, $\beta = 80$, $V_{BE(on)} = 0.7V$, $V_{BB} = 1.5V$, $V_{CC} = 6V$, $R_E = 500\Omega$, $R_B = 80k$, and $R_C = 5k$. Determine I_B , I_C , and V_{CE} .



$$V_{BB} - I_B R_B - V_{BE(on)} = 0$$

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$

$$= \frac{1.5 - 0.7}{80,000}$$

$$= 10 \mu A$$

$$\beta = \frac{I_C}{I_B}$$

$$I_C = \beta I_B$$

$$= 80 \times 10 \times 10^{-6}$$

$$= 0.8 \text{ mA}$$

$$I_E = I_B + I_C$$

$$= 810 \mu A$$

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 6 - (0.8 \times 10^{-3} \cdot 500) - (1.1 \times 10^{-3} \cdot 500)$$

X

$$V_{BB} - I_B R_B - V_{BE(on)} - I_E R_E = 0$$

$$V_{BB} = I_B R_B + V_{BE(on)} + I_E R_E$$

$$V_{BB} = I_B R_B + V_{BE(on)} + I_B (\beta + 1) R_E$$

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B + (\beta + 1) R_E}$$

$$V_{BE} = I_B R_B + V_{BE} + I_E R_E$$

$$= I_B R_B + V_{BE} + (I_B + I_C) R_E$$

$$= I_B R_B + V_{BE} + I_B (\beta + 1) R_E$$

$$\therefore I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1) R_E} = 6.6 \mu A$$

$$\therefore I_C = \beta I_B ; I_E = I_B + I_C = 0.5346 \text{ mA}$$

$$= 0.53 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 3.083 \text{ V}$$

recall

$$I_E = I_B (\beta + 1)$$