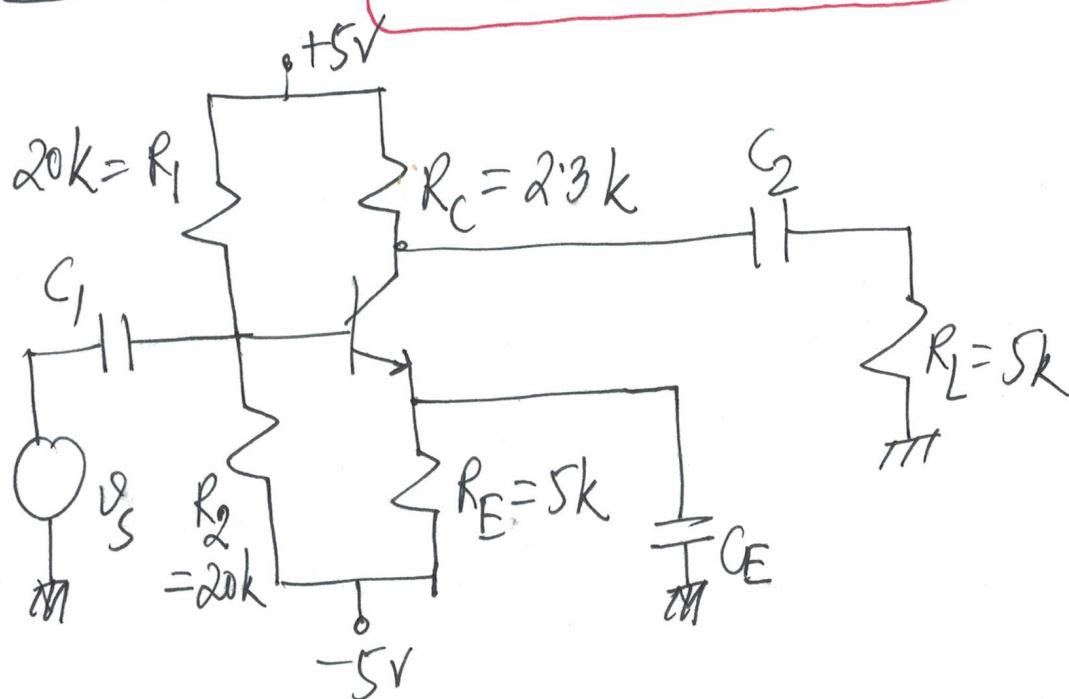


①

Practice Problem : 3
ENEL- 469

Problem 1 :



Given :

$$\beta = 125$$


$$V_{BE}(ON) = 0.7V$$

$$V_A = 200V$$

DC Analysis :

* All the capacitors are open circuit.

Equivalent Circuit :

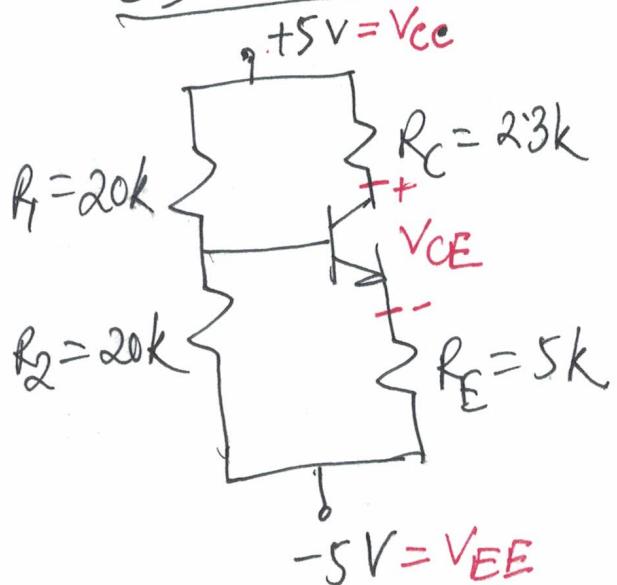

for DC Load Line,

Applying KVL in the collector loop:

$$\begin{aligned}
 V_{CC} - V_{EE} &= I_C R_C + V_{CE} + I_E R_E \\
 \Rightarrow 5 - (-5) &= I_C R_C + V_{CE} + \frac{\beta+1}{\beta} I_C R_E \\
 \Rightarrow 10 &= I_C \left(R_C + \frac{\beta+1}{\beta} R_E \right) + V_{CE} \\
 \Rightarrow V_{CE} &= 10 - \left(R_C + \frac{\beta+1}{\beta} R_E \right) I_C
 \end{aligned}$$

— (D)

(2)

Note that DC load lines indicate the linear relationships between V_{CE} and I_C .

From ①, we get the relationship between I_C and V_{CE} of the given circuit which is also known alternatively the mathematical expression for the DC load line.

$$V_{CE} = 10 - \left(R_C + \frac{\beta+1}{\beta} R_E \right) I_C$$

$$\therefore \text{slope} = - \left(R_C + \frac{\beta+1}{\beta} R_E \right)$$

$$= - \frac{1}{2.3k + 1.008 \times 5k}$$

$\boxed{\text{DC load line} = - \frac{1}{7.34k}}$

\leftarrow Note this
inverse is because
 V_{CE} in the X axis
and I_C in the
y-axis

$$I_C = - \frac{V_{CE}}{R_C + \frac{\beta+1}{\beta} R_E}$$


$$+ \frac{10}{R_C + \frac{\beta+1}{\beta} R_E}$$

(3)


AC Analysis:

- ⊗ Capacitors are short
- ⊗ DC voltages are short
- ⊗ DC current sources are open


Equivalent circuit:

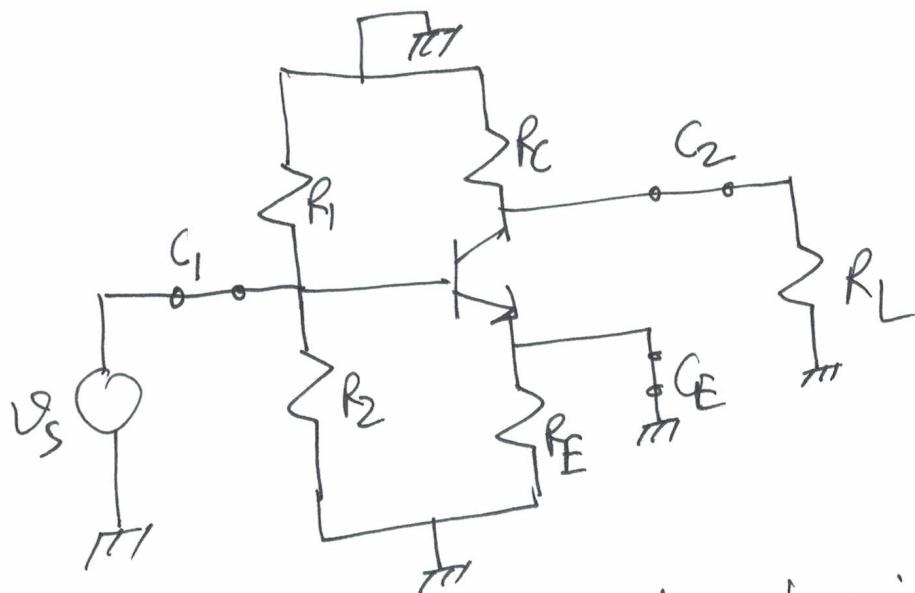

Small signal equivalent circuit:

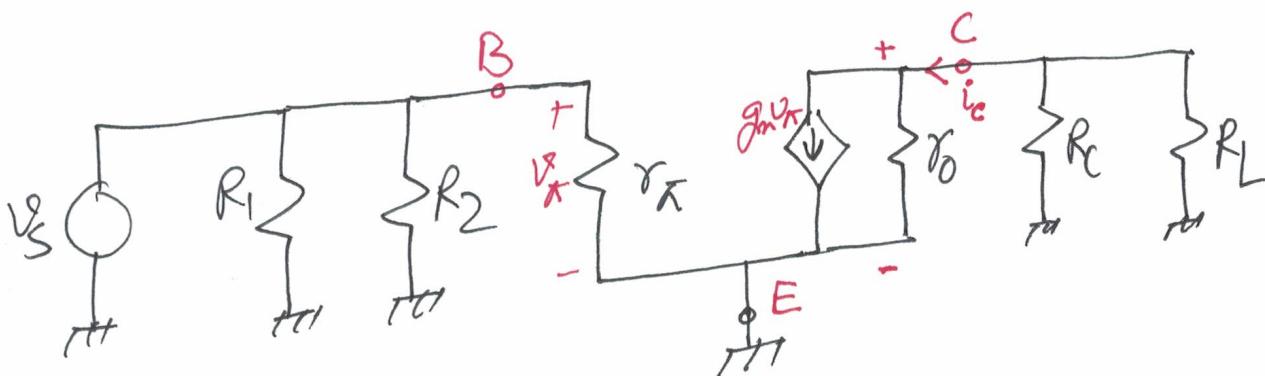

(4)

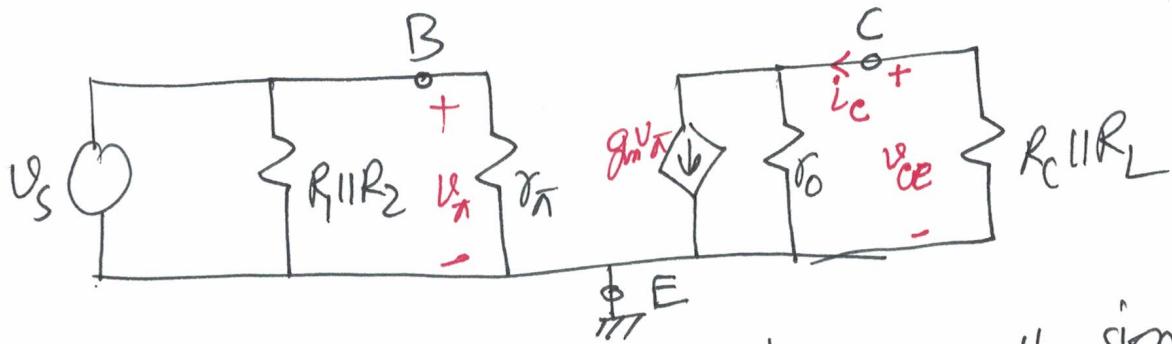


We can write from above small signal equivalent circuit:

$$v_{ce} = -i_c(R_C \parallel R_L)$$

$$\begin{aligned}\therefore \text{AC load line slope} &= -\frac{1}{R_C \parallel R_L} \\ &= -\frac{1}{2.3k \parallel 5k} \\ &= -\frac{1}{1.575k}\end{aligned}$$

DC and AC load lines:

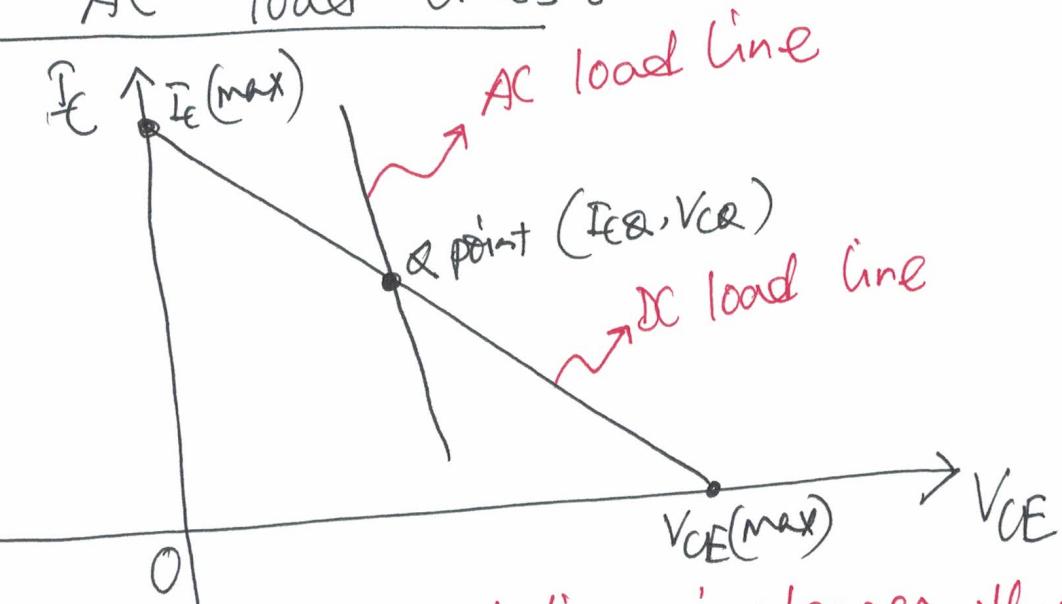


Note that the AC load line is steeper than the DC load line due to the slope differences.

(5)

Problem 2:

DC Analysis:

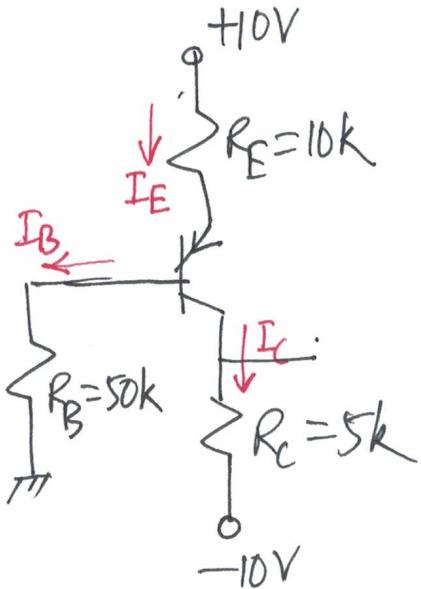

Given that:

$$\beta = 150$$

$$V_{EB(\text{ON})} = 0.7 \text{ V}$$

$$\text{and } V_A = \infty$$

Applying KVL in the E-B loop:

$$+10V = I_E R_E + V_{EB(\text{ON})} + I_B R_B$$

$$\Rightarrow +10V = (\beta + 1) I_B R_E + V_{EB(\text{ON})} + I_B R_B$$

$$\Rightarrow I_B = \frac{10 - 0.7}{(\beta + 1) R_E + R_B}$$

$$I_B = 5.96 \text{ mA}$$

$$\therefore I_C = \beta I_B = 0.894 \text{ mA} \quad \text{and}$$

$$I_E = (\beta + 1) I_B \\ = 0.90 \text{ mA}$$

(6)

Now, Applying KVL in the E-C loop:

$$+10 - (-10) = I_E R_E + V_{EC} + I_C R_C$$

$$\Rightarrow V_{EC} = 20 - I_E R_E - I_C R_C$$

$$\Rightarrow \boxed{V_{EC} = 6.53V}$$

Slope of the DC load line:

$$+10 - (-10) = I_E R_E + V_{EC} + I_C R_C$$


$$\Rightarrow 20 = \frac{\beta+1}{\beta} I_C R_E + V_{EC} + I_C R_C$$

$$\Rightarrow V_{EC} = 20 - \left(\frac{\beta+1}{\beta} R_E + R_C \right) I_C$$

$$\therefore \text{DC load line slope} = - \frac{1}{\frac{\beta+1}{\beta} R_E + R_C}$$

$$\approx - \frac{1}{15k}$$

AC Equivalent Circuit :

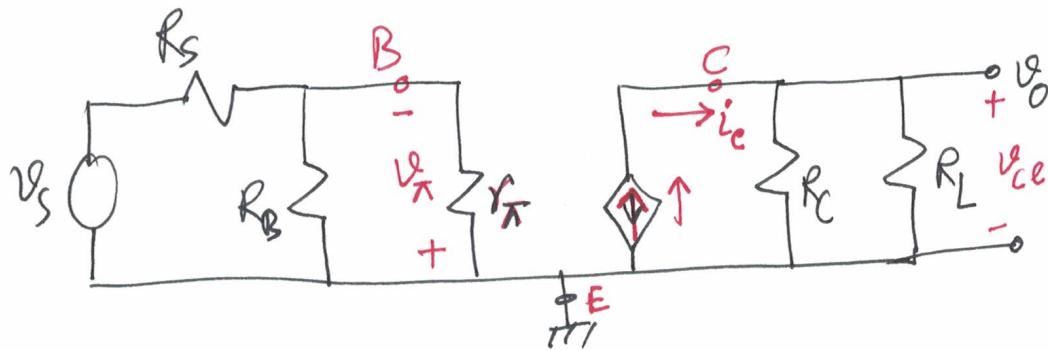


- # Note that the voltage and current source directions are changed for PNP transistor.
- # \$r_o\$ is not present since, \$V_A = \infty\$; \$\tau_0 = \infty\$

We can write: $v_{ce} = i_c (R_C \parallel R_L) \Rightarrow v_{ce} = -i_c (R_C \parallel R_L)$

$$\therefore \text{AC load line slope} = -\frac{1}{R_C \parallel R_L}$$


$$= -\frac{1}{1.43k}$$

Load Line's

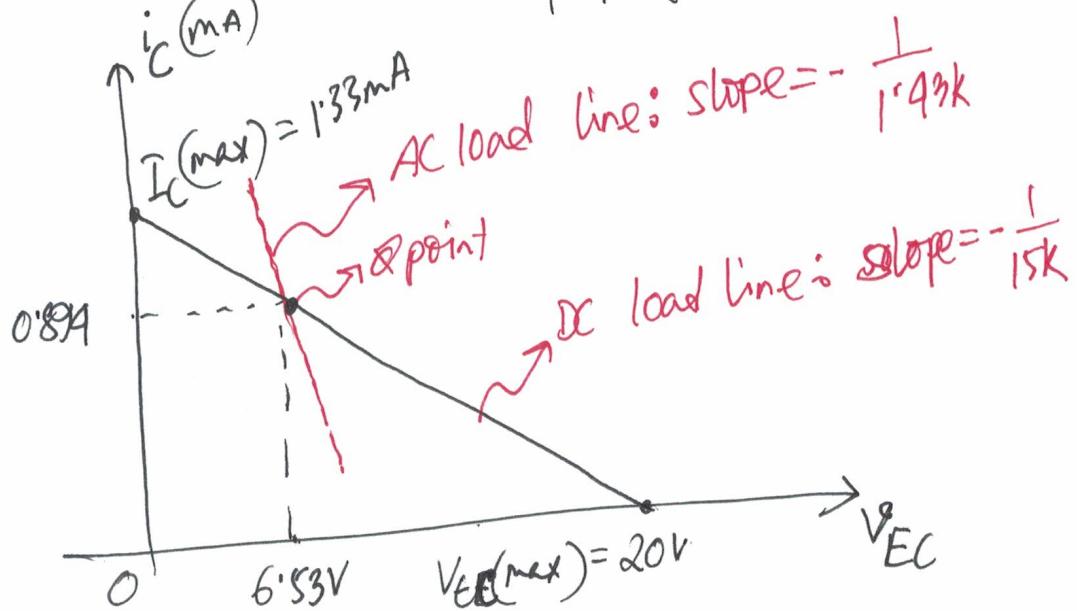

(8)

Problem 3:

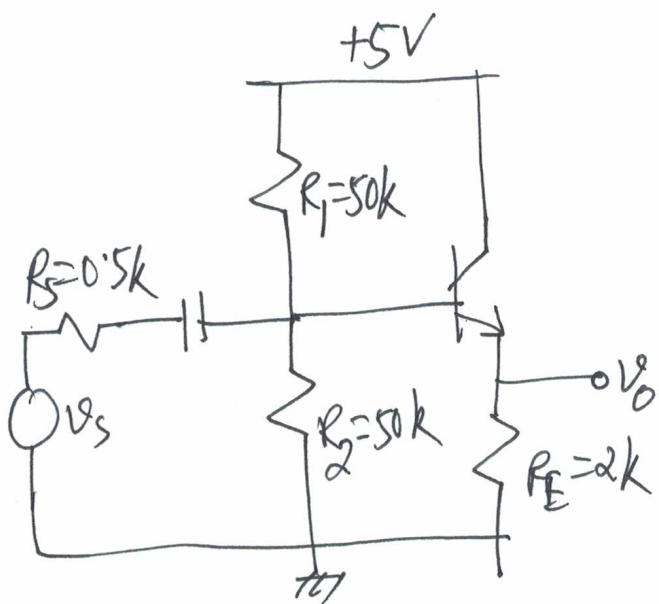

Givens:

$$\beta = 100$$

$$V_{BE(ON)} = 0.7V$$



$$V_A = 80V$$

~~approximate~~

Steps:

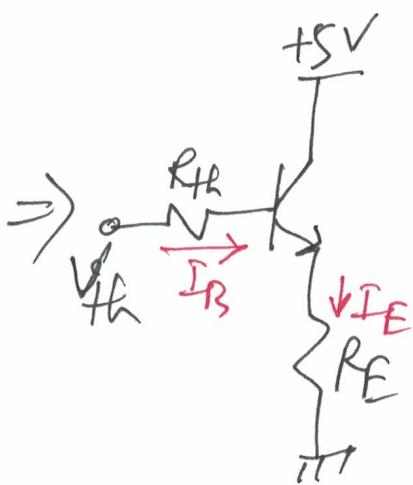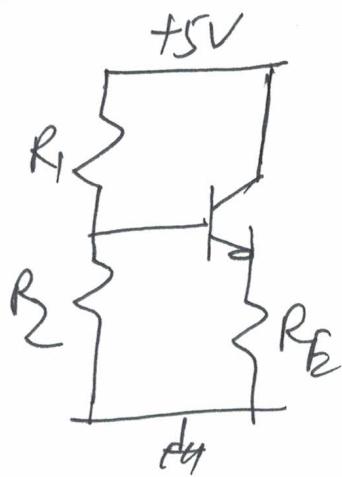1. find DC operating points (I_C , V_{CE})
2. find small signal parameters
3. find small-signal voltage gain from small-signal equivalent circuit.

Step 1: DC Analysis → Need to make sure the operating region of the transistor.
DC equivalent circuit:



$$R_{th} = R_1 \parallel R_2 = 25k$$

$$V_{th} = \frac{R_2}{R_1 + R_2} S = 2.5V$$

(9)

Now, applying KVL,

$$V_{Th} = I_B R_{Th} + V_{BE(ON)} + I_E R_E$$

$$\Rightarrow V_{Th} = \frac{I_C}{\beta} R_{Th} + V_{BE(ON)} + \frac{\beta+1}{\beta} I_C R_E$$

$$\Rightarrow I_C = 0.793 \text{ mA}$$

$$\text{Similarly; } +5 = V_{CE} + I_E R_E \Rightarrow V_{CE} = 3.4V$$

Step 2: small signal parameters

$$V_T = \frac{kT}{q} = 25 \text{ mV}$$


$$r_0 = \frac{V_A}{I_C} = \frac{80}{0.793 \text{ mA}} = 100 \text{ k}\Omega$$

$$r_I = \frac{V_I}{I_B} = \frac{V_T}{I_C/\beta} = 3.28 \text{ k}\Omega$$


$$r_E = \frac{V_T}{I_E} = \frac{V_T}{\frac{\beta+1}{\beta} I_C} = 32.475 \text{ }\Omega$$

$$g_m = I_C/V_T = 80.5 \text{ mA/V}$$

Step 3: small signal analysis

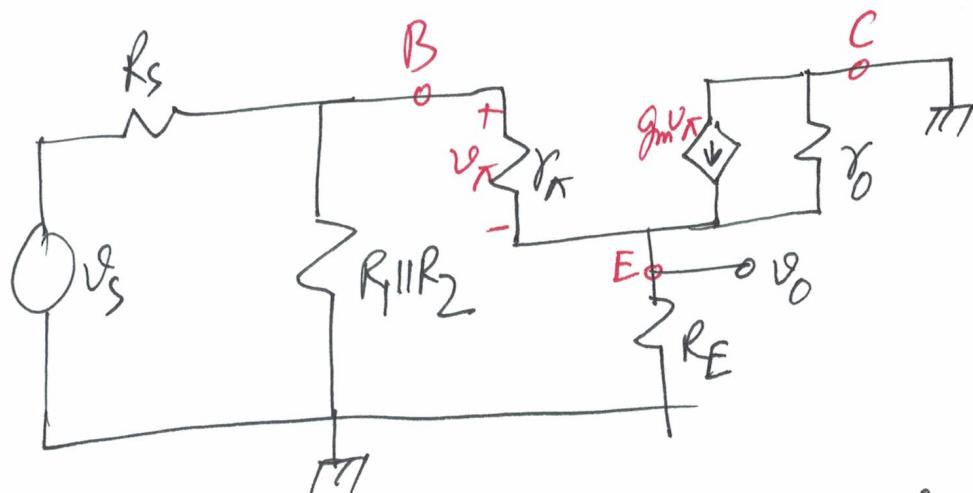

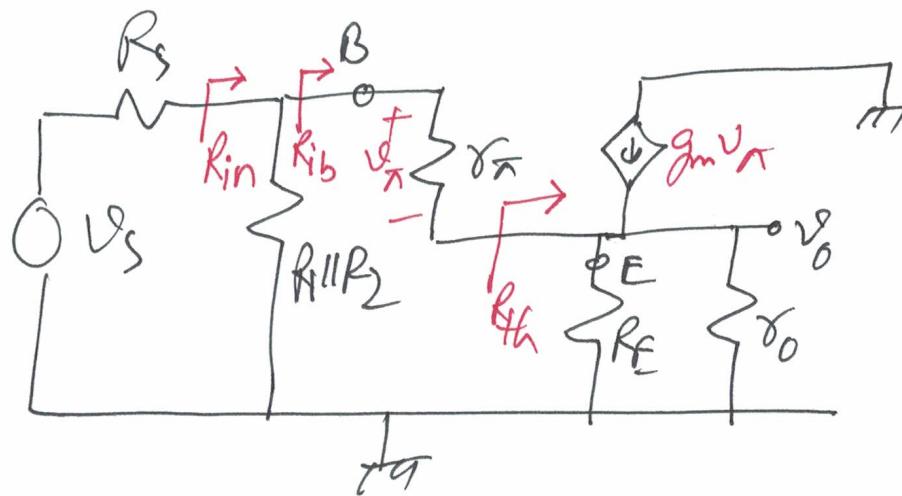Overall Small-signal gain, $A_{vo} = \frac{V_o}{V_s}$



$$\therefore V_o = V_s \frac{R_{in}}{R_s + R_{in}} \cdot \frac{R_{th}}{R_{th} + r_\pi}$$


$$R_{th} = (\beta + 1)(r_o \parallel R_E)$$

$$R_{th} = 201 \text{ k}\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel R_{th}$$


$$\Rightarrow \frac{V_o}{V_s} = \frac{R_{in}}{R_s + R_{in}} \cdot \frac{R_{th}}{R_{th} + r_\pi}$$

$$= 0.962$$

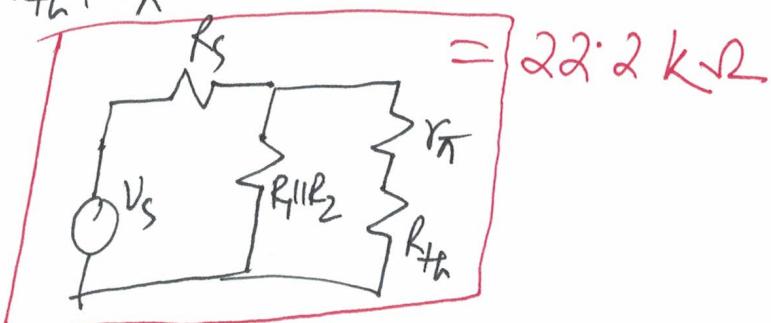

Problem 4:

(11)

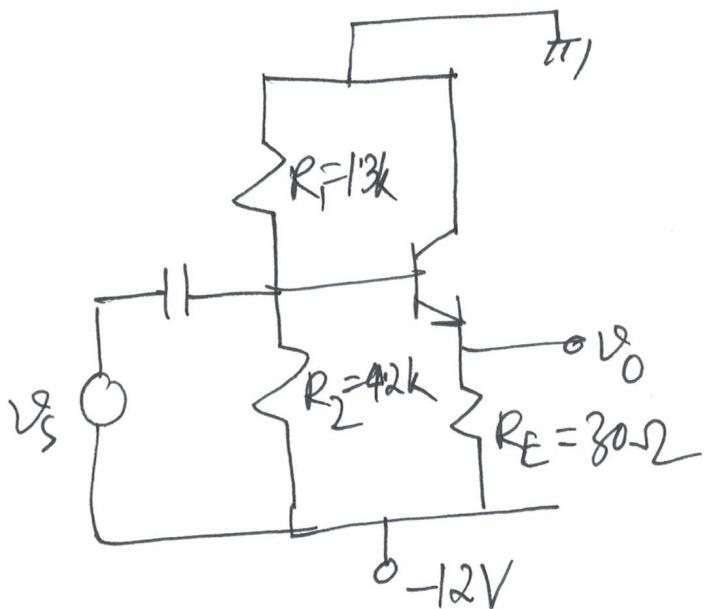



Given:

$$\beta = 80$$

$$V_{BE(ON)} = 0.7V$$

$$V_A = 75V$$

1. DC Analysis

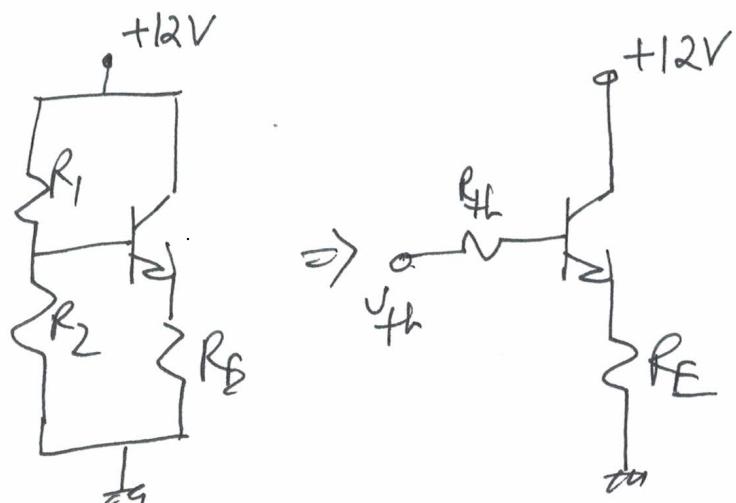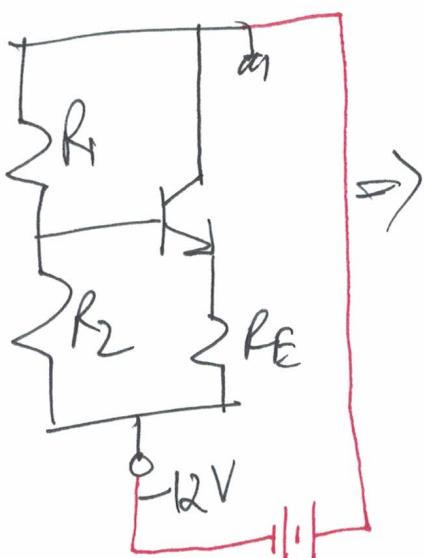

$$V_{th} = \frac{R_2}{R_1 + R_2} 12 = 9.16V$$

$$R_{th} = R_1 \parallel R_2 = 1k\Omega$$

$$\therefore V_{th} = I_B R_{th} + V_{BE} + I_E R_E \quad \Rightarrow I_E = 0.2A$$

$$\Rightarrow V_{th} = \frac{I_E}{\beta + 1} R_{th} + V_{BE} + I_E R_E$$

(12)

Also,

$$+12V = V_{CE} + I_E R_E$$

$$\boxed{\Rightarrow V_{CE} = 6V}$$

2. small signal parameters:


$$g_m = I_c / V_T = \frac{I_E \cdot \frac{\beta}{\beta+1}}{V_T} = 0.1975 \text{ A/V}$$

$$r_T = V_T / I_B = \frac{V_T}{I_E \cdot \frac{\beta}{\beta+1}} = 10.125 \Omega$$

$$r_o = V_A / I_c = V_A / \left(I_E \cdot \frac{\beta}{\beta+1} \right) = 379.69 \Omega$$

3. small signal analysis:

similar to problem 3:

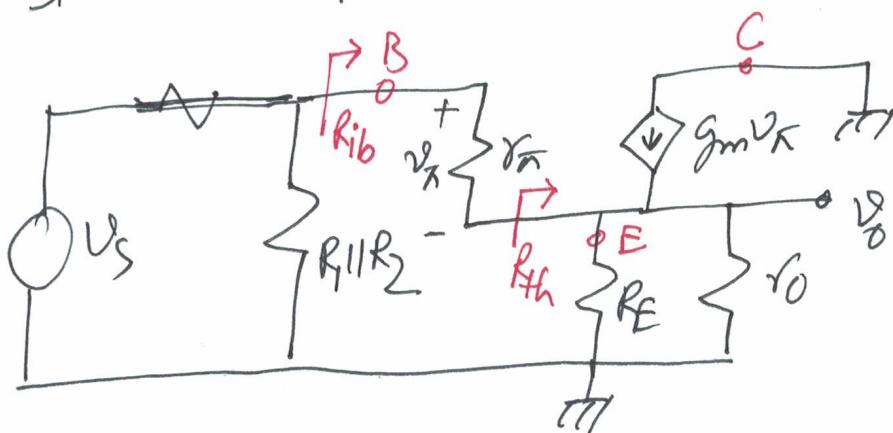

$$R_{th} = (\beta + 1) (r_o \parallel R_E) = 2.252 \text{ k}\Omega$$


$$R_{ib} = r_n + R_{th} = 2.262 \text{ k}\Omega$$

(13)

$$\therefore V_o = \frac{R_{th}}{R_i + R_{th}} V_s \Rightarrow \frac{V_o}{V_s} = \frac{R_{th}}{R_i + R_{th}} = \frac{R_{th}}{R_{ib}}$$

$$\Rightarrow \frac{V_o}{V_s} = \frac{2.252k}{2.262k} = 0.9956$$

Problem 5°

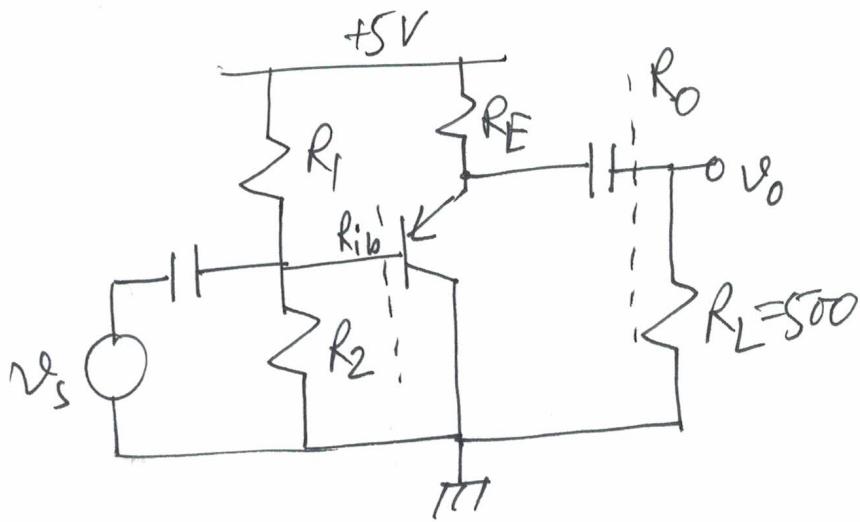

Given:



$$R_E = 2k$$

$$R_1 = R_2 = 50k$$

$$\beta = 100$$

$$V_{EB(\text{ON})} = 0.7V$$

$$V_A = 125V$$

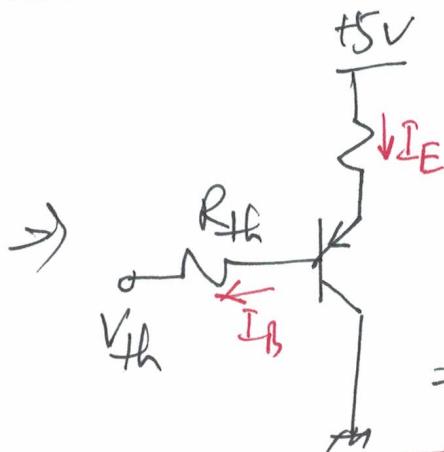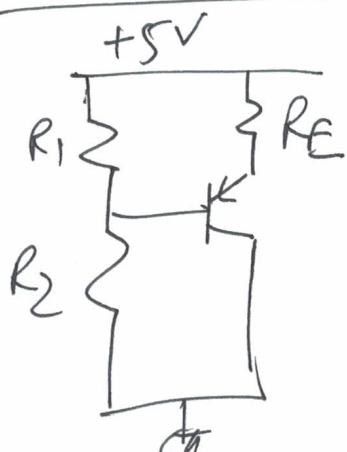DC Analysis:

$$R_{th} = R_1 \parallel R_2 = 25k$$

$$V_{th} = 2.5V$$

$$5 - V_{th} = I_E R_E + V_{EB} + I_E R_{th}$$

$$\Rightarrow 2.5 = I_E \left(R_E + \frac{R_{th}}{\beta+1} \right) + V_{EB}$$

$$\therefore V_{CE} = 5 - I_E R_E = 3.4V$$

$$\Rightarrow I_E = 0.8mA$$

small signal parameters:

(19)


$$r_T = \frac{V_T}{I_B} = \frac{V_T}{I_E(\beta+1)} = 3156 \text{ k}\Omega$$

$$r_0 = \frac{V_A}{I_C} = \frac{V_A}{I_E \cdot \frac{\beta}{\beta+1}} = 157.81 \text{ k}\Omega$$


$$g_m = \frac{I_C}{V_T} = \frac{I_E \cdot \frac{\beta}{\beta+1}}{V_T} = 31.68 \text{ mA/V}$$

$$r_e = \frac{V_T}{I_E} = 31.25 \text{ }\Omega$$

small signal analysis:

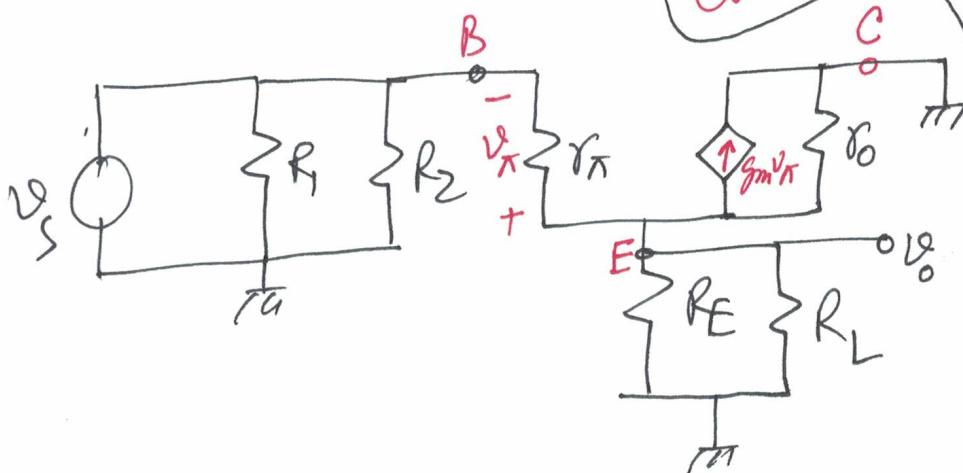

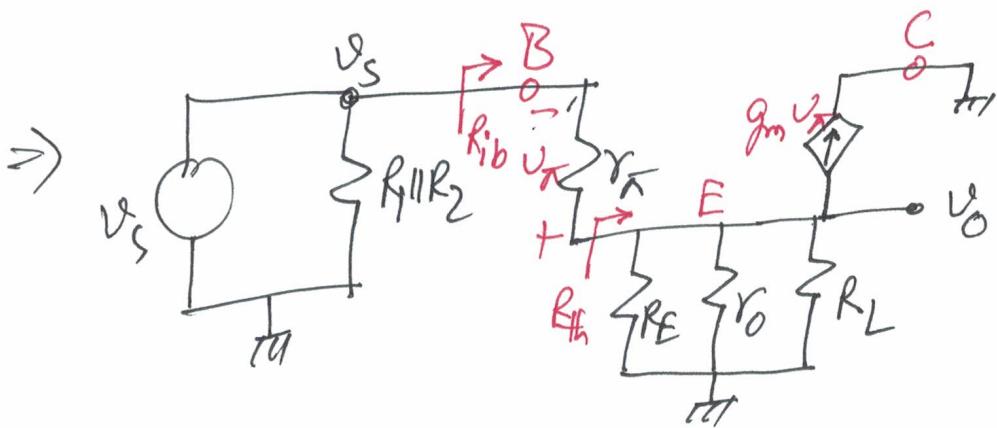Note that: for NPN transistor current source direction from Emitter to collector is defined from E to B as well





(15)

$$R_{ib} = r_\pi + (R_E \parallel r_o \parallel R_L)(\beta+1)$$

$$= 3.156 \text{ k} + 398.98 \cdot (\beta+1)$$

$$R_{ib} = 43.855 \text{ k}\Omega$$

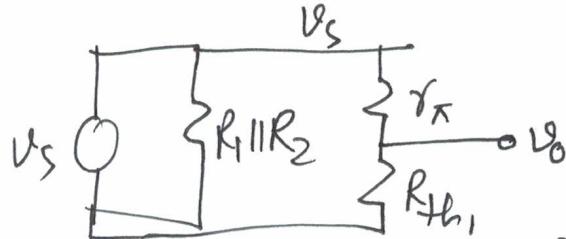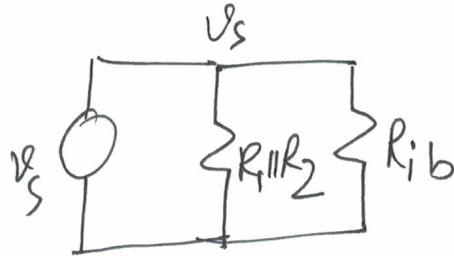


$$\therefore V_o = V_s \frac{R_{Th1}}{r_\pi + R_{Th1}}$$

$$= V_s \frac{R_{Th}}{R_{ib}}$$

$$\Rightarrow \boxed{\frac{V_o}{V_s} = \frac{R_{Th}}{R_{ib}}} \\ = 0.92$$

$$\begin{aligned} R_{Th1} &= (R_E \parallel r_o \parallel R_L)(\beta+1) \\ &= 398.98 \times (\beta+1) \\ &= 40.3 \text{ k}\Omega \end{aligned}$$

Calculation of R_o :

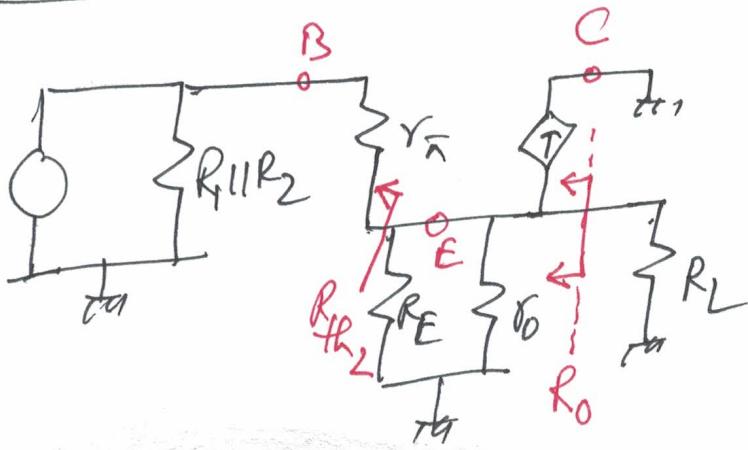



$$R_{Th2} = r_\pi = 3.156 \text{ k}\Omega$$

$$\begin{aligned} \therefore R_o &= \boxed{R_{Th2} \parallel R_E \parallel r_o} \\ &= 1.2146 \text{ k}\Omega \end{aligned}$$

(16)

Problem 6 :

Given : $\beta = 125$; $V_A = \infty$

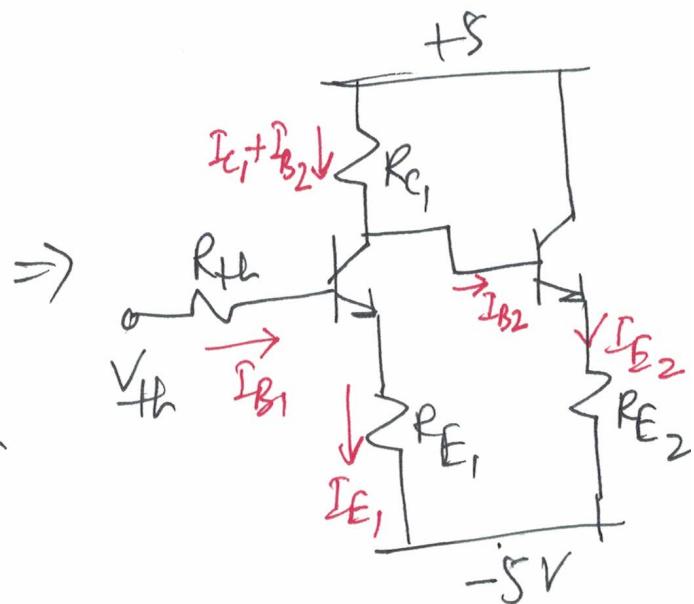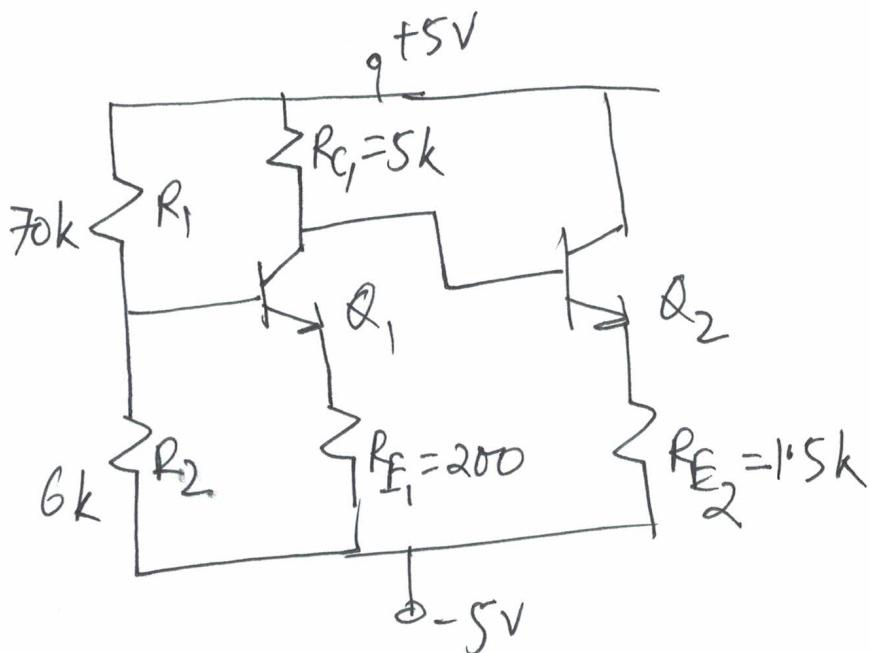

$$V_{th} = \left[\frac{R_2}{R_1 + R_2} \{ 5 - (-5) \} \right] - 5 = \frac{R_2 \cdot 10}{R_1 + R_2} - 5 = -4.21 V$$

$$R_{th} = R_1 \parallel R_2 = 5.526 k\Omega$$

$$\therefore V_{th} - (-5) = V_{BE2} + I_{E1} R_{E1} + I_{B1} R_{th}$$

$$\Rightarrow 0.7895 - 0.7 = I_{E1} \left(R_{E1} + \frac{R_{th}}{\beta + 1} \right)$$

$$\Rightarrow I_{E1} = 0.367 \text{ mA}$$

$$I_C = \alpha I_{E1} = 0.364 \text{ mA}$$

(17)

$$\therefore (I_{C_1} + I_{B2}) R_{C_1} + V_{BE} + I_{E2} R_{E2} = 10$$

$$\Rightarrow I_{C_1} R_{C_1} + I_{B2} R_{C_1} + V_{BE} + I_{B2} (\beta+1) R_{E2} = 10$$

$$\Rightarrow I_{B2} = \frac{10 - I_{C_1} R_{C_1} - V_{BE}}{(\beta+1) R_{E2} + R_{C_1}}$$

$$= 38.55 \text{ mA}$$

$$\therefore I_{C_2} = \frac{4.82 \text{ mA}}{4.82 \text{ mA}} ; I_{E2} = \frac{4.86 \text{ mA}}{4.8573 \text{ mA}}$$

$$\text{Now, } 10 = V_{CE2} + I_{E2} R_{E2} \Rightarrow V_{CE2} = 10 - I_{E2} R_{E2} \\ = 2.71 \text{ V} \\ 2.71 \text{ V}$$

$$\text{Again, } 10 = (I_{C_1} + I_{B2}) R_{C_1} + V_{CE1} + I_{E1} R_{E1}$$

$$\Rightarrow V_{CE1} = 10 - (I_{C_1} + I_{B2}) R_{C_1} - I_{E1} R_{E1} \\ = 7.91 \text{ V}$$

$$\therefore \boxed{\text{8 points: } I_{C_1} = 0.3641 \text{ mA}, V_{CE1} = 7.91 \text{ V}}$$


$$\frac{I_{C_2}}{4.82 \text{ mA}} = \frac{4.82 \text{ mA}}{4.82 \text{ mA}}$$

$$V_{CE2} = 2.71 \text{ V}$$

$$2.71 \text{ V}$$

small signal analysis

(18)

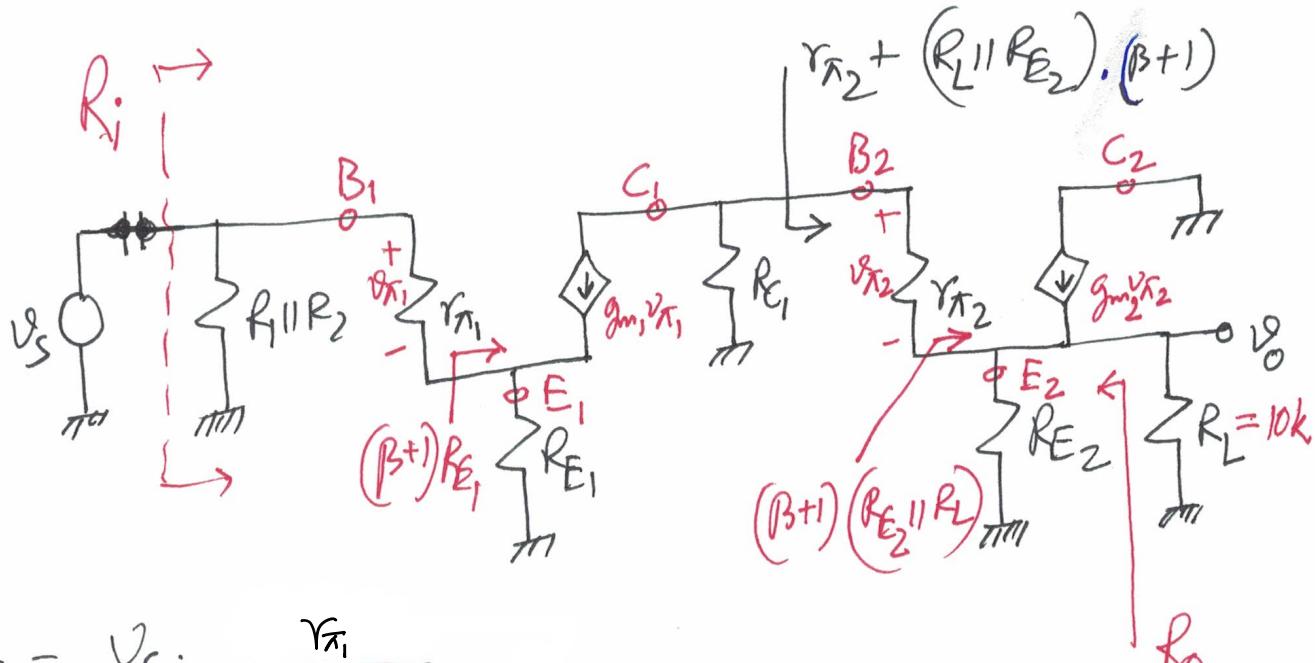

$$I_{\pi_1} = V_S \cdot \frac{r_{\pi_1}}{(\beta+1)R_{E1} + r_{\pi_1}}$$

$$V_{C_1} = g_{m1}v_{\pi_1} \cdot \left\{ R_{C_1} \parallel \left[r_{\pi_2} + (R_L \parallel R_{E2}) \cdot (\beta+1) \right] \right\}$$

$$= g_{m1}v_{\pi_1} \cdot R_{th_1}$$

$$V_O = V_{C_1} \cdot \frac{(\beta+1)(R_{E2} \parallel R_L)}{r_{\pi_2} + (\beta+1)(R_{E2} \parallel R_L)}$$

$$\text{Red note: } R_{th_2} = R_C \parallel [r_{\pi_2} + (R_L \parallel R_{E2}) \cdot (\beta+1)]$$

$$= g_{m1}v_{\pi_1} \cdot R_{th_1} \cdot \frac{(\beta+1)(R_{E2} \parallel R_L)}{r_{\pi_2} + (\beta+1)(R_{E2} \parallel R_L)}$$

$$= V_S \cdot \frac{r_{\pi_1}}{(\beta+1)R_{E1} + r_{\pi_1}} \cdot g_{m1}R_{th_1} \cdot \frac{(\beta+1)(R_{E2} \parallel R_L)}{r_{\pi_2} + (\beta+1)(R_{E2} \parallel R_L)}$$

$$\Rightarrow \frac{V_o}{V_s} = g_{m1} R_{th1} \cdot \frac{r_{\pi_1}}{(B+1)R_E + r_{\pi_1}} \cdot \frac{(B+1)(R_E || R_L)}{r_{\pi_2} + (B+1)(R_E || R_L)}$$

Now,

$$g_{m1} = \frac{I_{C1}}{V_T} = 14.6 \text{ mA/V}$$

$$r_{\pi_1} = \frac{V_T}{I_{D1}} = \frac{V_T}{I_{C1}/B} = 8.583 \text{ k}\Omega$$

$$r_{\pi_2} = \frac{V_T}{I_{B2}} = \frac{V_T}{I_{C2}/B} = 0.648 \text{ k}\Omega$$

$$\therefore R_{th1} = R_C || [r_{\pi_2} + (R_L || R_E) \cdot (B+1)]$$

$$= R_C || 165 \text{ k}$$

$$= 4.853 \text{ k}$$

$$\therefore A_{vo} = \frac{V_o}{V_s} = g_{m1} R_{th1} \cdot \frac{r_{\pi_1}}{(B+1)R_E + r_{\pi_1}} \cdot \frac{(B+1)(R_E || R_L)}{r_{\pi_2} + (B+1)(R_E || R_L)}$$

↓ ↓

$$0.2541 \quad 0.9961$$

$$= 17.934$$

Input Resistance:

$$R_i = R_1 \parallel R_2 \parallel \left(r_{\pi 1} + (\beta + 1) R_{E1} \right)$$

$$= 5.526k \parallel 33.783k$$

$$= 4.7492k\Omega$$

Output Resistance:

$$R_o = R_{E2} \parallel \left(r_{\pi 2} + R_{C1} \right) / (\beta + 1)$$


$$= R_{E2} \parallel 44.54$$

$$= 43.256\Omega$$



Problem 7

(21)

Equivalent AC circuit:

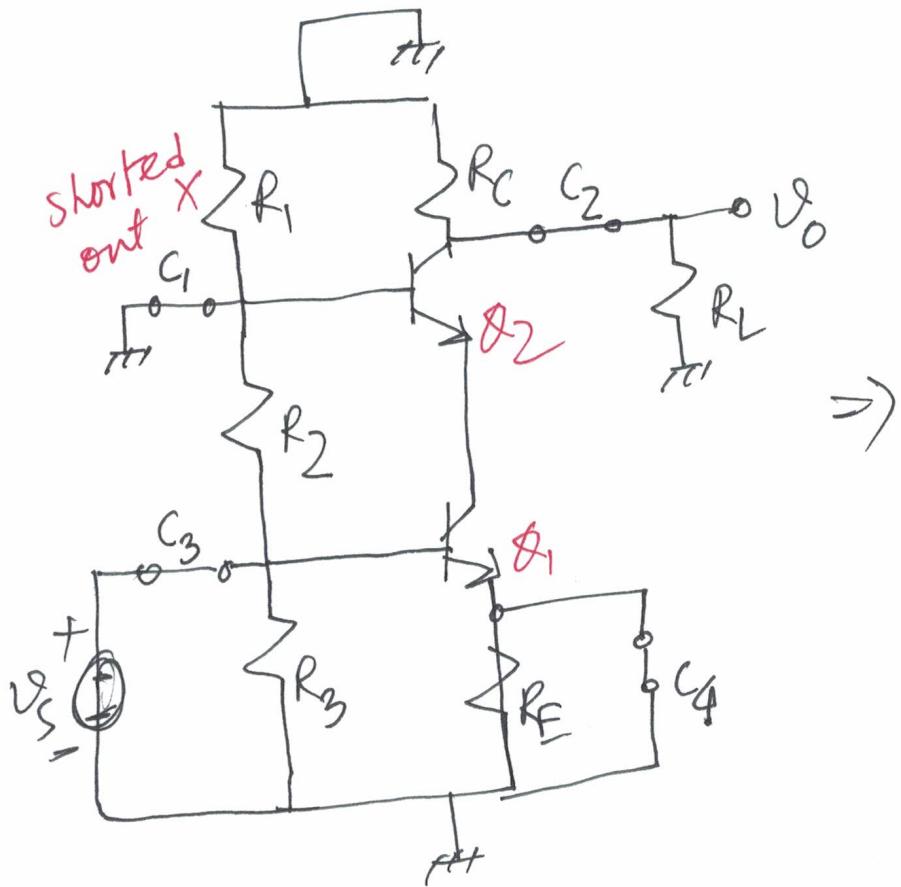



\Rightarrow

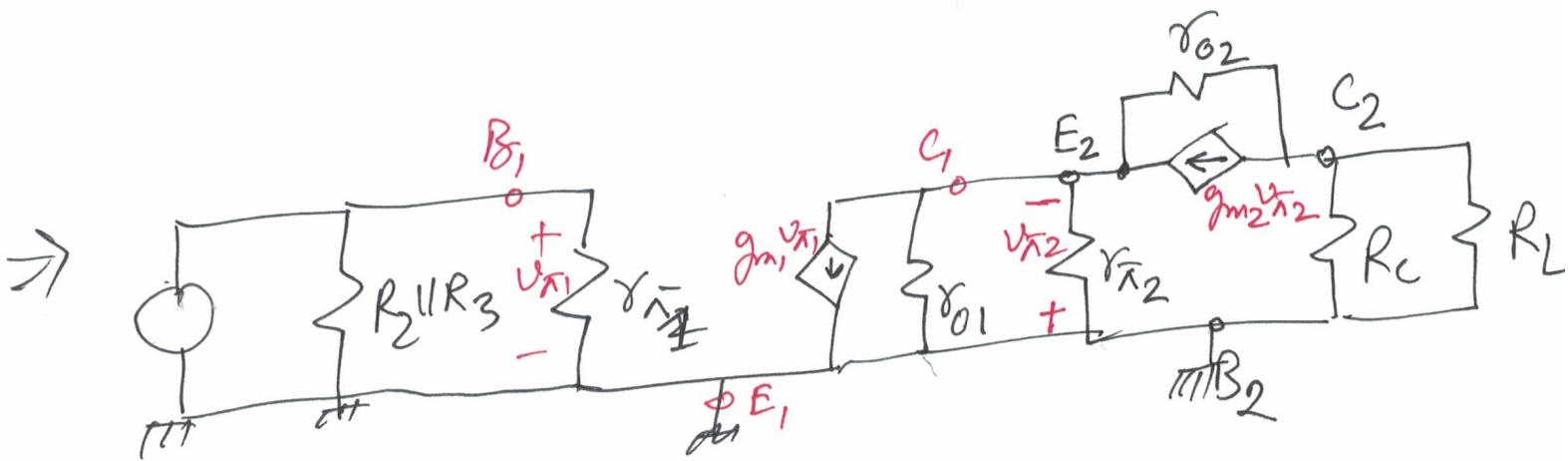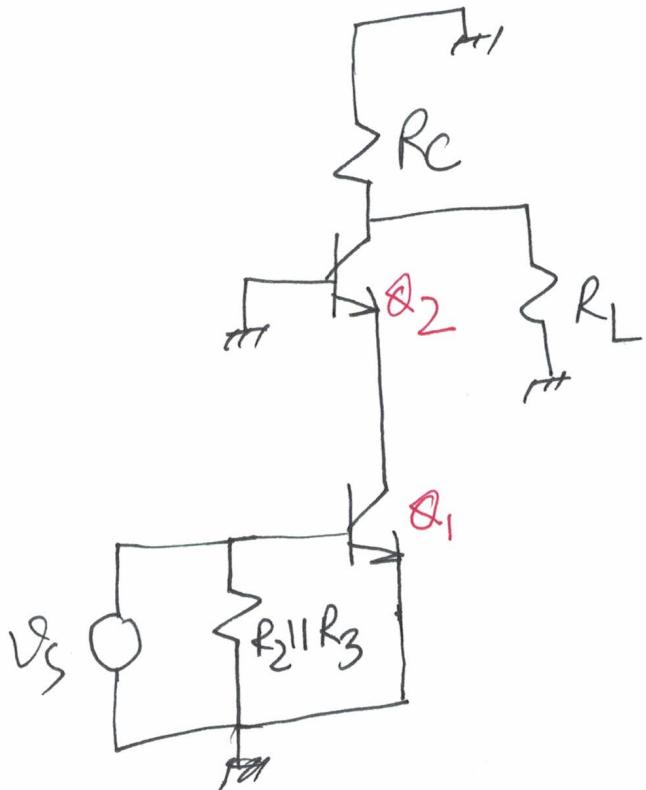

Problem 8:

(22)

AC Equivalent Circuit:

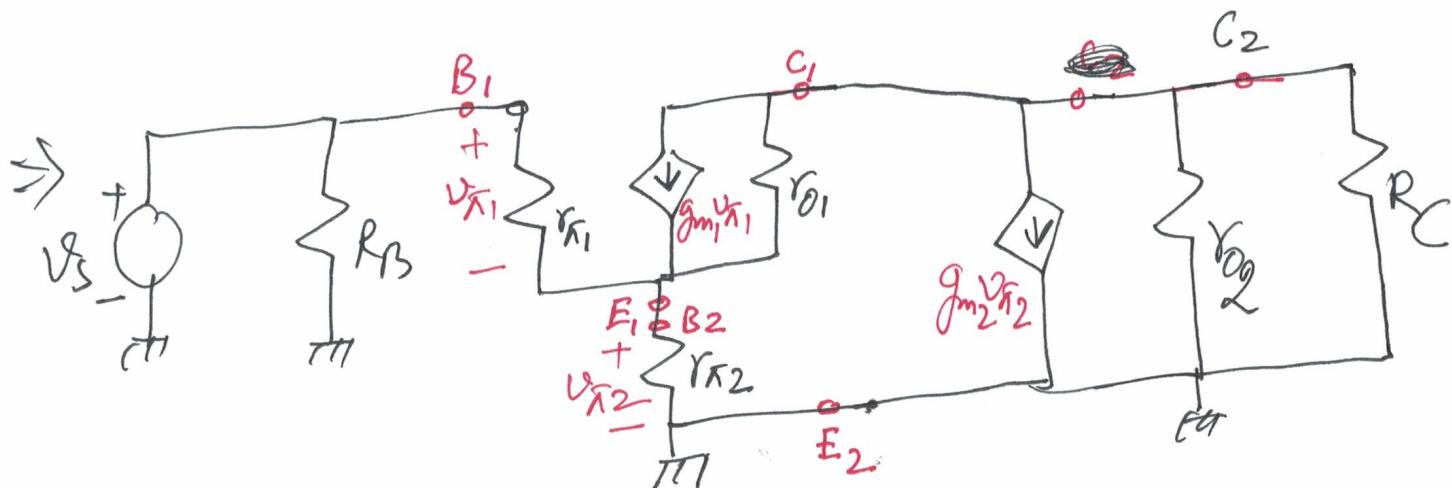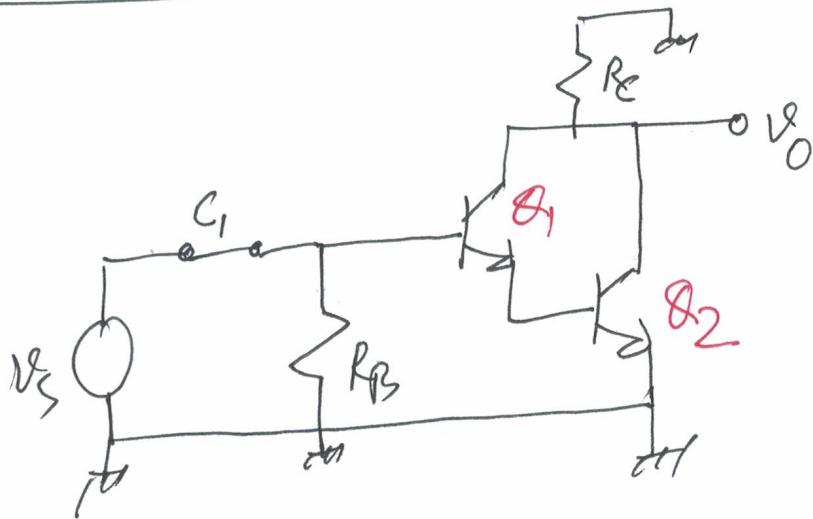

For any question, contact: sager.shar@ucalgary.ca