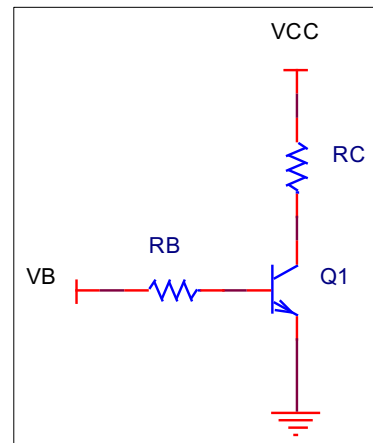


Practice Problem Set #2
Biasing Basic-2
ENEL469: Analog Electronics

Consider the following circuits where $\beta = 100$, $|V_{BE(ON)}| = 0.7\text{V}$. Assume $|V_{CE}| = 0.3\text{V}$ if the collector base junction is forward biased. **For all the following circuits (A-N)**, determine I_B , I_C , V_{CE} , V_{CB} and the type of biasing applied to the BE and CB junctions. If needed use the following transistor equations, $I_C = \beta I_B$, and $I_E = I_C + I_B$.


A) Use the following given values

$$V_{CC} = 10\text{ V}, V_B = 4\text{ V}, \\ R_B = 66\text{ k}\Omega, \text{ and } R_C = 1\text{ k}\Omega.$$



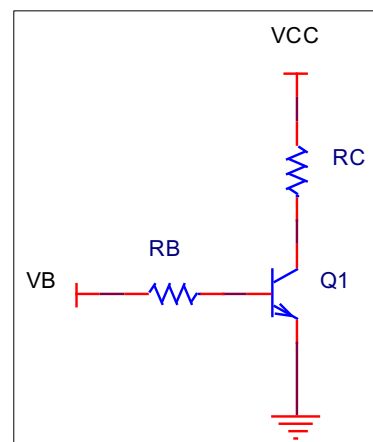
B) Use the following given values

$$V_{CC} = -10\text{ V}, V_B = 4\text{ V}, \\ R_B = 66\text{ k}\Omega, \text{ and } R_C = 1\text{ k}\Omega.$$



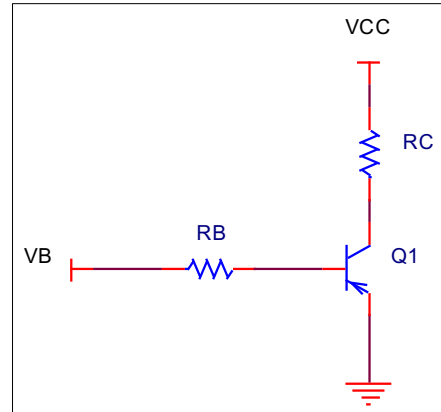
C) Use the following given values

$V_{CC} = 10\text{ V}$, $V_B = -4\text{ V}$,
 $R_B = 66\text{ k}\Omega$, and $R_C = 1\text{ k}\Omega$.



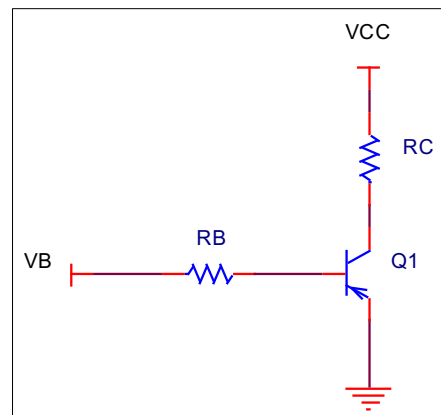
D) Use the following given values

$V_{CC} = 10\text{ V}$, $V_B = 4\text{ V}$,
 $R_B = 66\text{ k}\Omega$, and $R_C = 1\text{ k}\Omega$.



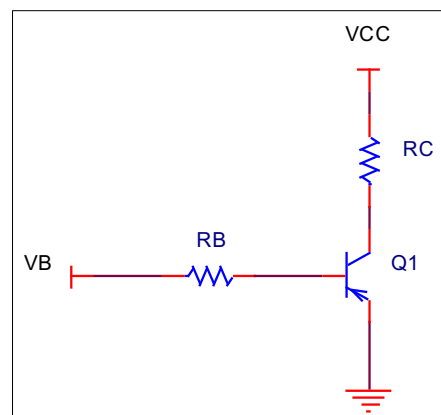
E) Use the following given values

$V_{CC} = -10\text{ V}$, $V_B = -4\text{ V}$,
 $R_B = 66\text{ k}\Omega$, and $R_C = 1\text{ k}\Omega$.



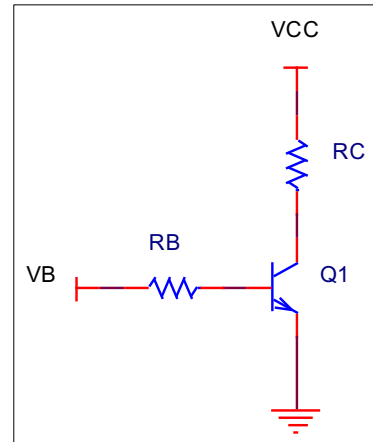
F) Use the following given values

$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 0, \text{ and } R_C = 1 \text{ k}\Omega.$$



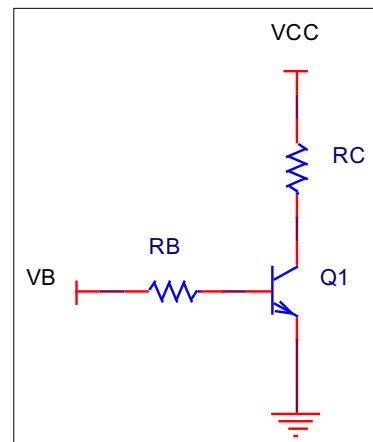
G) Use the following given values

$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 66 \text{ k}\Omega, \text{ and } R_C = 0.$$



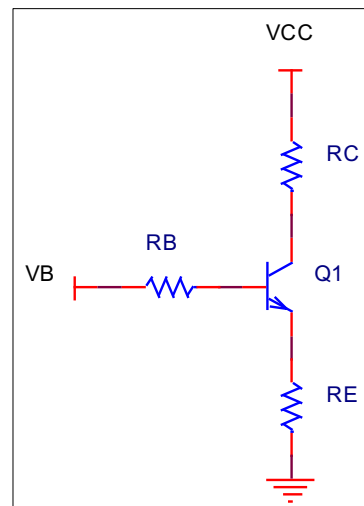
H) Use the following given values

$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 0, R_C = 1 \text{ k}\Omega, \text{ and } R_E = 1 \text{ k}\Omega.$$



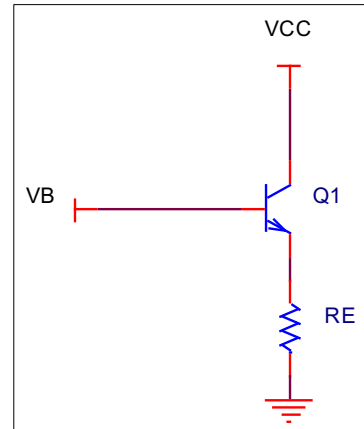
I) Use the following given values

$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V and } R_E = 1 \text{ k}\Omega.$$




J) Use the following given values
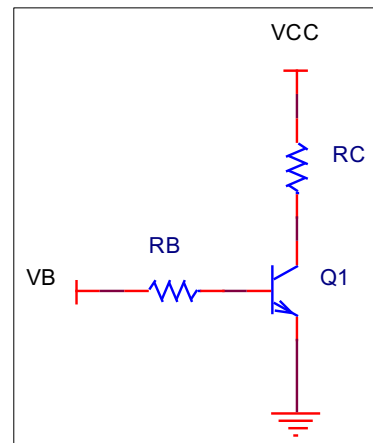
$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 11 \text{ k}\Omega \text{ and } R_C = 1 \text{ k}\Omega.$$




K) Use the following given values
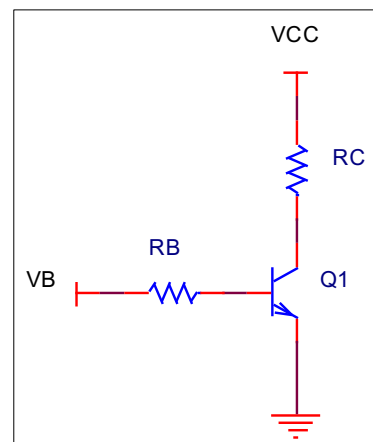
$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 66 \text{ k}\Omega \text{ and } R_C = 5 \text{ k}\Omega.$$




L) Use the following given values
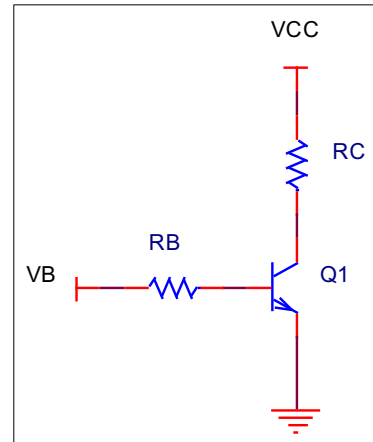
$$V_{CC} = 10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 11 \text{ k}\Omega \text{ and } R_C = 200 \text{ }\Omega.$$



M) Use the following given values
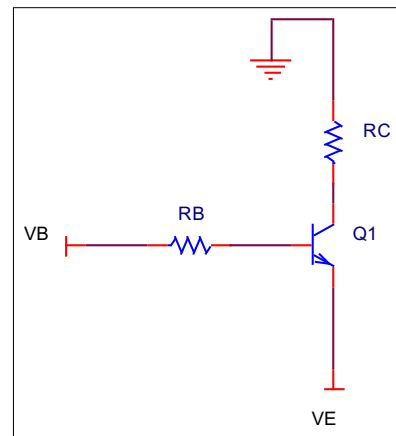
$$V_E = -10 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 66 \text{ k}\Omega \text{ and } R_C = 1 \text{ k}\Omega.$$



N) Use the following given values

$$V_{CC} = 5 \text{ V}, V_E = -5 \text{ V}, V_B = 4 \text{ V}, \\ R_B = 66 \text{ k}\Omega \text{ and } R_C = 1 \text{ k}\Omega.$$

