
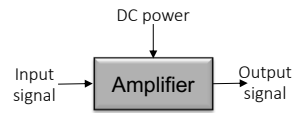


## An Amplifier

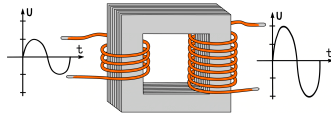

- voltage gain,  $A_v = \frac{\text{output voltage}}{\text{input voltage}} = \frac{v_o}{v_{in}}$
- current gain,  $A_i = \frac{\text{output current}}{\text{input current}} = \frac{i_o}{i_{in}}$
- Power gain,  $A_p = A_v \times A_i$
- Additional power is supplied by the DC source; conservation of energy

since  
 $P = VT$




- A step-up transformer is **not** a voltage amplifier
- There is **no power gain**
- $V_p \times I_p = V_s \times I_s$

1

1

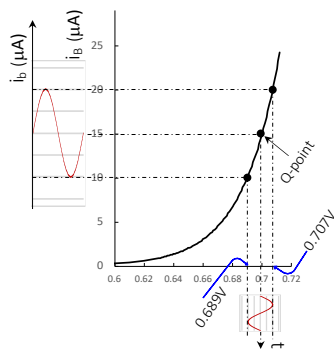
## Transistor as an Amplifier: Graphical Illustration



$$A_i = \frac{(4 - 2) \times 10^{-3}}{(20 - 10) \times 10^{-6}} = 200 = \beta$$

$$A_v = \frac{(2 - 6)}{(0.707 - 0.689)} = -222$$

$$A_p = |A_v| \times |A_i| = 44,400$$

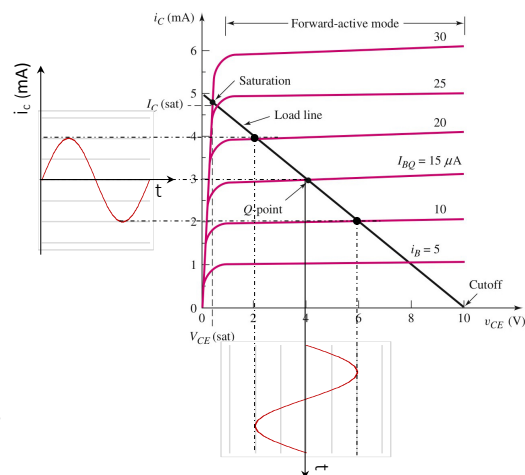


- A CE amplifier provides enormous power gain
- The negative voltage gain indicates **180° phase difference** between input and output voltages

2

2

## Coupling Capacitors

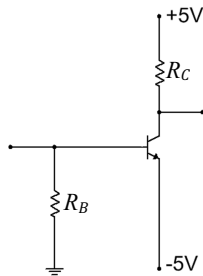

- You wanted to design an audio amplifier, where the operating point had to be almost at the middle of the load-line
- You obtained  $R_C = 2 \text{ k}\Omega$  and  $R_B = 200 \text{ k}\Omega$ , where it was given that  $\beta = 100$

Without any signal and load being connected to this amplifier, the operating point was set to

$$I_C = \beta I_B$$

$$I_C = 2.15 \text{ mA}$$

$$I_B = \frac{(5 - 0.7)}{200 \times 10^3}$$

$$I_B = 21.5 \text{ }\mu\text{A}$$

$$V_{CE} = 5 - (-5) + I_C R_C$$


$$V_{CE} = 5.7 \text{ V}$$

Perfect design-great job!


3

3

## Coupling Capacitors (Continued ...)

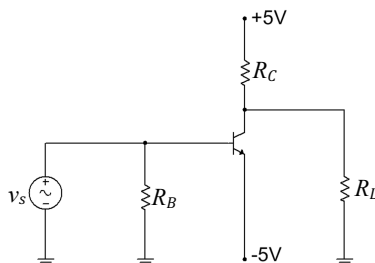

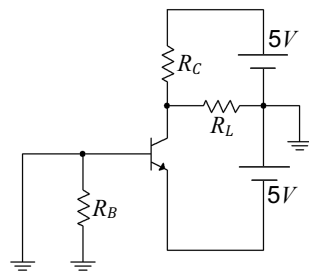- Now connect a very low-impedance (assume zero) microphone to the amplifier input with  $v_s$  input voltage
- Also, connect an  $8 \text{ }\Omega$  speaker at the output (assume  $R_L \approx 0$ )
- The DC equivalent circuit will become as shown in the left-bottom corner



With the mic and speaker connected, the Q-point will change to

$$V_{BE} = 0 \quad I_B = 0 \quad I_C = 0$$

$$V_C = 5 \times \frac{R_L}{R_C + R_L} = 0.02 \text{ V} \quad V_C \approx 0$$

The biasing is completely lost, and the Q-point is set to cut-off!


4

4

voltage  
division

### Coupling Capacitors (Continued ...)

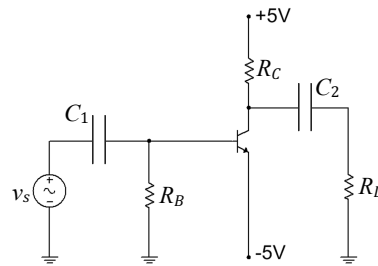**Question:** How to apply input signal and connect a load without changing transistor biasing or Q-point?



**Eureka!!** We have capacitors, which is an **open circuit for DC**, but for a suitable selection it becomes a **short circuit for the signal**.

Recall that  $Z_C = \frac{1}{2\pi fC}$

↑  
impedance



The coupling capacitors:

- keep the DC biasing unchanged
- create an almost shorted path for the AC signal

5

5
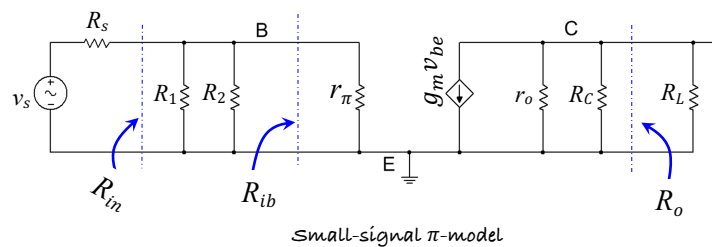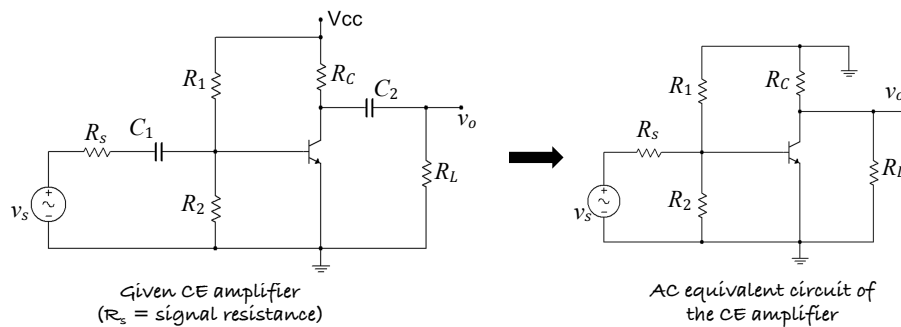
### Small-Signal Analysis of a CE Amplifier




Small-signal  $\pi$ -model

6

6
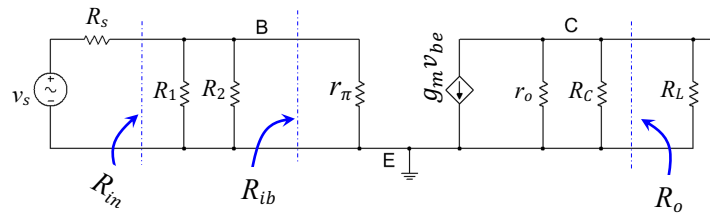
### Small-Signal Analysis of a CE Amplifier: Input Resistance



Input resistance at the base,  $R_{ib}$ , is

$$R_{ib} = r_{\pi}$$

Input resistance seen by the source,  $R_{in}$ , is

$$R_{in} = R_1 || R_2 || R_{ib}$$

or,  $R_{in} = R_B || R_{ib}$

where,  $R_B = R_1 || R_2$


Note

- $R_{in} < r_{\pi}$
- If  $R_B \gg r_{\pi}$ ,  $R_{in} \approx r_{\pi}$
- The input resistance of a CE amplifier without emitter resistor ( $R_E$ ) is low

7

7
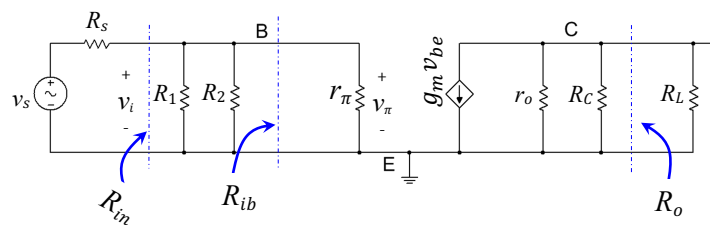
### Small-Signal Analysis of a CE Amplifier: Input Voltage




Input voltage at the base is

$$v_i = v_{\pi} = v_{be} = v_{in} \neq v_s$$

$$v_i = v_s \frac{R_{in}}{R_{in} + R_s}$$

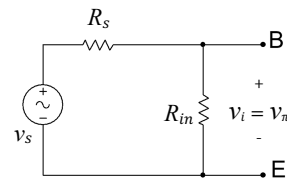or,  $v_i \approx v_s \frac{r_{\pi}}{r_{\pi} + R_s}$  [If  $R_B \gg r_{\pi}$ ]




What would you expect in your design, higher  $R_s$  or lower  $R_s$ ?

8

8
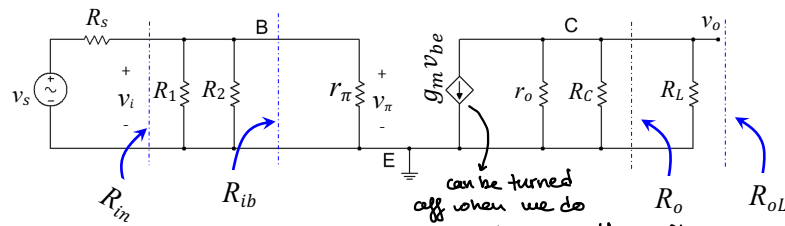
### Small-Signal Analysis of a CE Amplifier: Output Resistance



can be turned off when we do A.C. analysis, even though it is a dependent source, because we know it's internal Resistance

Output resistance  $R_o$  is

$$R_o = R_C || r_o$$

Output resistance  $R_{oL}$  is

$$R_{oL} = R_o || R_L$$

Thus,  $R_{oL} < R_o$

Typically,  $r_o \gg R_C$ , which gives


$$R_o \approx R_C$$



9

9
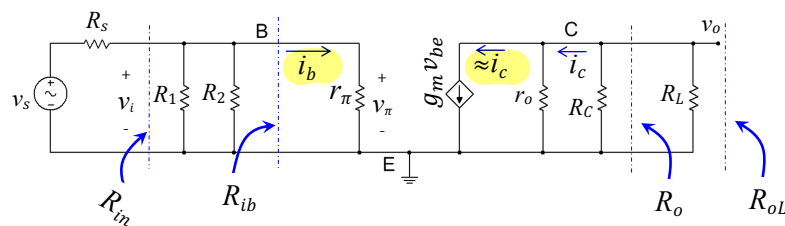
### Small-Signal Analysis of a CE Amplifier: Current Gain



Current gain  $A_i$  is

$$A_i = \frac{i_c}{i_b} \approx \frac{g_m v_{be}}{\left(\frac{v_{be}}{r_{\pi}}\right)}$$

or,  $A_i = g_m r_{\pi}$  [Since  $v_{be} = v_{\pi}$ ]

$$\text{But } r_{\pi} = \frac{V_T}{I_B} = \frac{V_T \beta}{I_C} = \frac{\beta}{g_m}$$

$$\text{or, } r_{\pi} g_m = \beta$$

Thus, we can write,


$$A_i = \beta$$

Therefore  $\beta$  is called **common-emitter current gain**, this is an **inherent parameter**.

10

10
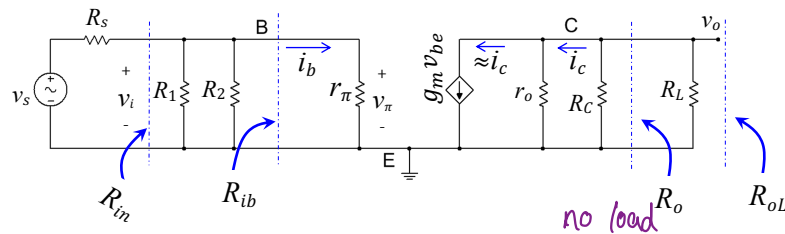
### Small-Signal Analysis of a CE Amplifier: Voltage Gain



voltage gain  $A_v$  is

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_{\pi}}$$

*why?*

$$\text{or, } A_v = \frac{-(g_m v_{\pi})(r_o || R_C || R_L)}{v_{\pi}}$$

$$\text{or, } A_v = -g_m (r_o || R_C || R_L) = -g_m R_{oL}$$

The negative sign indicates  
**180° phase difference** in CE amp

The open circuit voltage gain is

$$A_{vo} = -g_m (r_o || R_C) = -g_m R_o$$

- If  $r_o \gg R_C$


$$A_{vo} \approx -g_m R_C$$

- Lower value of  $v_A$  ( $r_o$ )  
reduces the voltage gain

11

11
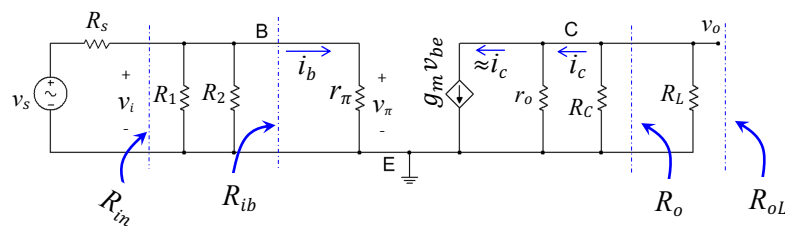
### Small-Signal Analysis of a CE Amplifier: Voltage Gain (continued ...)



The voltage gain with load  $R_L$  is

$$\text{or, } A_v = -g_m (r_o || R_C || R_L)$$

$$\text{or, } A_v = -g_m (R_C || R_L)$$

$$\text{or, } A_v = -g_m R_o \frac{R_L}{R_o + R_L}$$


$$\text{or, } A_v = A_{vo} \frac{R_L}{R_o + R_L}$$

A load can significantly  
reduce the voltage gain

12

12

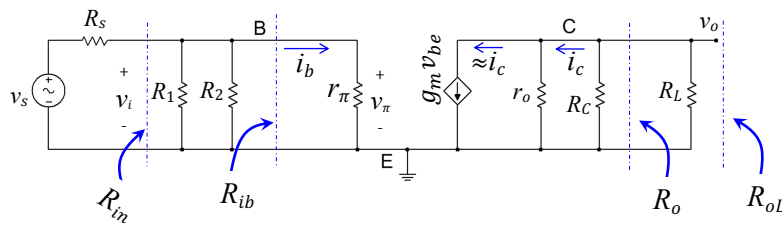
### Small-Signal Analysis of a CE Amplifier: Effect of Source Resistance



We have just obtained voltage gain using the definition

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_\pi}$$

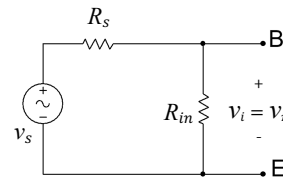Notice that the actual input signal is  $v_s$ , where  $v_i$  is the signal that appears at the base.



$$\text{and, } v_i = v_s \frac{R_{in}}{R_{in} + R_s}$$

Thus, the overall voltage gain is further dropped by source resistance


13

13

### Small-Signal Analysis: CE Amplifier Example

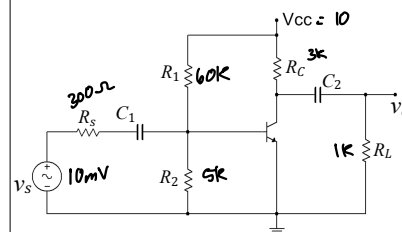**Example:** In the given circuit,  $V_{CC} = 10$  V,  $R_1 = 60$  k $\Omega$ ,  $R_2 = 5$  k $\Omega$ ,  $R_C = 3$  k $\Omega$ ,  $R_L = 1$  k $\Omega$ ,  $R_s = 300$   $\Omega$ ,  $v_s = 10$  mV,  $\beta = 100$ , and  $V_A = 80$  V. Determine:

- Small-signal parameters
- Signal voltage at the base
- voltage gain without load
- voltage gain with load
- Output voltage



**Soln:**

In order to determine the small-signal parameters, DC analysis is required

DC analysis

$$I_{R2} = V_{BE(ON)} / R_2$$

$$I_{R2} = 0.7 / 5 \times 10^3$$

$$I_{R2} = 140 \mu A$$

$$I_{R1} = [V_{CC} - V_{BE(ON)}] / R_1$$

$$I_{R1} = (10 - 0.7) / 60 \times 10^3$$

$$I_{R1} = 155 \mu A$$

$$I_B = I_{R1} - I_{R2}$$

$$I_B = 15 \mu A$$

$$I_C = \beta \times I_B = 1.50 \text{ mA}$$


$$I_E = (\beta + 1) I_B = 1.52 \text{ mA}$$

14

14
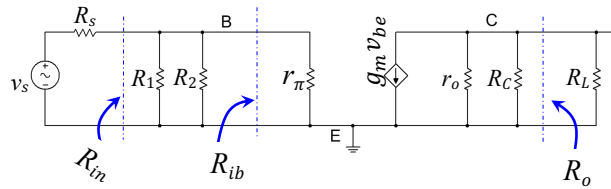
### Small-Signal Analysis: CE Amplifier Example (Continued ...)

**Given:**  $V_{CC} = 10\text{ V}$ ,  
 $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $R_S = 300\text{ }\Omega$ ,  $V_s = 10\text{ mV}$ ,  $\beta = 100$ ,  
 and  $V_A = 80\text{ V}$



#### Solution to part (a): small-signal parameters

$$r_{\pi} = V_T / I_B$$

$$r_{\pi} = 25 \times 10^{-3} / 15 \times 10^{-6}$$

$$r_{\pi} = 1.67\text{ k}\Omega$$

$$r_o = V_A / I_C$$

$$r_o = 80 / 1.5 \times 10^{-3}$$

$$r_o = 53.3\text{ k}\Omega$$

$$g_m = I_C / V_T$$

$$g_m = 1.5 \times 10^{-3} / 25 \times 10^{-3}$$

$$g_m = 60\text{ mA/V}$$

$$r_e = V_T / I_E$$

$$r_e = 25 \times 10^{-3} / 1.52 \times 10^{-3}$$


$$r_e = 16.45\text{ }\Omega$$

15

15
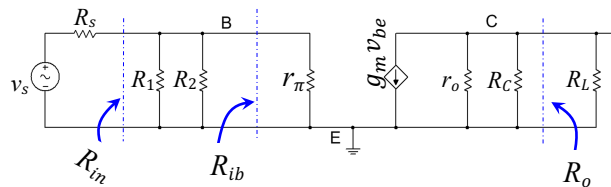
### Small-Signal Analysis: CE Amplifier Example (Continued ...)

**Given:**  $V_{CC} = 10\text{ V}$ ,  
 $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $R_S = 300\text{ }\Omega$ ,  $V_s = 10\text{ mV}$ ,  $\beta = 100$ ,  
 and  $V_A = 80\text{ V}$



#### Solution to part (b): signal voltage at the base

$$v_{\pi} = v_{be} = v_{ib} = v_s \frac{R_{in}}{R_{in} + R_s}$$

$$\text{or, } v_{ib} = 10 \times 10^{-3} \times \frac{(60 // 5 // 1.67) \times 10^3}{300 + (60 // 5 // 1.67) \times 10^3}$$

$$\text{or, } v_{ib} = 10 \times 10^{-3} \times \frac{1226}{300 + 1226}$$

$$\text{or, } v_{ib} = 10 \times 10^{-3} \times 0.803 = 8.03\text{ mV}$$

Notice that only 80.3% of the input signal appears at the base. This is only because of  $R_s$ .


16

16


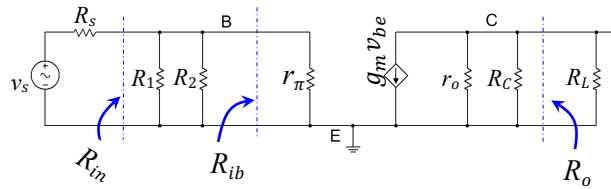
### Small-Signal Analysis: CE Amplifier Example (Continued ...)

**Given:**  $V_{CC} = 10\text{ V}$ ,  
 $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $R_S = 300\text{ }\Omega$ ,  $V_s = 10\text{ mV}$ ,  $\beta = 100$ ,  
 and  $V_A = 80\text{ V}$



**Solution to part (c): no-load voltage gain**

$$A_{vo} = -g_m(r_o // R_C)$$

$$\text{or, } A_{vo} = -60 \times 10^{-3} \times \frac{53.3 \times 3 \times 10^6}{(53.3 + 3) \times 10^3}$$

$$\text{or, } A_{vo} = 60 \times 10^{-3} \times 0.947 \times 3 \times 10^3$$

$$\text{or, } A_{vo} = -170.5 \quad \text{or, } |A_{vo}| = 170.5$$


- Had we ignored  $r_o$  ( $r_o = \infty$ ), the voltage gain would have been **180**.
- The no load gain has **dropped by a factor 0.947** because of considering  $r_o$ .
- Had we had  $R_C = 1\text{ k}\Omega$ , the voltage gain would have been three times lower, i.e.,  **$|A_{vo}| = 56.8$**

17

17
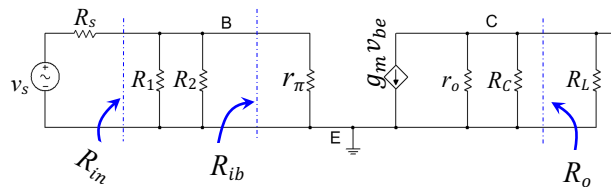
### Small-Signal Analysis: CE Amplifier Example (Continued ...)

**Given:**  $V_{CC} = 10\text{ V}$ ,  
 $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $R_S = 300\text{ }\Omega$ ,  $V_s = 10\text{ mV}$ ,  $\beta = 100$ ,  
 and  $V_A = 80\text{ V}$



**Solution to part (d): voltage gain with load**

$$A_v = -g_m(r_o // R_C // R_L)$$

$$\text{or, } A_v = -60 \times 10^{-3} \times (53.3 // 3 // 1) \times 10^3$$

$$\text{or, } A_v = 60 \times 10^{-3} \times 739.6$$

$$\text{or, } A_v = -44.4 \quad \text{or, } |A_v| = 44.4$$


- Had we ignored  $r_o$  ( $r_o = \infty$ ), the voltage gain would have been **45**.
- That would have been only **1.4% error**.
- Had we had  $R_C = 1\text{ k}\Omega$ , the voltage gain would have been  **$|A_v| = 29.7$**  instead of 44.4.

18

18
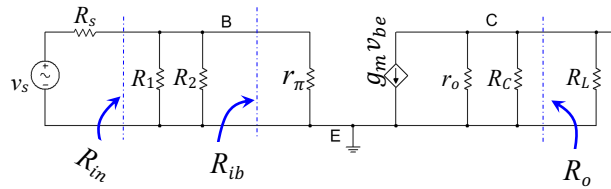
### Small-Signal Analysis: CE Amplifier Example (Continued ...)

**Given:**  $V_{CC} = 10\text{ V}$ ,  
 $R_1 = 60\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_C = 3\text{ k}\Omega$ ,  $R_L = 1\text{ k}\Omega$ ,  $R_S = 300\text{ }\Omega$ ,  $v_s = 10\text{ mV}$ ,  $\beta = 100$ ,  
 and  $V_A = 80\text{ V}$



#### Solution to part (e): Output voltage

The output voltage without load is

$$v_o = A_{vo} \times v_{ib}$$

$$\text{or, } v_o = -170.5 \times 8.03 \times 10^{-3}$$

$$\text{or, } v_o = -1.37\text{ V}$$

$$\text{or, } |v_o| = 1.37\text{ V}$$

The output voltage with load is

$$v_o = A_v \times v_{ib}$$

$$\text{or, } v_{oL} = -44.4 \times 8.03 \times 10^{-3}$$


$$\text{or, } v_o = -356.5\text{ mV}$$

$$\text{or, } |v_o| = 0.357\text{ V}$$

19

19
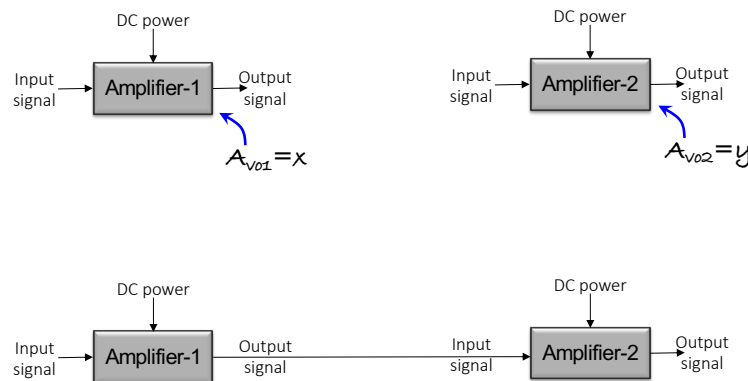
### Small-Signal Analysis of a CE Amplifier: Voltage Gain (continued ...)



$$A_{v,12} = \frac{v_{o2}}{v_{i1}} = \frac{v_{o2}}{v_{o1}} \times \frac{v_{o1}}{v_{i1}} = A_{vo1} \times A_{vo2} = xy$$


Is this valid?

20

20

Quiz 2, ends here

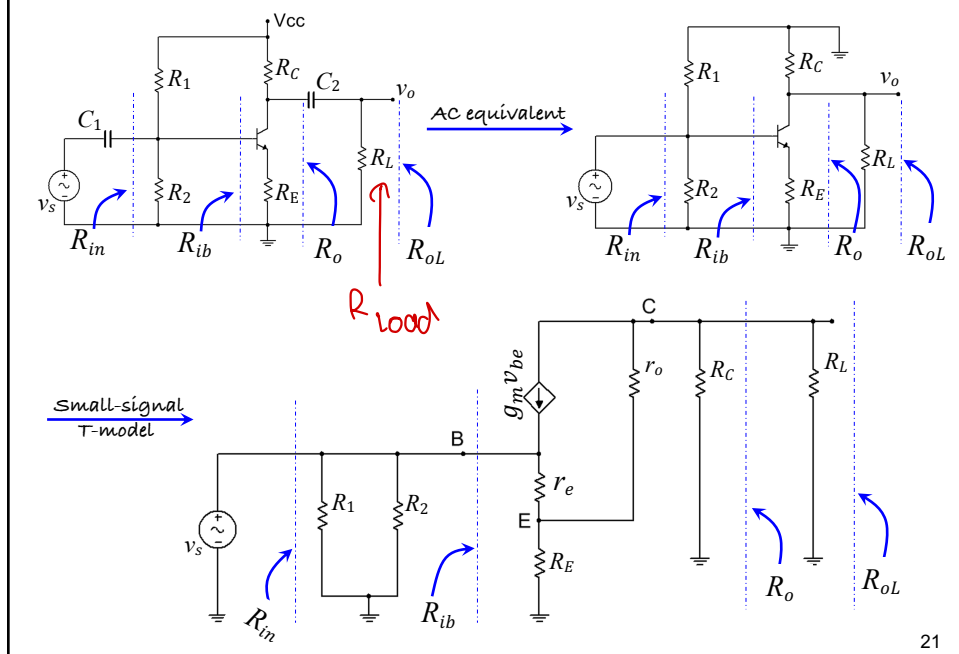
### Small-Signal Analysis of a CE Amplifier With Emitter Resistor $R_E$



21

21
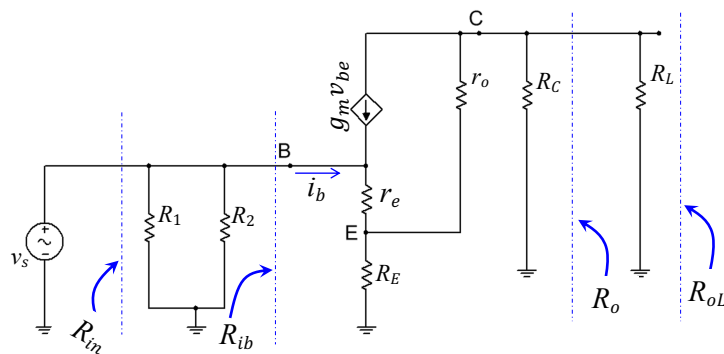
### CE Amplifier With Emitter Resistor $R_E$ : Input Resistance



Input resistance at the base is

$$R_{ib} = \frac{v_b}{i_b}$$

$$\text{or, } R_{ib} = \frac{(\beta + 1)v_b}{i_e}$$

[Since  $i_e = (\beta + 1)i_b$ ]

Typically  $r_o \gg (r_e \text{ and } R_E)$

Setting  $r_o = \infty$  we have,


$$R_{ib} = (\beta + 1)(r_e + R_E)$$

Notice how the factor  $(\beta + 1)$  is introduced in the input resistance. We'll use it frequently.

22

22
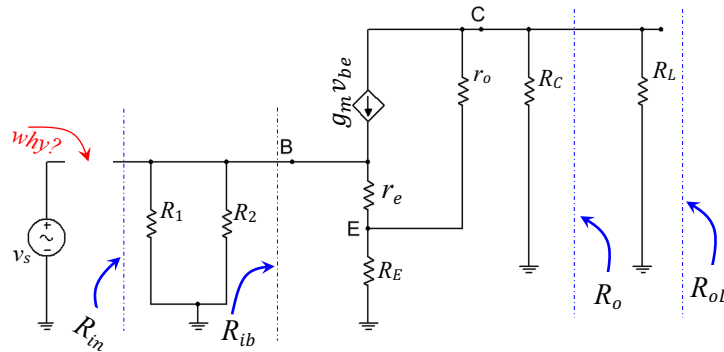
### CE Amplifier With Emitter Resistor $R_E$ : Output Resistance



Output resistance  $R_o$  is

$$R_o = R_C \parallel \left[ r_o + \left\{ R_E \parallel \left( r_e + \frac{R_1 \parallel R_2}{\beta + 1} \right) \right\} \right]$$

Where would  $R_s$  go in this equation if it was not ignored?

If  $r_o \gg (r_e \text{ and } R_E)$

Setting  $r_o = \infty$  we have,

$$R_o = R_C$$


and  $R_{oL} = R_o \parallel R_L$

23

23

we have this because we are not adding resistors that have same current passing through,  $R_1 \parallel R_2$  have  $i_b$  rest have  $i_e$  or derivations of  $i_e$
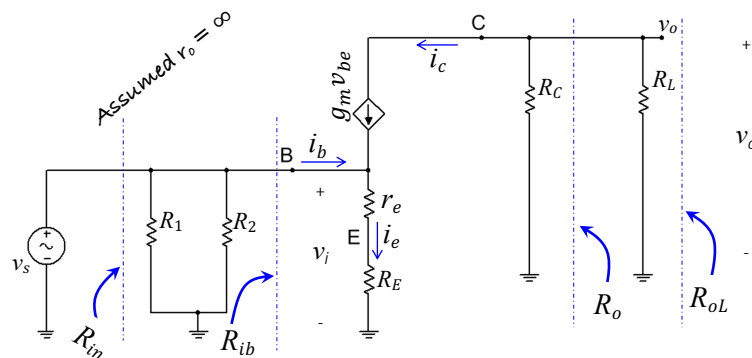
### CE Amplifier With Emitter Resistor $R_E$ : Voltage Gain



The voltage gain  $A_v$  is

$$A_v = \frac{v_o}{v_i} = \frac{-i_c(R_C \parallel R_L)}{i_e(r_e + R_E)}$$

$$\text{or, } A_v = \frac{-\alpha(R_C \parallel R_L)}{(r_e + R_E)} \dots \dots (1)$$

$$\text{or, } A_v = -\frac{\alpha}{r_e} \times \frac{(R_C \parallel R_L)}{\left(1 + \frac{1}{r_e} \times R_E\right)}$$


using  $g_m = \frac{\alpha}{r_e} \cong \frac{1}{r_e}$  we have,

$$A_v \cong -\frac{g_m(R_C \parallel R_L)}{(1 + g_m R_E)}$$

24

24
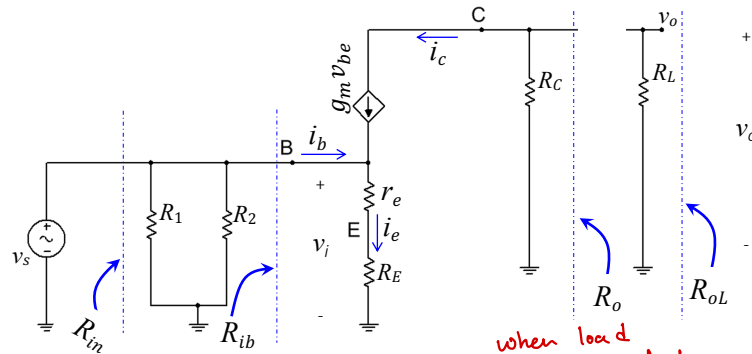
### CE Amplifier With Emitter Resistor $R_E$ : No-Load Voltage Gain



The no-load voltage gain  $A_{v_o}$  is

$$A_{v_o} \cong -\frac{g_m R_C}{(1 + g_m R_E)}$$

The voltage gain is **reduced** by a factor  $(1 + g_m R_E)$ .  
What if  $R_E = 0$ ?

when load is not connected  
For open circuit, eq (1) becomes

$$A_{v_o} \cong -\frac{R_C}{r_e + R_E}$$


or,  $A_{v_o} = \frac{\text{Total resistance in the collector}}{\text{Total resistance in the emitter}}$

used when modelling Resistors

25

25
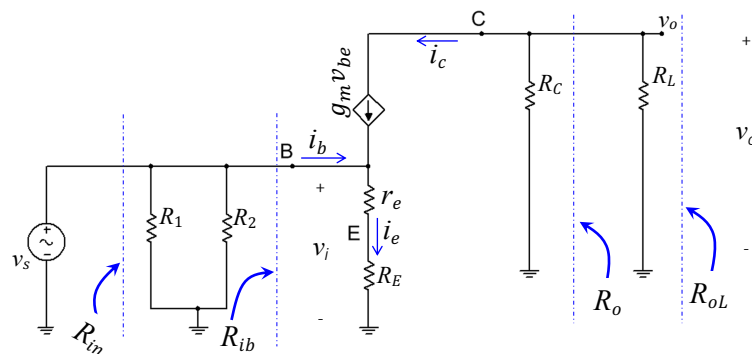
### CE Amplifier With Emitter Resistor $R_E$ : Current Gain



The current gain remains the same, i.e.

$$A_i = \beta$$


Regardless of whether  $R_E > 0$  or  $= 0$

26

26
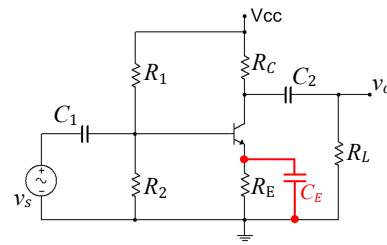
### CE Amplifier With Emitter Resistor $R_E$ : Bypass Capacitor

We have learned that the voltage gain of this circuit drops by a factor  $(1 + g_m R_E)$ . Why do we use the emitter resistor,  $R_E$ ?



$R_E$  provides thermal stability - **How?**

- If  $I_C$  increases because of temp
- $V_{RE}$  will increase
- Increase of  $V_{RE}$  will reduce  $V_{BE}$
- The reduced  $V_{BE}$  will lower  $I_B$
- The reduced  $I_B$  will lower  $I_C$
- This is called **negative feedback**

How can we take the advantage of this thermal stability without losing voltage gain?


Let the signal bypass  $R_E$  but make the DC biasing current flow through  $R_E$  by using a capacitor. This capacitor is called **emitter bypass capacitor**.

Now,  $A_v = -g_m(R_C || R_L)$

27

27

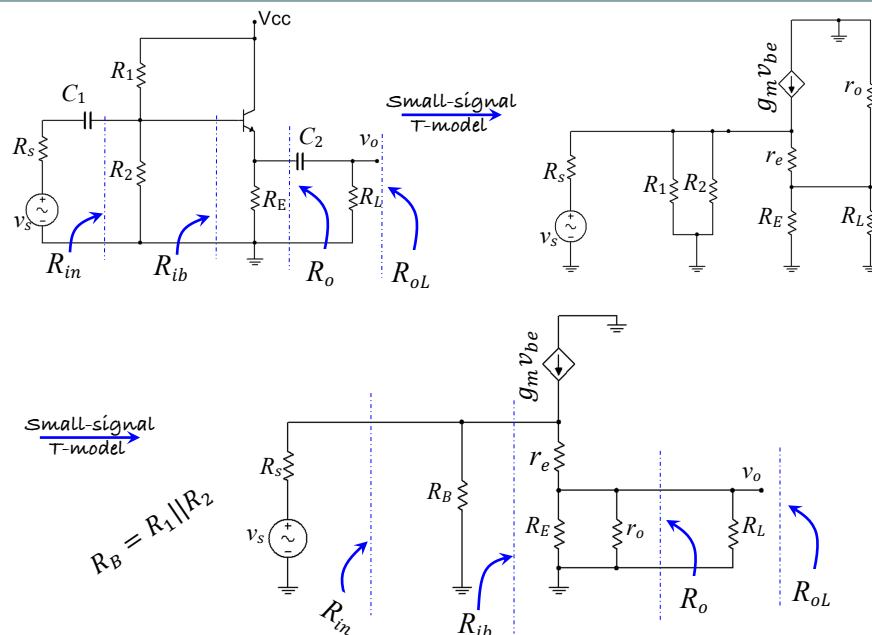
### Small-Signal Analysis of a CC Amplifier



28

28
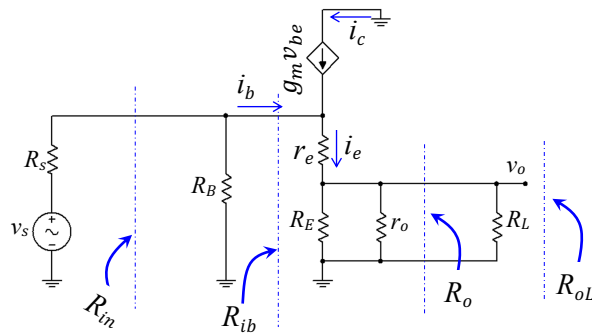
### Small-Signal Analysis of a CC Amplifier: Input Resistance



Input resistance at the base is

$$R_{ib} = \frac{v_b}{i_b}$$

$$\text{or, } R_{ib} = \frac{(\beta + 1)v_b}{i_e}$$

$$\text{Here, } \frac{v_b}{i_e} = r_e + (R_E || r_o || R_L)$$


$$\text{Thus, } R_{ib} = (\beta + 1)[r_e + (R_E || r_o || R_L)]$$

$$\text{Also, } R_{in} = R_B || R_{ib}$$

29

29

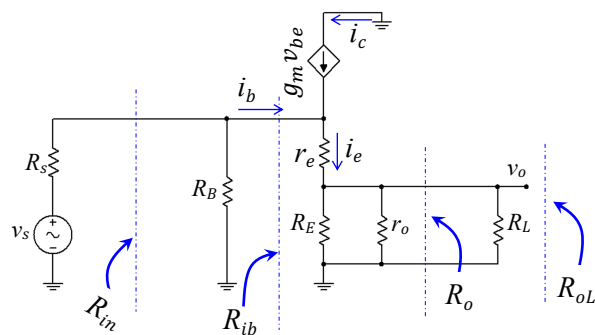
### Small-Signal Analysis of a CC Amplifier: Output Resistance



Output resistance  $R_o$  is

$$R_o = \left[ r_o || R_E || \left( r_e + \frac{R_B || R_s}{\beta + 1} \right) \right]$$

$$\text{Also, } R_{oL} = R_L || R_o$$

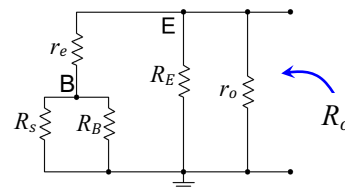


Notice that resistors in the base side are **divided by  $(\beta + 1)$**

30

30
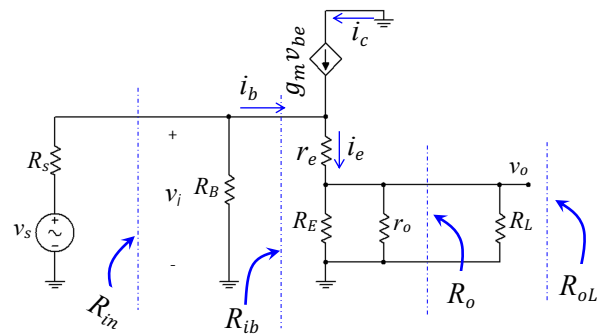
### Small-Signal Analysis of a CC Amplifier: Voltage Gain



The voltage gain  $A_v$  is

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_b}$$

$$\text{or, } A_v = \frac{i_e (R_L || r_o || R_E)}{i_e [r_e + (R_E || r_o || R_L)]}$$

If  $r_e \ll R_L$ , we can write


$$A_v = \frac{(R_L || r_o || R_E)}{r_e + (R_E || r_o || R_L)} \cong 1$$

- $A_v$  cannot be higher than one
- If  $R_L$  is comparable with  $r_e$ ,  $A_v$  can be significantly lower than one

31

31
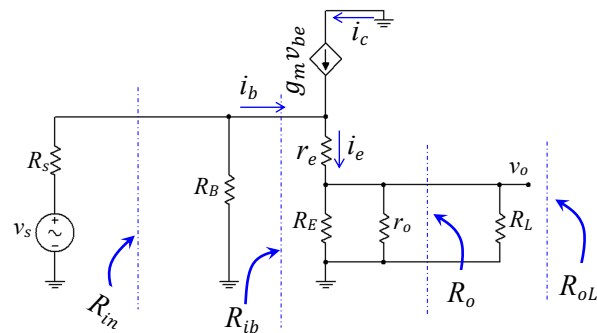
### Small-Signal Analysis of a CC Amplifier: Current Gain



The current gain remains the same, i.e.


$$A_i = \beta$$

32

32


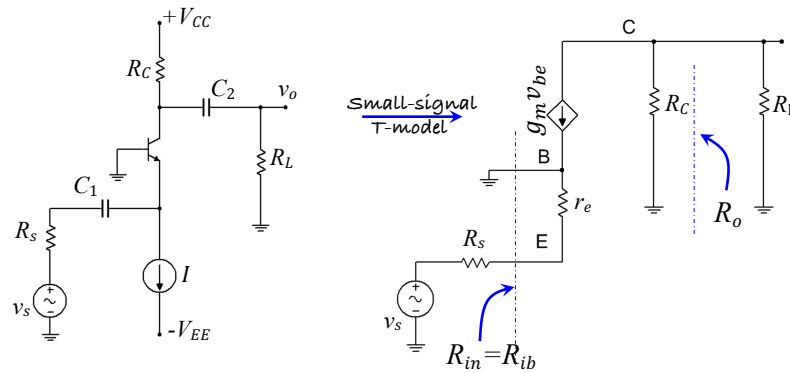
### Small-Signal Analysis of a CB Amplifier



Input resistance

$$R_{in} = r_e$$

Open circuit voltage gain

$$A_{vo} = g_m R_C$$

Output resistance

$$R_o = R_C$$


Current gain

$$A_i = \alpha \approx 1$$

33

33


### Impedance Matching

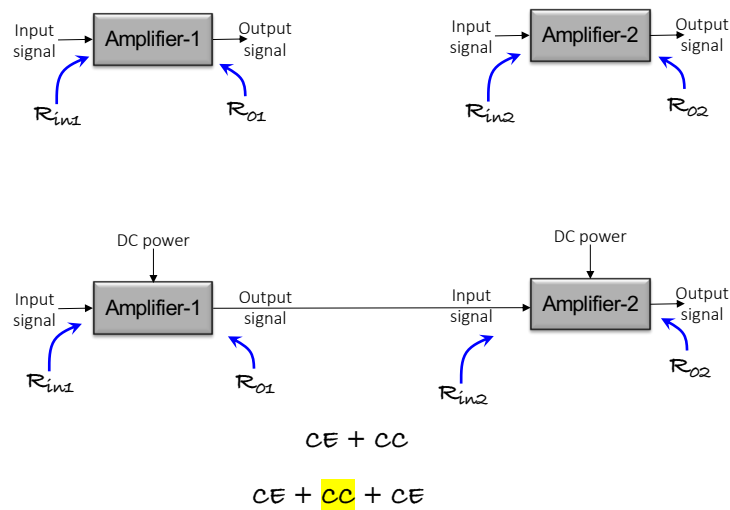

34

34
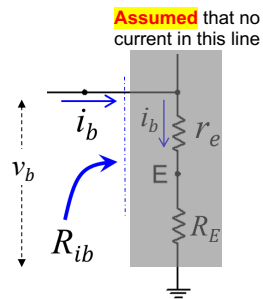
### EXTRA Slide for Understanding $(\beta + 1)$ Factor in the Resistance




Here, the resistance  $R_{ib}$  is

$$R_{ib} = \frac{v_b}{i_b} = \frac{i_b(r_e + R_E)}{i_b}$$

$$\text{or, } R_{ib} = r_e + R_E$$

This is incorrect for a transistor

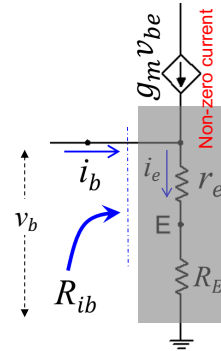

$$R_{ib} = \frac{v_b}{i_b} = \frac{i_e(r_e + R_E)}{i_b}$$

$$\text{or, } R_{ib} = \frac{i_b(\beta + 1)(r_e + R_E)}{i_b}$$

[Since  $i_e = (\beta + 1)i_b$ ]

$$R_{ib} = (\beta + 1)(r_e + R_E)$$

35

35