

ENEL469: Analog Electronic Circuits

Department of Electrical and Computer Engineering
University of Calgary

Lab #1: Analyzing a BJT Common Emitter amplifier and logic gates

Everyone must complete pre-lab and bring his/her own (printed) copy of this lab manual

Student's Name	
----------------	--

Do not write here

	Late arrival	
	Pre-lab ready	
	Report printed	
	Table interview	

Supplies:

- a) BJT transistor: 2N3904 (Datasheet uploaded on Blackboard)
- b) Available resistors: See a list posted on D2L
- c) Potentiometer (10k)
- d) Assume $\beta = 165$, $V_A = 100 \text{ V}$, $V_{CE(\text{Sat})} = 0.2 \text{ V}$, $V_{BE(\text{ON})} = 0.7 \text{ V}$

Pre-lab Exercises

Pre-lab (Part 1):


Consider the circuit shown in figure 1 with $R_2 = 6.8K$. Determine I_B , I_C , I_E , and V_{CE} . Assume $V_{BE(ON)} = 0.7$ V. Show your work in the space provided below and write these calculated current and voltage values in the second column of table-1 on page #7.

Pre-lab (Part 2): Consider the circuit shown in figure 1 with $R_2 = 6.8K$. Calculate the small signal parameters r_π , r_e , r_0 and g_m . Show your work and write your answers in the table below.

r_π	K Ω
r_e	Ω
r_0	K Ω
g_m	mA/V

Pre-lab (Part 3): Consider the circuit shown in figure 1 with $R_2 = 6.8K$. Draw the load line in the graph provided below (Do not neglect base current).

Show your work here.

 

Pre-lab (Part 4): Consider the BJT NAND gate circuit given in figure 3. V_A and V_B are two inputs of the logic gate. The dc output is taken from the collector of Q_1 . Design (i.e., determine R_{B1} and R_{B2}) the circuit for NAND operation. Determine the currents and voltages indicated in the following table for all four possible combinations. For simplicity, assume the collector emitter saturation voltage is 0.2 V (i.e., $V_{CE(Sat)} = 0.2 \text{ V}$) and $I_C = I_E$.

Space for calculating R_{B1} and R_{B2}

Case-A: $V_A = 0 \text{ V}$ and $V_B = 0 \text{ V}$:

Case-B: $V_A = 0 \text{ V}$ and $V_B = 5 \text{ V}$:

Case-C: $V_A = 5 \text{ V}$ and $V_B = 0 \text{ V}$:

Case-D: $V_A = 5\text{ V}$ and $V_B = 5\text{ V}$:

Current and voltage values obtained in part-4 of the pre-lab exercise


	Input voltages		Input currents		Output currents		Output
	$V_A\text{ (V)}$	$V_B\text{ (V)}$	$I_{B1}\text{ (}\mu\text{A)}$	$I_{B2}\text{ (}\mu\text{A)}$	$I_{C1}\text{ (mA)}$	$I_{C2}\text{ (mA)}$	$V_0\text{ (V)}$
Case-A	0	0					
Case-B	0	5					
Case-C	5	0					
Case-D	5	5					

Does it look like an AND gate?

Lab Studies

A: Measure biasing currents and voltages

 Implement the following circuit on a breadboard. This is the circuit, which you have analyzed in the pre-lab. Record the data in table 1.



Resistor values as per colour code

$R_1 = 47 \text{ K}\Omega$

$R_2 = 6.8 \text{ K}\Omega$

$R_C = 1 \text{ K}\Omega$

$R_E = 150 \Omega$

Measured values of the resistors

$R_1 = \quad \text{K}\Omega$

$R_2 = \quad \text{K}\Omega$

$R_C = \quad \text{K}\Omega$

$R_E = \quad \Omega$

Figure 1: Common-emitter amplifier circuit with emitter resistor

Table 1: A comparison between calculated (pre-lab) and experimental results

Parameters	Calculated result (from the pre-lab)	Experimental result
$V_{BE} \text{ (V)}$		
$I_B \text{ (}\mu\text{A)}$		
$V_{CE} \text{ (V)}$		
$I_C \text{ (mA)}$		
$I_E \text{ (mA)}$		
Effective β at the operating condition		
Effective α at the operating condition		

Verify $I_E = I_C + I_B$ using the obtained current values in your experiment. Do you see anything strange? Why so?

B: Determine DC gains and small-signal parameters

For this part, you need to measure currents and voltages at two different operating points Q1 and Q2. **The only element you are allowed to change in this circuit is R_2 .** It would be better to use a potentiometer to set the operating points Q1 and Q2.

You must be able to explain how I_C and V_{CE} depend on R_2 ?

a) Set the operating point (Q_1) at $V_{CE} = 3\text{ V}$ by adjusting R_2 . Measure I_B , V_{BE} , I_C , and V_{CE} and record these in table-2.

b) Set the operating point (Q_2) at $V_{CE} = 11\text{ V}$ by adjusting R_2 . Measure I_B , V_{BE} , I_C , and V_{CE} and record these in table-2.

Table-2: Data for DC gains

	I_B (μA)	V_{BE} (V)	I_C (mA)	V_{CE} (V)
At Q_1				
At Q_2				

c) Determine the DC current gain, DC voltage gain and DC power gain using the current and voltage values recorded in table 2.

$$\text{DC current gain} = A_{I(\text{DC})} = (I_{C, Q1} - I_{C, Q2}) / (I_{B, Q1} - I_{B, Q2})$$

$$\text{Voltage gain} = A_{V(\text{DC})} = (V_{CE, Q1} - V_{CE, Q2}) / (V_{BE, Q1} - V_{BE, Q2})$$

$$\text{Power gain} = A_{P(\text{DC})} = A_{V(\text{DC})} \times A_{I(\text{DC})}$$

d) Using the current and voltage values recorded in table 2, calculate the small-signal parameters and voltage gain [$A_v = -g_m \times (\text{load})$] and record them in table 3.

Table-3: Obtained values of the small signal parameters.

	r_π (k Ω)	r_e (Ω)	r_o (k Ω)	g_m (mA/V)	$A_v \approx - (g_m R_C) / (1 + g_m R_E)$
At Q₁					
At Q₂					

Discussion:

Did you expect the corresponding small-signal parameters at Q1 and Q2 to be different?

Are the values obtained in table-3 reasonable?

Compare the DC voltage gain with the voltage gains recorded in table 3. Are they same or different? Why so?

C: Determine the load-line

Measure collector currents for different collector-emitter voltages. Change V_{CE} by changing R_2 . You can use a potentiometer. Record your data in table 4 and plot these in the graph provided in figure 2.

Table-4: Data for determining load-line

V_{CE} (V)	2	4	8	10	12	14
I_C (mA)						

 


Figure 2. Load line determined from experimental data

C: Construct a two-input BJT NAND gate

- Implement the circuit shown in figure 3.
- Consider the following logic definition: 0.0–0.5 V: Logic '0' and 4.5–5.0 V: Logic '1'
- Verify the NAND operation

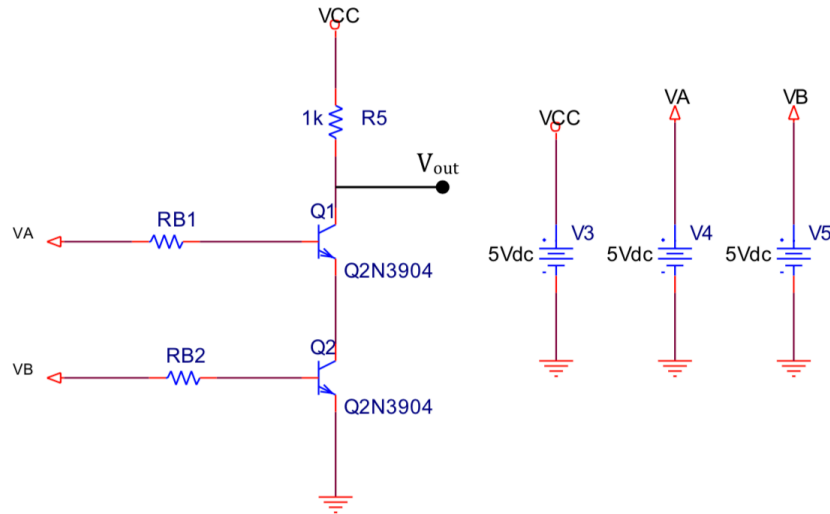


Figure 3. Two-input BJT NAND gate.

Table-5: The BJT NAND gate truth table

V_A		V_B		V_o	
Logic	(V)	Logic	(V)	Logic	(V)
0	0	0	0		
0	0	1	5		
1	5	0	0		
1	5	1	5		
Observations					

Optional work: Construct and verify a two-input AND gate