
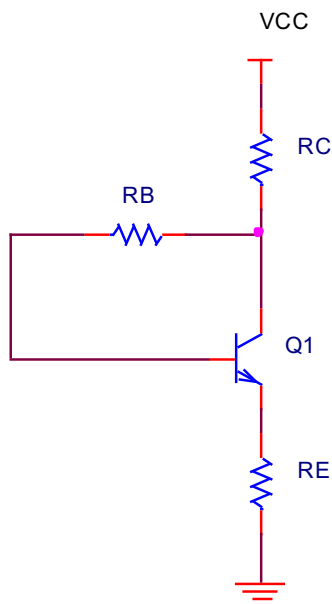


**Practice Problem Set #3**  
**Biassing Techniques**  
**ENEL469: Analog Electronics**

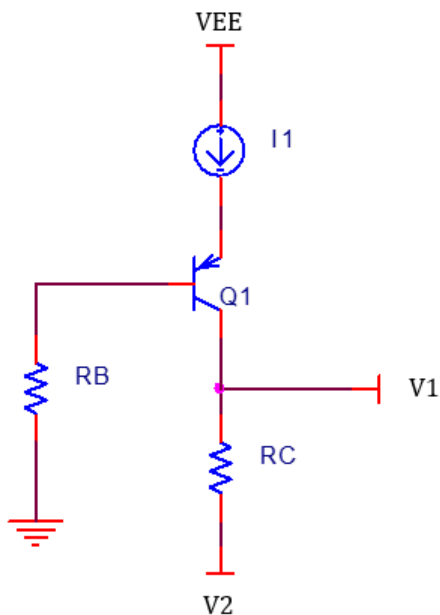
1. For the circuit shown below, determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CB}$  and  $V_{CE}$ . Use the following characteristics:  $\beta = 75$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ ,  $V_{CC} = 5 \text{ V}$ ,  $R_C = 10 \text{ k}\Omega$ ,  $R_B = 20 \text{ k}\Omega$  and  $R_E = 2 \text{ k}\Omega$ .



2. Consider the following circuit where  $\beta = 75$  and  $|V_{BE(ON)}| = 0.7 \text{ V}$ ,  $V_{EE} = 5 \text{ V}$ ,  $V_1 = -1 \text{ V}$ ,  $V_2 = -5 \text{ V}$ ,  $I_1 = 0.5 \text{ mA}$ ,  $R_B = 25 \text{ k}\Omega$ . Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $R_C$ ,  $V_{CB}$ ,  $V_{CE}$ , and power absorbed or delivered by the  $I_1$  current source.




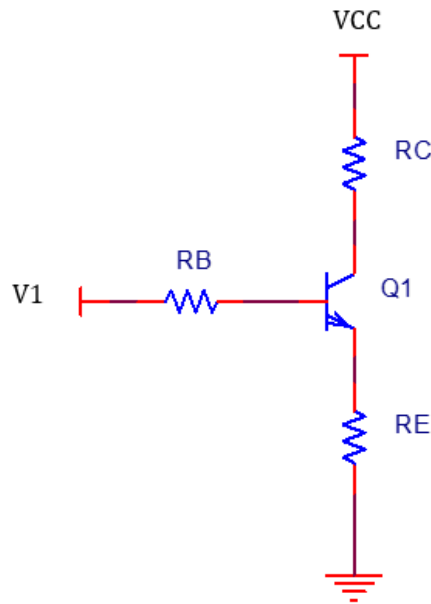3. The circuit shown below to be designed such that  $I_C = 0.8 \text{ mA}$  and  $V_{CE} = 2 \text{ V}$  for the case when  $R_E = 1 \text{ k}\Omega$ . Assume  $\beta = 80$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ ,  $V_{CC} = 5 \text{ V}$  and  $V_1 = 2 \text{ V}$ . Find the value of  $R_C$  and  $R_B$ .




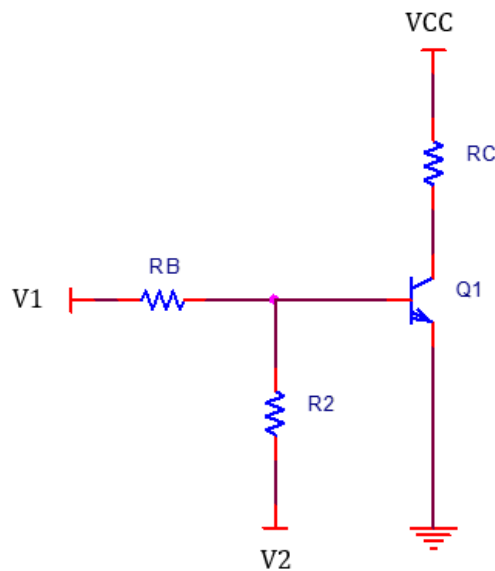4. Consider the given circuit where  $\beta = 80$  and  $V_{BE(ON)} = 0.7 \text{ V}$ . Determine  $V_1$  such that  $V_{CE} = 6 \text{ V}$ . Use the following characteristics:  $R_C = 2.2 \text{ k}\Omega$ ,  $R_B = 15 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $V_{CC} = 12 \text{ V}$ ,  $V_2 = -12 \text{ V}$ .


Note: The terminal where  $V_1$  is measured is not open, but it is connected to other part of the circuit not shown here.



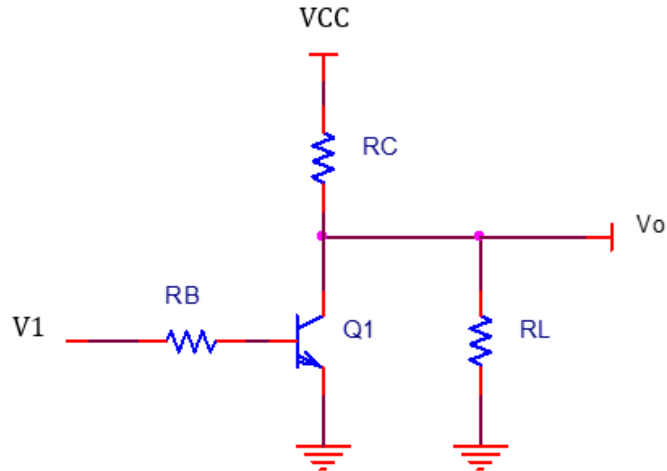5. The current gain of the transistor shown in the following circuit is 75 and  $V_{CE(sat)} = 0.2 \text{ V}$ . Given,  $V_{CC} = 5 \text{ V}$ ,  $R_C = 5 \text{ k}\Omega$ ,  $R_B = 50 \text{ k}\Omega$ ,  $R_L = 10 \text{ k}\Omega$ . Determine  $V_o$  for,  
a)  $V_1 = 0 \text{ V}$  and  
b)  $V_1 = 2 \text{ V}$ .



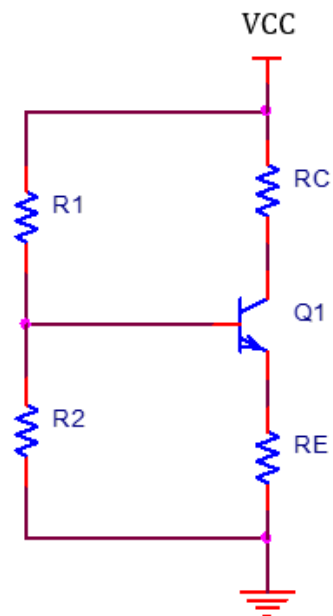6. In the circuit below,  $\beta = 100$ ,  $V_{CC} = 10 \text{ V}$ ,  $V_{BE(ON)} = 0.7 \text{ V}$ ,  $R_1 = 56 \text{ k}\Omega$ ,  $R_2 = 12.2 \text{ k}\Omega$ ,  $R_C = 2 \text{ k}\Omega$ ,  $R_E = 400 \Omega$ . Determine  $I_B$ ,  $I_C$ ,  $I_E$ , and  $V_{CE}$ .



7. The circuit below shows multistage amplifier where  $\beta = 100$  for each transistor and here the B-E junctions require 0.7 V to turn on. Given,  $V_{CC} = 5V$ ,  $V_1 = -5V$ ,  $R_1 = 100\text{ k}\Omega$ ,  $R_2 = 50\text{ k}\Omega$ ,  $R_{C1} = 5\text{ k}\Omega$ ,  $R_{E1} = 2\text{ k}\Omega$ ,  $R_{C2} = 1.5\text{ k}\Omega$ ,  $R_{E2} = 2\text{ k}\Omega$ . Determine  $V_{CE2}$ .

Note: Do not ignore the base currents.

