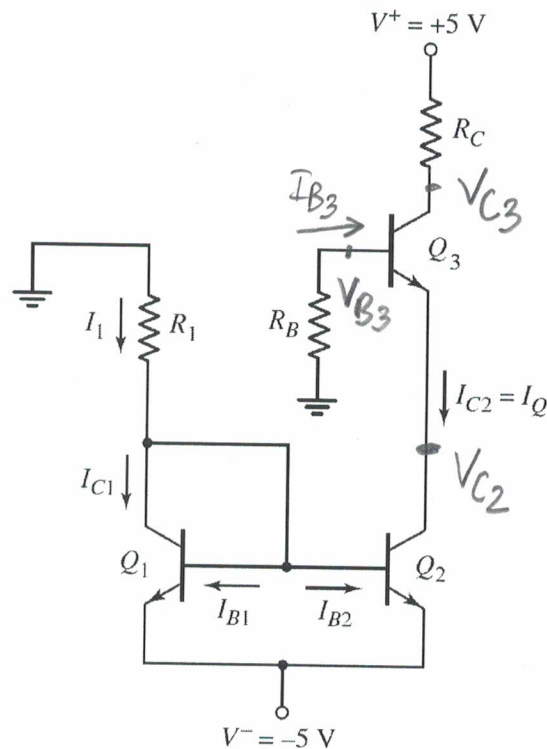


Practice Problem Set # 4

ENEL 469

1. Consider the circuit shown below where all the transistors are identical and, $R_1 = 10 \text{ k}\Omega$, $R_B = 100 \text{ k}\Omega$, $R_C = 2 \text{ k}\Omega$, $\beta = 50$, $V_{BE(ON)} = 0.7 \text{ V}$ and $V_A = \infty$. Find I_{B1} , I_{B2} , I_{B3} , V_{CE2} , and V_{CE3} . Do not ignore base currents.



Solution:

$$I_1 = \frac{0 - V_{BE(ON)} - V^-}{R_1} = \frac{-0.7 - (-5)}{10\text{k}} = 0.43 \text{ mA}$$

$$I_{C2} = \frac{I_1}{1 + 2/\beta} = \frac{0.43 \text{ mA}}{1 + 2/50} = 0.413 \text{ mA}$$

$$\therefore I_{B1} = I_{B2} = \frac{I_{C2}}{\beta} = 8.27 \text{ }\mu\text{A}$$

$$I_{C3} = I_{C2} \cdot \frac{\beta}{\beta + 1} = 0.405 \text{ mA} ; \quad I_{B3} = \frac{I_{C3}}{\beta} = 8.1 \text{ }\mu\text{A}$$

$$\therefore V_{B3} = -I_{B3} R_B = -0.81V$$


$$\therefore V_{C2} = V_{B3} - 0.7 = -0.81 - 0.7 = -1.51V$$

$$\therefore V_{CE2} = V_{C2} - V_{E2} = -1.51 - (-5) = 3.49V$$

$$V_{C3} = 5 - I_{C3} R_C = 4.19V$$

$$\therefore V_{CE3} = V_{C3} - V_{E3} = 4.19 - (-1.51) = 5.7V$$

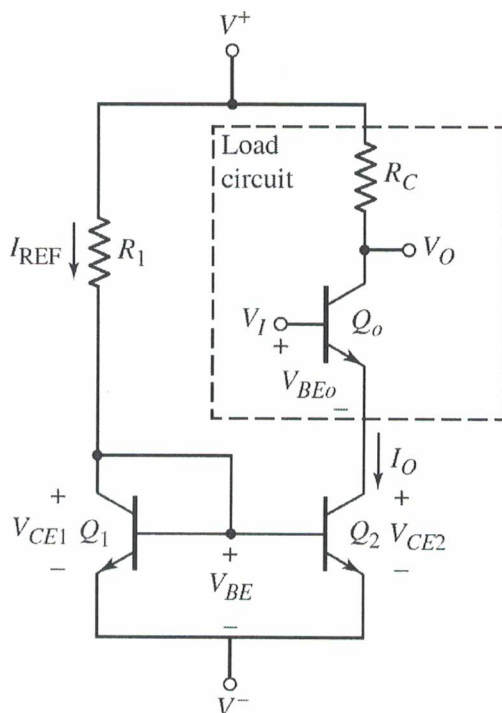2. Consider the following circuit with the parameters: $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$, $R_1 = 9.3\text{ k}\Omega$, $\beta = 50$, $V_{BE(ON)} = 0.7\text{ V}$, and $V_A = 80\text{ V}$. Determine the change in I_0 as V_{CE2} changes from 0.7 V to 5 V .



Solution:

$$I_{ref} = \frac{V^+ - V_{BE(ON)} - V^-}{R_1} = 1\text{ mA}$$

For $V_{CE2} = 0.7\text{ V}$, Q_1 and Q_2 are identically biased.

$$\therefore I_0 = \frac{I_{ref}}{1 + 2/\beta} = 0.962\text{ mA}$$

$$\therefore r_o = \frac{V_A}{I_0} = 83.2\text{ k}\Omega$$

Now, the change in load current is determined from:

$$\frac{dI_0}{dV_{CE2}} = \frac{1}{r_0}$$

$$\Rightarrow dI_0 = \frac{1}{r_0} dV_{CE2}$$


$$= \frac{1}{83.2k} (5 - 0.7)$$

$$= 0.052 \text{ mA}$$

\therefore The change in I_0 as V_{CE2} changes from 0.7V to 5V is: 0.052 mA

$$\therefore \text{Percent change in } I_0 : \frac{dI_0}{I_0} = \frac{0.052}{0.962} = 5.4\%$$

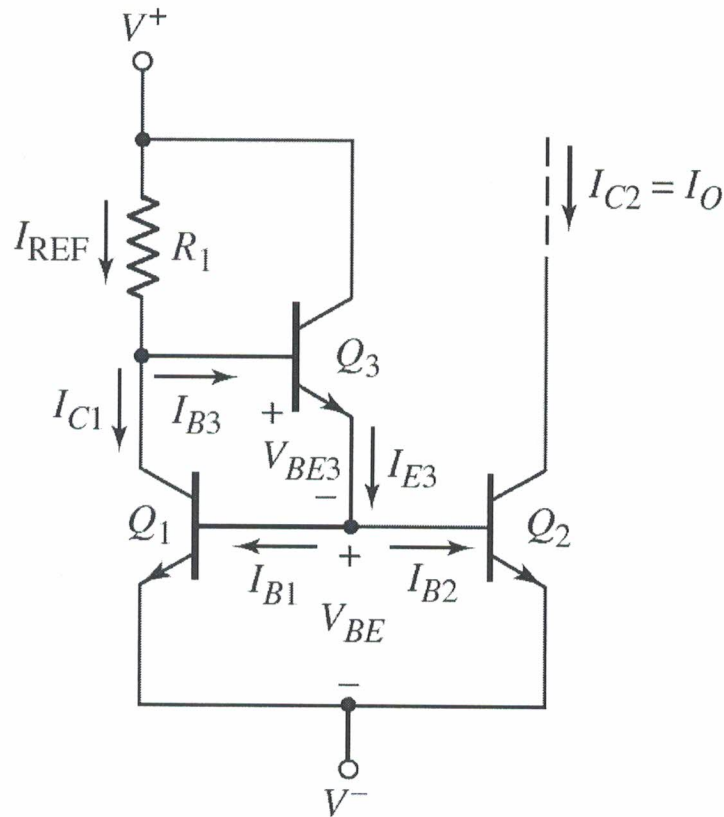3. Consider the circuit shown below having the parameters: $V^+ = 3 \text{ V}$, $V^- = -3 \text{ V}$, and $R_1 = 30 \text{ k}\Omega$. The parameters of the transistors Q_1 and Q_2 are $V_{BE1,2(\text{on})} = 0.7 \text{ V}$ and $\beta = 120$. The parameters of the transistor Q_3 are $V_{BE3(\text{on})} = 0.6 \text{ V}$ and $\beta_3 = 80$. Assume $V_A = \infty$ for all three transistors. Determine the value of each current indicated in the circuit.



$$I_{\text{ref}} = \frac{V^+ - V^- - V_{BE3(\text{on})} - V_{BE1,2(\text{on})}}{R_1}$$

$$= \frac{6 - 0.7 - 0.6}{30 \text{ k}} = 0.157 \text{ mA}$$

$$\therefore I_{\text{ref}} = I_{C1} + I_{B3} = I_{C1} + \frac{I_{E3}}{\beta_3 + 1} = I_{C1} + \frac{1}{\beta_3 + 1} (I_{B1} + I_{B2})$$

$$= I_{C1} + \frac{1}{\beta_3 + 1} \cdot \frac{2I_{C1}}{\beta} = I_{C1} \left(1 + \frac{2}{\beta\beta_3 + \beta} \right)$$

$$\Rightarrow I_{C1} = I_{\text{ref}} \cdot \frac{1}{1 + 2/(\beta + \beta\beta_3)} = 0.156968 \text{ mA} = I_{C2}$$

$$\therefore I_{B1} = I_{B2} = \frac{I_{C1}}{\beta} = 1.31 \text{ mA}$$

$$\therefore I_{E3} = 2I_{B1} = 2I_{B2} = 2.62 \text{ mA}$$

$$I_{B3} = I_{E3} / (\beta + 1) = 0.0323 \text{ mA}$$


4. Design a Widlar current source (find the values of R_1 and R_E) as shown in the following figure with the specifications:

Bias voltages: $V^+ = 5\text{ V}$, $V^- = -5\text{ V}$

Currents: $I_{\text{REF}} = 1\text{ mA}$ and $I_O = 12\text{ }\mu\text{A}$.

The transistors Q_1 and Q_2 are described as $V_{\text{BE}} = 0.8\text{ V}$ at $I_C = 10\text{ mA}$ and $\beta = 50$.

Do not ignore base currents.

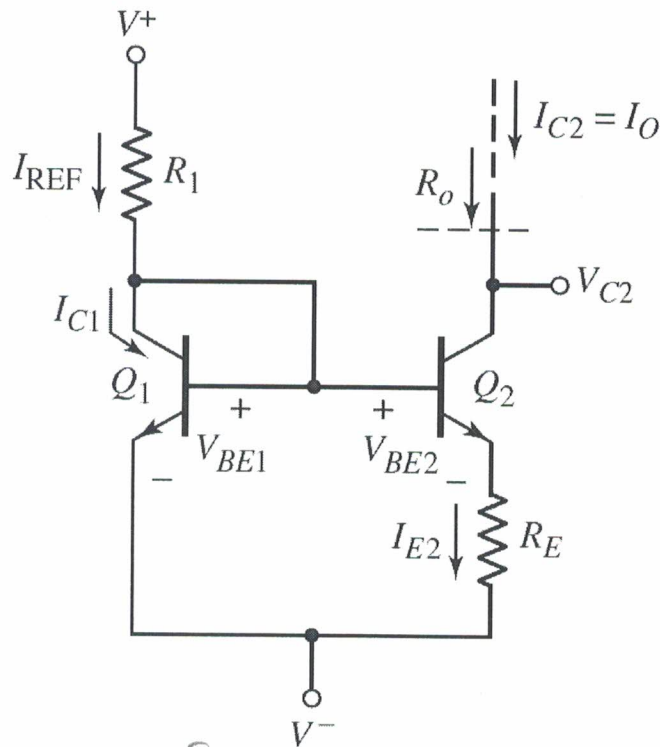

Solution:


$$I_{\text{ref}} = I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta} \Rightarrow I_{C1} = \frac{I_{\text{ref}} - I_{C2}/\beta}{1 + 1/\beta} = 0.98\text{ mA}$$

$$\therefore V_{\text{BE1}} = 0.8 + V_T \ln \frac{0.98\text{ mA}}{10\text{ mA}} = 0.742\text{ V}$$

$$V_{\text{BE2}} = 0.8 + V_T \ln \frac{12\text{ }\mu\text{A}}{10\text{ mA}} = 0.632\text{ V}$$

$$\therefore R_1 = \frac{V^+ - V^- - V_{\text{BE1}}}{I_{\text{ref}}} = 9.258\text{ k}\Omega; R_E = \frac{V_{\text{BE1}} - V_{\text{BE2}}}{I_{E2} = 12.24\text{ }\mu\text{A}} = 8.987\text{ k}\Omega$$

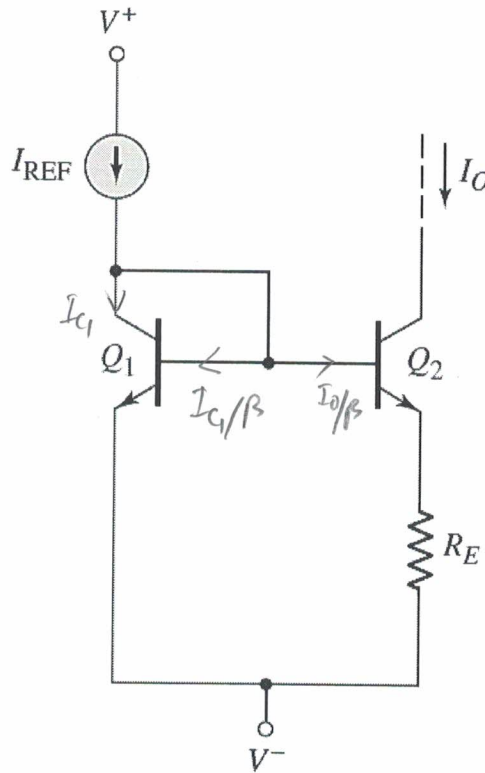5. In the following circuit assume that $I_{REF} = 120 \mu A$, $I_{S1} = I_{S2} = 2 \times 10^{-16} A$. a) Find V_{BE1} , b) If $I_0 = 50 \mu A$, determine V_{BE2} and R_E , c) Find I_0 if $R_E = 700 \Omega$, what is V_{BE2} ?



$$I_{C1} = I_S e^{V_{BE1}/V_T}$$

$$\Rightarrow V_{BE1} = V_T \ln \frac{I_{C1}}{I_S}$$

Solution:

a) Ignoring base currents:

$$I_{C1} = I_{REF} = 120 \mu A$$

$$\therefore V_{BE1} = V_T \ln \frac{I_{C1}}{I_S} = 0.678 V$$

b) $I_0 = 50 \mu A$;

$$\therefore V_{BE2} = V_T \ln \frac{I_0}{I_S} = 0.656 V$$

$$\therefore R_E = \frac{V_{BE1} - V_{BE2}}{I_0} = 440 \Omega$$

c) $R_E = 700 \Omega$

$$V_{BE1} - V_{BE2} = I_0 R_E = V_T \ln \frac{I_{ref}}{I_0}$$

By applying trial and error method:


$$I_0 = 40 \mu A$$

$$\therefore V_{BE2} = V_{BE1} - I_0 R_E$$

$$= 0.678 - 40 \times 10^{-6} \times 700$$

$$= 0.65 V$$

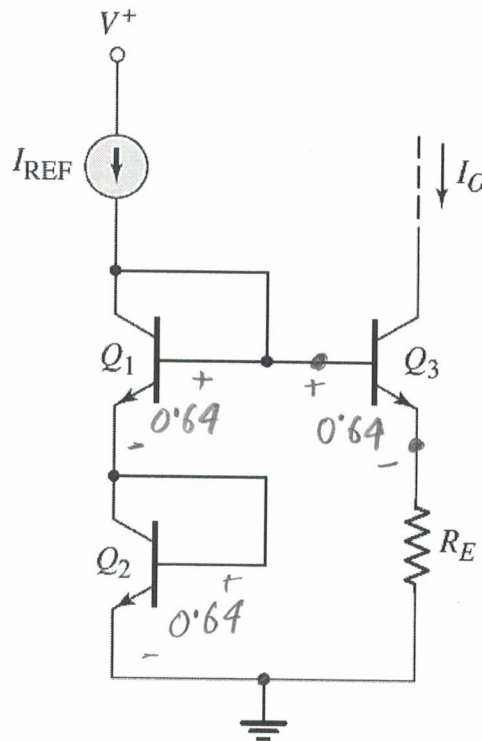6. Consider the circuit shown below. Neglect base currents and assume $V_A = \infty$. Determine the value of R_E such that $I_O = I_{REF} = 100 \mu A$. Assume $V_{BE} = 0.7 V$ at a collector current of $1 mA$.




Solution: $I_O = I_{ref} = 100 \mu A = 0.1 mA$

$$V_{BE} \text{ at } 0.1 mA \Rightarrow V_{BE} = 0.7 + V_T \ln \frac{0.1 mA}{1 mA} \\ = 0.64 V$$

Note that ignoring base current will cause every transistor to draw $0.1 mA$, thus, $V_{BE} = 0.64$ for all transistors.

$$\therefore I_O R_E = V_{BE} \\ \Rightarrow R_E = \frac{V_{BE}}{I_O} = 6.4 k\Omega$$

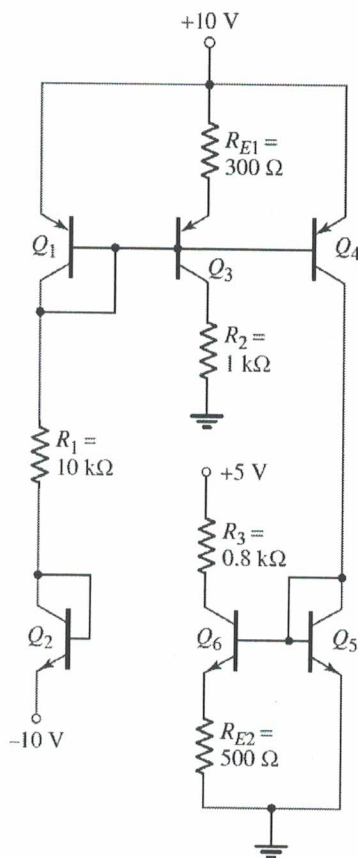7. For the circuit shown in the following figure assume transistor parameters $V_{BE} = V_{EB} = 0.7 \text{ V}$ for all transistors except Q3 and Q6, and let $\beta = \infty$. Find the collector current in each transistor.



Solution: $\beta = \infty$; ignoring base currents.

$$I_{E1} = I_{C2} = \frac{10 - 0.7 - 0.7 - (-10)}{10 \text{ k}} = 1.86 \text{ mA}$$

$$I_{C4} = I_{C5} = 1.86 \text{ mA}$$

$$I_{C3} R_{E1} = V_{BE1} - V_{BE3} = V_T \ln \frac{I_{E1}}{I_{C3}}$$

By trial and error method; Students will not be required to do trial and error method in exams

$$I_{C3} = 0.195 \text{ mA}$$

Again;

$$I_{C6} R_{E2} = V_{BE5} - V_{BE6} = V_T \ln \frac{I_{C5}}{I_{C6}}$$

By trial and error;

$$I_{C6} = 0.136 \text{ mA}$$

