
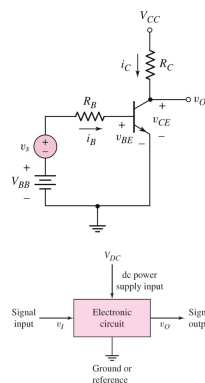



Application of an Input Signal

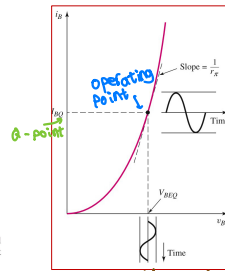

-DC biasing condition
(not changing with time)



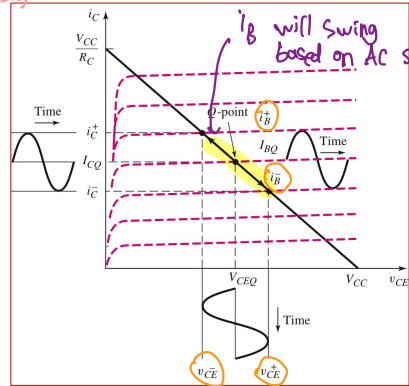* The current and voltage changes based on signal applied



* i_b will change v_c

$$V = I R$$



$$R = \frac{V}{I}$$

- At $v_s = 0$ (no input signal), $V_{CE} = V_{CEQ}$ and $I_C = I_{CQ}$ (Q-point)
- The **operating point** moves along the **load-line** with the changes of **input signal**

1

1

Transfer Characteristics

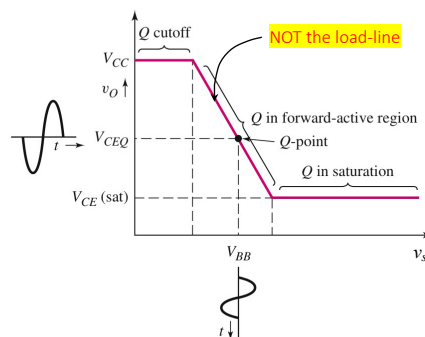
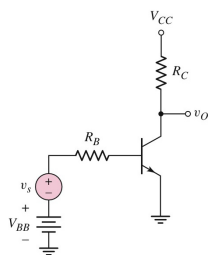


- When an alternating input signal (v_s) is applied V_{CE} and I_C start **changing with time in accordance with the input signal**
- Large v_s can take the transistor into **saturation mode**
- Large **negative** v_s can take the transistor into **cut-off mode**
- A **small input signal** can keep the transistor in **active region**

2

2

Small-Signal Operation: Basic Equations

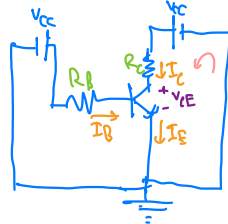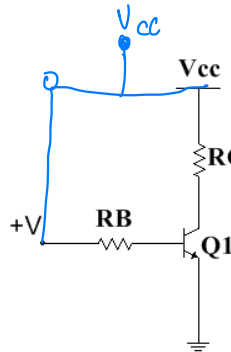

$$V_{CC} - I_C R_C - V_{CE} = 0$$

Recall that

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \dots \dots \dots (1)$$

$$I_E = \frac{I_C}{\alpha} \dots \dots \dots (2)$$

$$I_B = \frac{I_C}{\beta} \dots \dots \dots (3)$$

$$V_C = V_{CE} = V_{CC} - I_C R_C \dots \dots (4)$$

$$V_{CE} - I_C R_C - V_{CE} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

3

Shockley's

3

Small-Signal Operation: Conventions

I or V upper case means DC current or voltage

DC only

$I_B, V_C, V_E, \text{ or } I_E$ upper case suffix means respective DC current or voltage

i or v lower case means AC signal current or voltage

AC only

$i_b, v_c, v_e, \text{ or } i_e$ lower case suffix means respective signal current or voltage

$i_B, v_C, v_E, \text{ or } i_E$ This means DC + Signal = total current or total voltage

mix

4

4

Small Signal Analysis of BJT

Neso Academy #92


- A small signal is one that will keep transistor in active region

Active \rightarrow CB is rev biased
 \rightarrow EB is fwd biased

(transistor acts as amplifier)

Total response = DC response + AC response

BJT amplifier circuit:

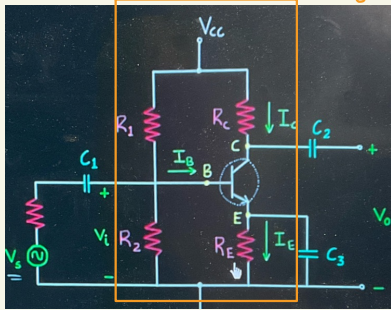

voltage divider bias

- In DC we only consider circuit inside rectangle, cuz C_1 and C_2 will act as open circuits
- In AC, must consider rest of circuit cuz capacitors will act as short circuits

C_1 and C_2 are coupling capacitors

C_3 is bypass capacitor

reactance of capacitor

$$X_C = \frac{1}{2\pi f C}$$

capacitance

for DC signal:
 $f = 0$

$$X_C = \frac{1}{0} \approx \infty$$

\therefore all 3 capacitors will act as open circuits

for AC signal:
 $f \neq 0$

capacitance is high

$$X_C = \frac{1}{\text{large num}} \approx 0$$

\therefore all capacitors act as short circuits

they all have high capacitance values,
 \therefore short circuit for AC

- C_1 is coupling previous stage with orange rect
- C_2 is coupling next stage with orange rect

\therefore needed so that V_s and V_o don't interfere with DC biasing voltage (V_{CC}), or else operating point will change

• C_3 bypasses AC signal

- AC signal can either go thru R_E or C_3 , but it picks C_3 cuz no resistance.
so R_E is short circuited.

allowing gain to increase

ASK prof
- what model is this?
 π , hybrid π , r_e , T

10/2/20

Equations
hold in active
region

it has to do with
expansion of exponential
series, no need
to know math behind
it

Small-Signal Parameters: Transconductance

The total base-emitter voltage is

$$v_{BE} = V_{BE} + v_{be}$$

Thus, the total collector current is

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} = I_S e^{\frac{V_{BE} + v_{be}}{V_T}}$$

$$i_C = I_S e^{\frac{V_{BE}}{V_T}} = I_S e^{\frac{V_{BE}}{V_T}} \times e^{\frac{v_{be}}{V_T}}$$

$$i_C = I_C \times e^{\frac{v_{be}}{V_T}} \dots \dots \dots (5)$$


If $v_{be} \ll V_T$ eq (5) can be written as

$$i_C \approx I_C \left(1 + \frac{v_{be}}{V_T} \right) = I_C + \frac{I_C}{V_T} v_{be} \dots \dots (6)$$

$$i_C = I_C + g_m v_{be}$$

Here, $g_m = \text{Transconductance}$
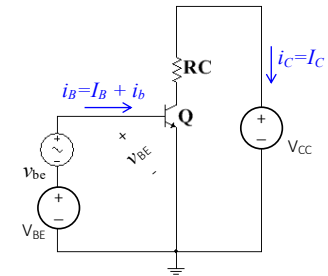
$$g_m = \frac{I_C}{V_T} \dots \dots \dots (7)$$



DC collector current

what is transconductance?
what effect does it have on circuit?

indicates biasing methods

5

5

signal current
doesn't depend on β

Total
current and AC
signal, are the
same symbol?

between
collector and
emitter

Small-Signal Parameters: Current Source


We have just obtained that

$$i_C = I_C + g_m v_{be}$$


$$i_C = I_C + i_c$$

Total current = DC + signal

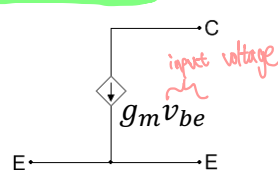Thus, transistor is a **voltage controlled current source** as shown below




For npn transistor
downwards

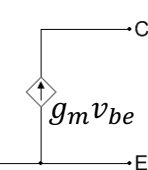

For pnp transistor
upwards

$$i_c = \frac{I_C}{V_T} v_{be} = g_m v_{be} \dots \dots \dots (8)$$

* g_m is constant factor

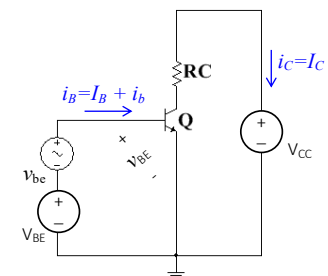

6

6

Small-Signal Parameters: The Input Resistance at the Base

The signal component of base current is


signal component of collector current $i_c = \frac{I_C}{V_T} \times v_{be}$ From eq (8)

or, $i_b = \frac{1}{\beta} \times (\beta I_B) \times \frac{1}{V_T} \times v_{be}$

or, $\frac{v_{be}}{i_b} = \frac{V_T}{I_B}$

or, $r_{\pi} = \frac{V_T}{I_B}$ (9)

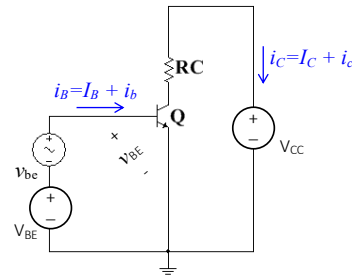- $r_{\pi} = (v_{be}) / (i_b) =$ small-signal resistance at the base
- r_{π} is also the small-signal input resistance for CE and CC configurations
- This is the resistance experienced by the signal at the base, i.e., between base and emitter
- r_{π} depends on biasing condition



*when you bias you fix the parameters.
AC doesn't change the parameters

7

Small-Signal Parameters: The Input Resistance at the Base (Continued)

The signal component of base current is

$i_b = \frac{i_c}{\beta} = \frac{1}{\beta} \times \frac{I_C}{V_T} \times v_{be}$ From eq (8)

or, $i_b = \frac{1}{\beta} \times (g_m) \times v_{be}$

or, $\frac{v_{be}}{i_b} = \frac{\beta}{g_m}$



or, $r_{\pi} = \frac{\beta}{g_m}$ (10)

$= \frac{V_T}{I_B}$

So g_m and G_r depends on our biasing, as I_B is in the term

Transconductance

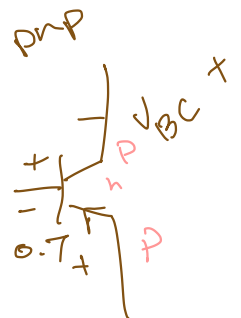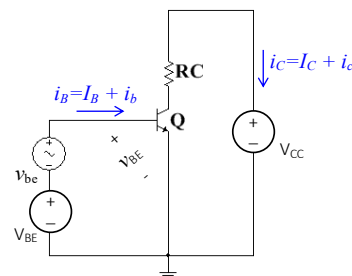- g_m depends on biasing condition
- β is an inherent property of a transistor




- if P is the wpt n then it's fwd



8

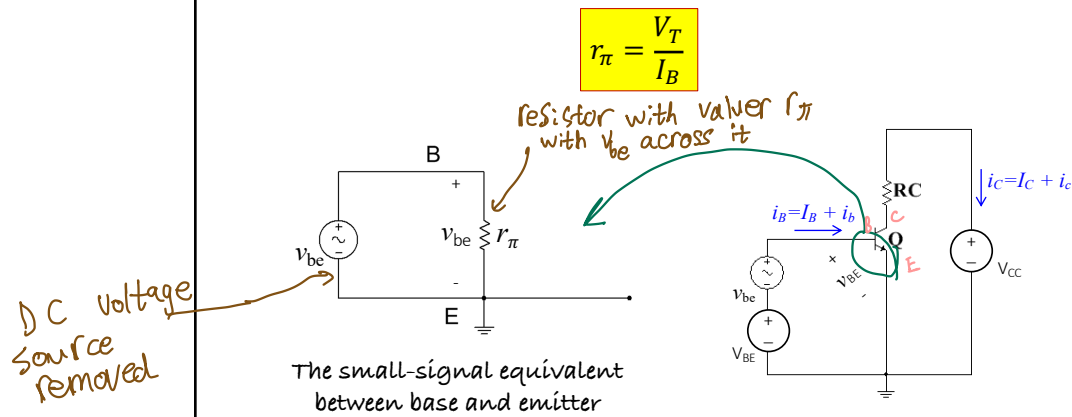Small-Signal Parameters: The Input Resistance at the Base (Continued)



9

9

Small-Signal Parameters: Emitter Resistance

The signal component of emitter current is

$$i_e = \frac{i_c}{\alpha} = \frac{1}{\alpha} \times \frac{I_C}{V_T} \times v_{be} \quad \text{From eq (8)}$$


$$\text{or, } i_e = \frac{I_E}{V_T} \times v_{be}$$

(Ohm's law)
Resistor equation

$$\text{or, } \frac{v_{be}}{i_e} = \frac{V_T}{I_E}$$

$$\text{or, } r_e = \frac{V_T}{I_E}$$

... (11)

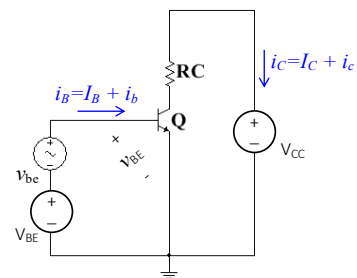

- $r_e = (v_{be}) / (i_e) = \text{small-signal resistance at the emitter}$
- r_e depends on biasing condition

10

10

- what will the small signal equivalent look like??
- does it replace r_π ??

Small-Signal Parameters: Emitter Resistance (Continued)

We have just derived

$$r_e = \frac{V_T}{I_E}$$

$$\text{or, } r_e = \frac{V_T \alpha}{I_C}$$

$$\text{or, } r_e = \frac{\alpha}{g_m} \dots \dots \dots (12)$$

$$= \frac{I_C}{V_T}$$


$$\text{or, } r_e \approx \frac{1}{g_m} \dots \dots \dots (13)$$

$$\alpha = \frac{I_C}{I_E}$$

$$\downarrow I_E = \frac{I_C}{\alpha}$$

[Using eq (2)]

$\alpha \approx 1$
in most cases

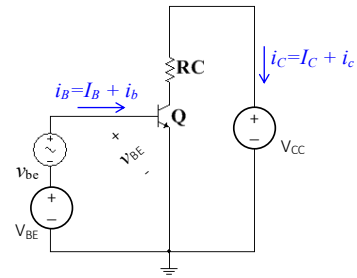

Notice that

$$v_{be} = i_b r_\pi = i_e r_e$$

$$\text{or, } r_\pi = \frac{i_e}{i_b} r_e = \frac{(\beta + 1) i_b}{i_b} r_e$$

$$r_\pi = (\beta + 1) r_e \dots \dots \dots (14)$$

11

11

Transistor Output Resistance

Recall Early voltage. The linear dependence of i_C versus v_{CE} is expressed by


$$i_C = I_S e^{\left(\frac{v_{BE}}{V_T}\right)} \left(1 + \frac{v_{CE}}{V_A}\right) \dots \dots \dots (15)$$

The output (collector) resistance is obtained from the slope as

$$\frac{1}{r_o} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{v_{BE} = \text{constant}}$$

using eq (15) we have,

$$r_o \cong \frac{V_A}{I_C}$$

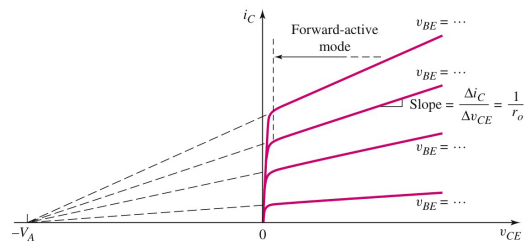

- If $V_A \rightarrow \infty$, $r_o = \infty$ and the curves get horizontal (zero slope)
- Transistor is a current source
- r_o is the internal resistance of the current source
- Recall that the internal resistance of an ideal current source is infinite

12

12

Huh??

where did this come from?

how did he go from here to here?

how??

do I need to
memorise derivatives?

Small-Signal Parameters: Summary

Transconductance $g_m = \frac{I_C}{V_T}$

Input resistance at base $r_\pi = \frac{V_T}{I_B}$ or $\frac{\beta}{g_m}$ or $(\beta+1)r_e$

Input resistance at emitter $r_e = \frac{V_T}{I_E} \approx \frac{1}{g_m}$

Output resistance $r_o \cong \frac{V_A}{I_C}$

Additional relationships

$r_\pi = \frac{\beta}{g_m}$ $r_e = \frac{\alpha}{g_m}$ $r_e \approx \frac{1}{g_m}$ $r_\pi = (\beta + 1)r_e$

13

13

Small-Signal Model: π -Model

npn transistor

Small-signal equivalent (npn transistor)

Diagram showing the π -model for an npn transistor. The base-emitter junction is represented by a voltage source v_{be} in series with a resistance r_π . The collector current is i_c , and the base current is i_b . The output resistance r_o is shown in parallel with the dependent current source $g_m v_{be}$.

Sometimes V_T is used to denote V_{be}


pnp transistor

Small-signal equivalent (pnp transistor)


Diagram showing the π -model for a pnp transistor. The base-emitter junction is represented by a voltage source v_{be} in series with a resistance r_π . The collector current is i_c , and the base current is i_b . The output resistance r_o is shown in parallel with the dependent current source $g_m v_{be}$.

14


14

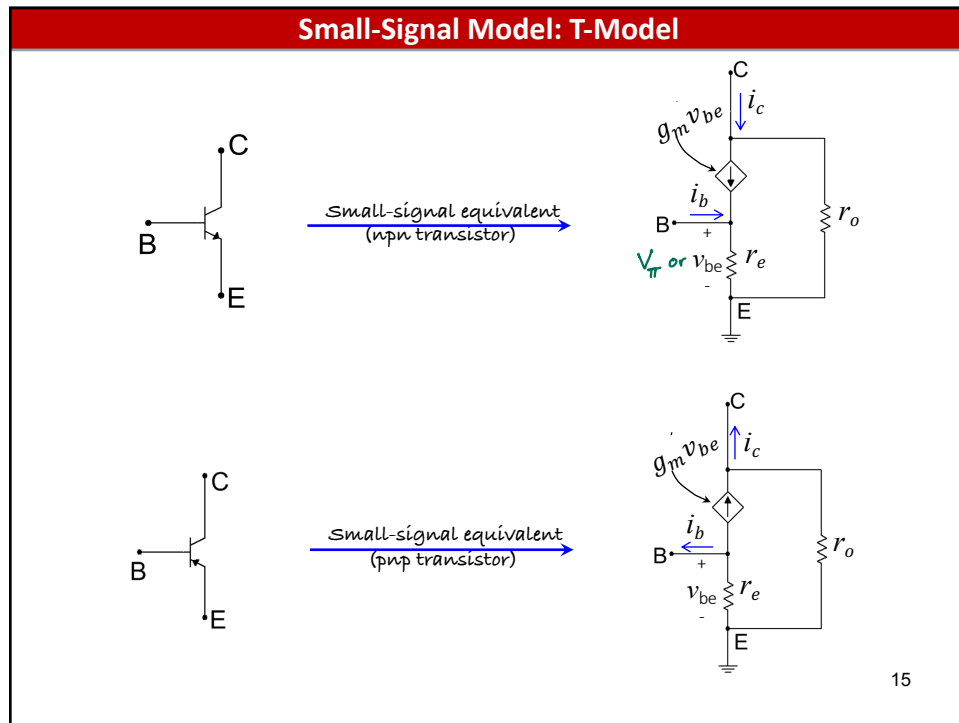


15

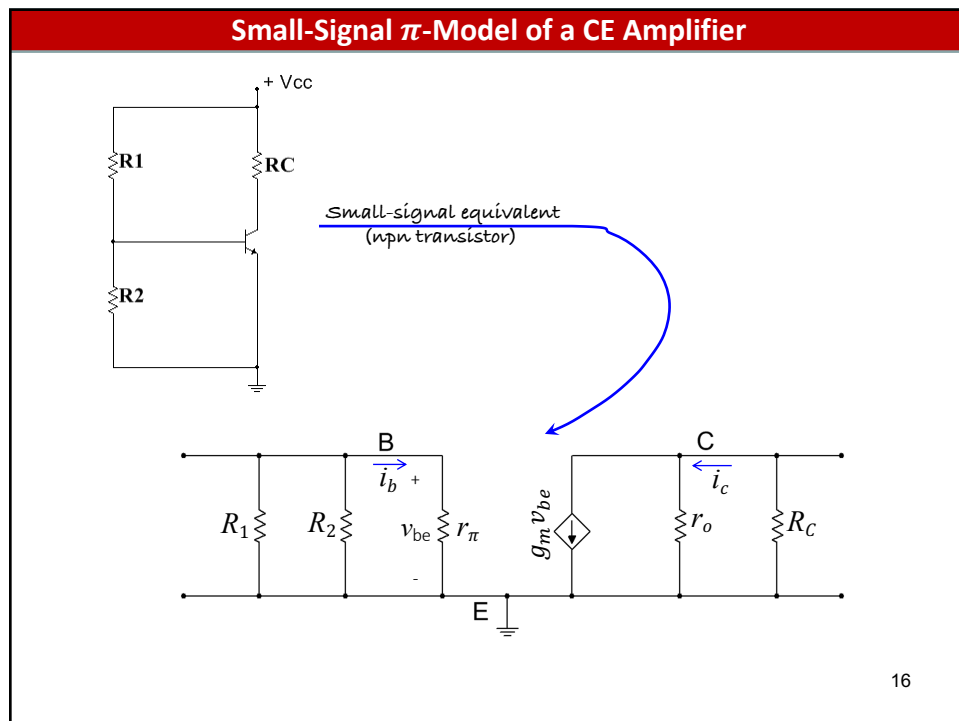

16

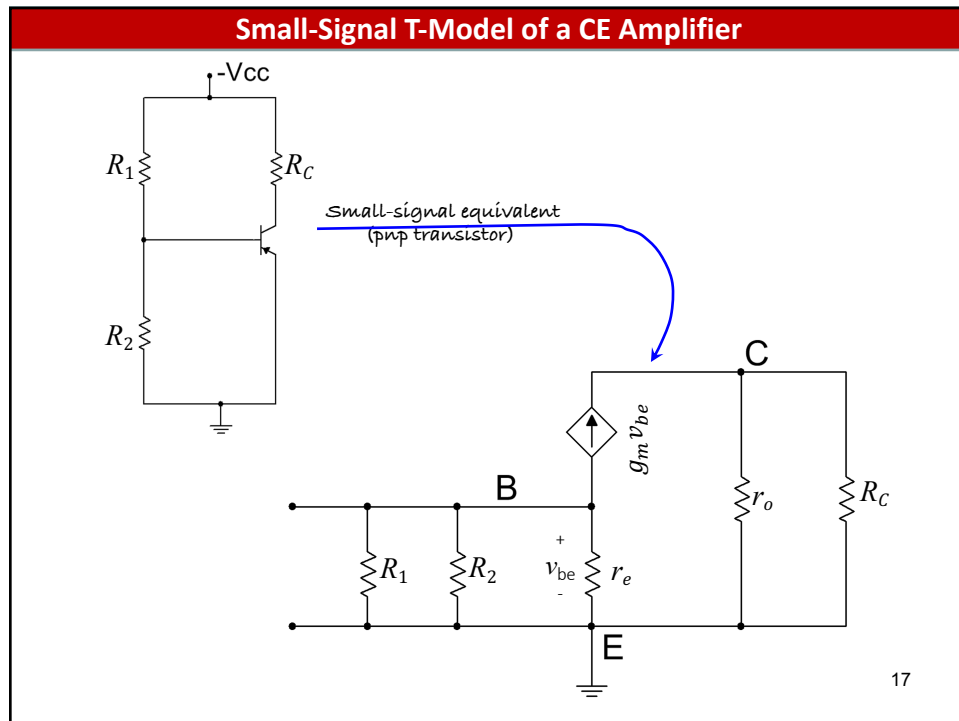


17

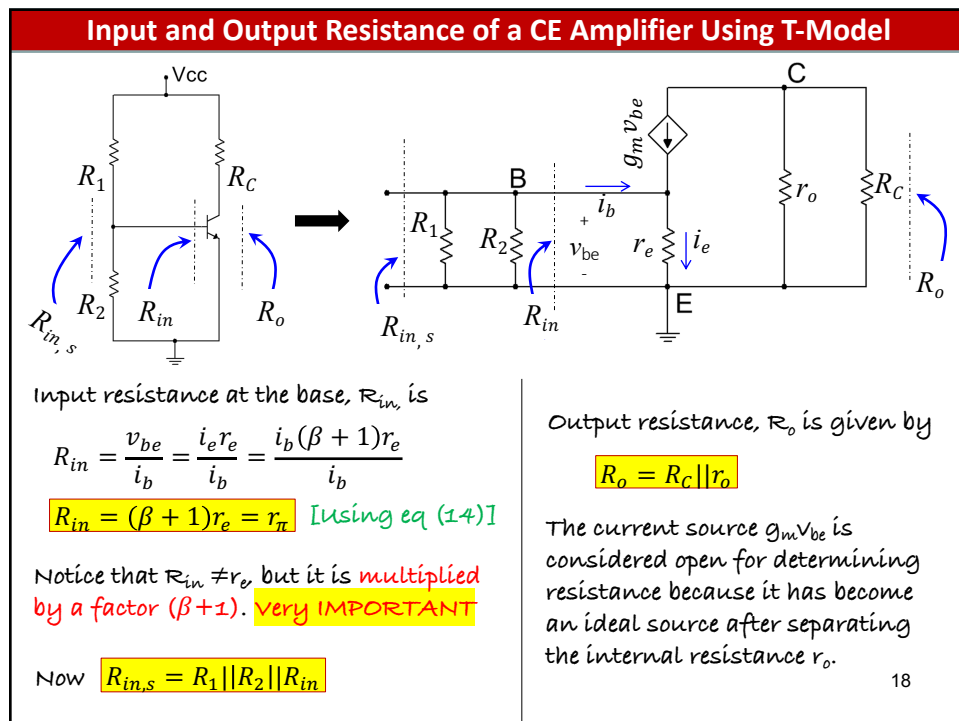

18

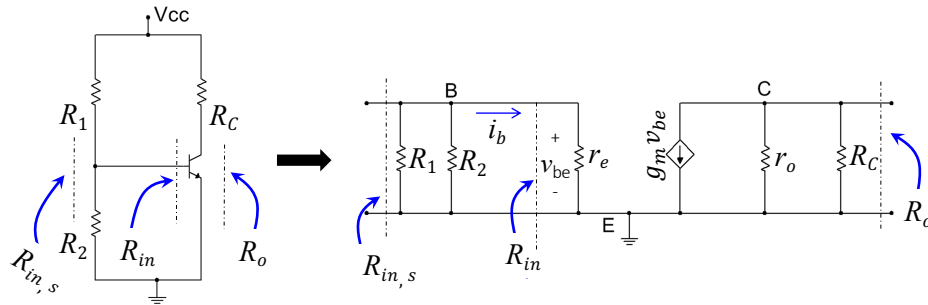Input and Output Resistance of a CE Amplifier Using π -Model



Input resistance at the base, R_{in} , is

$$R_{in} = \frac{v_{be}}{i_b} = \frac{i_b r_e}{i_b} \quad \text{or,} \quad R_{in} = r_{\pi}$$

Now $R_{in,s} = R_1 || R_2 || R_{in}$

Output resistance, R_o is given by

$$R_o = R_C || r_o$$

The current source $g_m v_{be}$ is considered open for determining resistance because it has become an ideal source after separating the internal resistance r_o .

Note that the π -model and T-model produce the same result

19