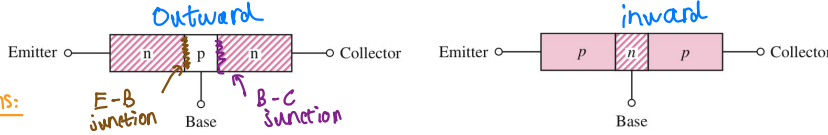


used in amplification of weak signals and switching operations

3 terminals


Bipolar Junction Transistor (BJT) Symbols

- Many people believe that the name Transistor came from: **Transfer of Resistor = Transistor.**
- Yes, it can transfer resistance, as we will see later in this course.



2 Regions:

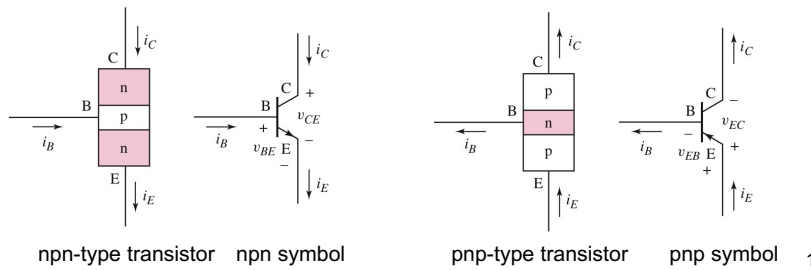- BJT is a 3-terminal device, where the **Emitter** emits charge carriers, the **Collector** collects them, and the **Base** controls the flow.



- collector is largest region
- smallest region is base

width:


$$C > E > B$$

Doping:

$$E > C > B$$


largest width cuz it has to collect electrons and heat is produced in it

EBC

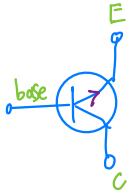

n p n

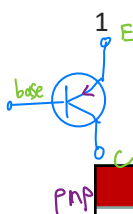- electrons move from E to B. So current is B to E




p n p

- electrons move from n to p. So B to E. = current is E to B

- one junction is forward biased while the other is reverse biased


BJT Working Principle

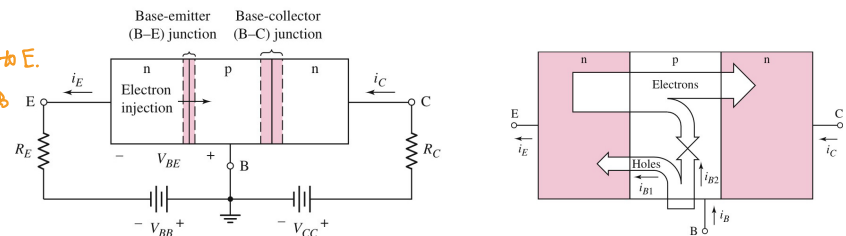

- Normally, the **B-E junction is forward biased**, and the **B-C junction is reverse biased**. We'll learn other cases later in this course.
- Emitter and collector are highly doped, but the base is lightly doped
- Emitter emits/injects electrons into base region
- The **base recombines only less than 1-2% of the emitted electrons**
- Rest of the emitted electrons in base can easily cross the B-C junction if a positive potential (reverse bias) is applied at the collector (why?)**
- Thus, the collector **collects the excess electrons from the base**
- Analyze this on your own for a pnp transistor

- plenty of questions in quizzes from class discussions

- leakage current

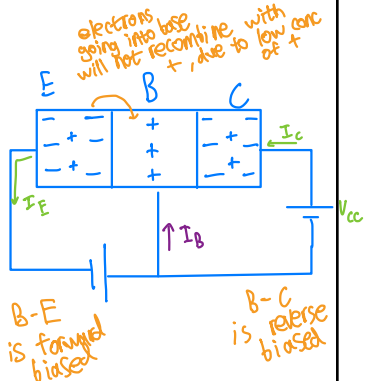


electrons going into base will not recombine with +, due to low conc of +

B-E is forward biased

B-C is reverse biased


usually is much smaller compared to IC

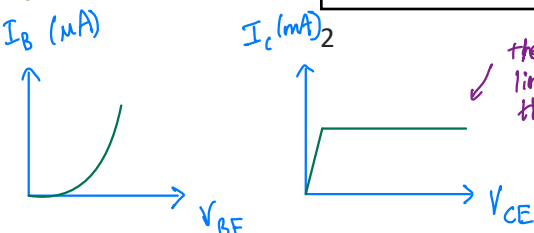


there is a limit, since there is a limited amount of electrons coming from emitter

there is some minority due to heat, electron-hole generation

eg minority

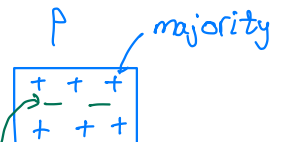

EB is fwd biased
BC is rev biased

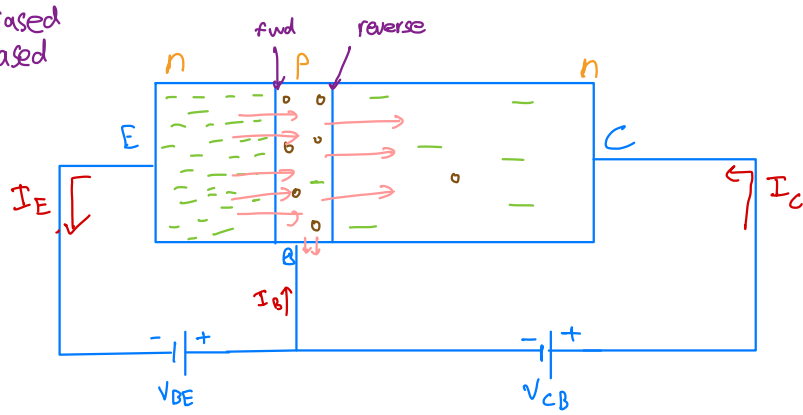


$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

looking at barrier potentials

V_b = barrier potential with no bias

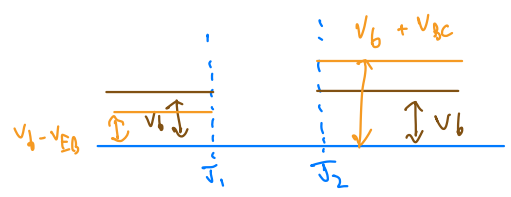

for EB

- depletion width became smaller
- electrons on n-side will cross and combine with holes in base

* Note that base is small and lightly doped
∴ therefore there is small recombination that occurs in base.
Most electrons go into collector

for CB

- there is reverse saturation current from minority charge carriers combining

← leakage

??

$$I_C = \alpha I_E + I_{CO}$$

using KCL

$$I_E = I_B + I_C$$

for npn:

- base has +ve V with respect to emitter
- collector has +ve V with respect to base

I think rule is when p is +ve wrt n then it's fwd

≈ n is -ve wrt +

4 possible ways of biasing BJT:


9/14/20

J_1	J_2	Region of operation
f.b.	r.b.	Active \rightarrow amplifier
f.b.	f.b.	Saturation \rightarrow "ON"
r.b.	r.b.	Cutoff \rightarrow "off"
r.b.	f.b.	inverted

↑ rarely used
- E and B switch roles

In active mode:

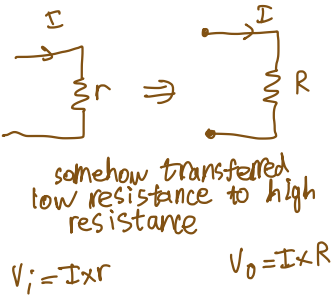$J_1 \rightarrow$ f.b. then resistance is 0 when on and ∞ when off
 $J_2 \rightarrow$ r.b.



$V_i < V_o$
had weak signal at input now we have large at output \therefore amplification

Current Relationship


nnp-type transistor nnp symbol

pnp-type transistor pnp symbol

By KCL for nnp transistor,
 $i_E - i_C - i_B = 0$
 or, $i_E = i_C + i_B$

By KCL for pnp transistor,
 $-i_E + i_C + i_B = 0$
 or, $i_E = i_C + i_B$

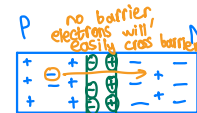Do NOT forget this
 This is valid regardless
 current equation remains the same



-the charges in depletion region determine direction of electric field

Current Relationship

Common-base* current gain $\alpha = \frac{i_C}{i_E}$

Common-emitter* current gain $\beta = \frac{i_C}{i_B}$

*we will learn common-base and common-emitter later in this course

- The value of α cannot be higher than one ↗ due to equations next page
- The value of α is approximately equal to 1 i.e., ($\alpha \approx 1$)
- The value of β can widely vary. Examples: $\beta = 20, \beta = 75, \beta = 112, \beta = 165, \beta = 200$
- α and β have no units
- α and β are inherent properties, available in transistor datasheet
- α and β must be related to each other

typical β value is usually high. Many more electrons cross while only 1 recombines

$$I_C < I_E$$

α is usually 0.99

Current Relationship

Recall, $I_E = I_C + I_B$
 using this equation and the definitions of α & β ,
 one can easily derive the following relationships

$$I_E = I_C + I_B$$

$$\frac{I_E}{I_B} = \frac{I_C}{I_B} + \frac{I_B}{I_B}$$

$$\frac{I_E}{I_B} = \beta + 1$$

$I_E = I_B(\beta + 1)$

$$\alpha = \frac{I_C}{I_E}$$

$$\alpha = \frac{I_C/I_B}{I_E/I_B}$$

$\alpha = \frac{\beta}{\beta + 1}$

$$\beta = \frac{I_C}{I_E - I_C}$$

$$\beta = \frac{I_C/I_E}{I_E/I_E - I_C/I_E}$$

$\beta = \frac{\alpha}{1 - \alpha}$

relates emitter and base currents

relate α and β

** V.I.P
 - will not be given in formula sheet
 - need to memorise


5

5

To remember
NPN and PNP


Voltage Relationship

2 in 1 out

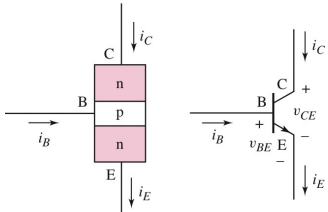

nnp-type transistor nnp symbol

1 in 2 out

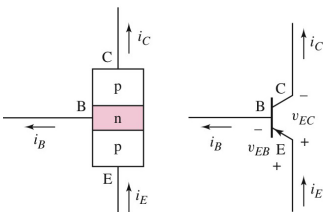

pnp-type transistor pnp symbol

how is KVL used?
I don't see it

By KVL for nnp transistor,
 $-V_{BE} - V_{CB} + V_{CE} = 0$
 or, $V_{CB} = V_{CE} - V_{BE}$

By KVL for pnp transistor,
 $V_{EB} - V_{CB} - V_{EC} = 0$
 or, $V_{CB} = -V_{EC} + V_{EB}$
 or, $V_{CB} = V_{CE} - V_{BE}$

Do NOT memorize this


This is valid regardless

6

6

NPN

Voltage Relationship: Example

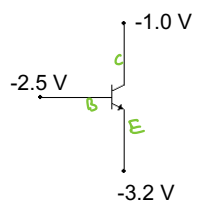

$V_B - V_E = -2.5 - (-3.2) = 0.7$
 $V_C - V_B = -1 - (-2.5) = 1.5$

Example: Consider the npn transistor with given voltages. Determine the type of biasing applied to B-E and C-B junctions of this transistor.

Soln: Here $V_{BE} = V_B - V_E$
 or, $V_{BE} = -2.5 - (-3.2) = 0.7 \text{ V}$

Since the base has a positive voltage with respect to emitter, the B-E junction of this npn transistor is forward biased.

Again, $V_{CB} = V_C - V_B$
 or, $V_{CB} = -1 - (-2.5) = V_{CB} = 1.5 \text{ V}$

Since the collector has a positive voltage with respect to base, the C-B junction of this npn transistor is reverse biased.

Notes:

- Notice that the collector base junction is reverse biased although the n-type collector has a negative voltage applied to it
- The biasing depends on voltage difference across the junction


7

∴ Therefore transistor is properly biased

7

PNP

Voltage Relationship: Example

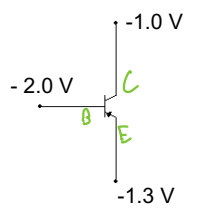

Example: Consider the given transistor. Determine the type of biasing applied to B-E and C-B junctions of this transistor.

Soln: Here $V_{BE} = V_B - V_E$
 or, $V_{BE} = -2 - (-1.3) = -0.7 \text{ V}$

Since the base has a negative voltage with respect to emitter, the B-E junction of this pnp transistor is forward biased.

Again, $V_{CB} = V_C - V_B$
 or, $V_{CB} = -1 - (-2) = V_{CB} = 1 \text{ V}$

Since the collector has a positive voltage with respect to base, the C-B junction of this pnp transistor is forward biased.

Notes:

- Notice that the collector base junction is forward biased although the p-type collector has a negative voltage applied to it
- The biasing depends on voltage difference across the junction

8

both forward biased
so transistor won't work

8

Collector Current

We know, $i_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)}$

Also, $i_B = \frac{1}{\beta} I_S e^{\left(\frac{V_{BE}}{V_T}\right)}$

Also, $i_E = \frac{1}{\alpha} I_S e^{\left(\frac{V_{BE}}{V_T}\right)}$

Where,

I_S = Saturation current or scale current

V_T = Thermal voltage = (kT/q)

k = Boltzmann's constant

$k = 1.38 \times 10^{-23} \text{ J/K}$

T = Temperature in $^{\circ}\text{K}$

q = electron charge = $1.6 \times 10^{-19} \text{ C}$

Thus, at 20°C $V_T = 25.27 \text{ mV}$

Use $V_T = 25 \text{ mV}$ in this course

Notes:

- Above equations are for npn transistors
- Use V_{EB} instead of V_{BE} for pnp transistors
- Collector current (also I_B and I_E) depends on temperature
- $|V_{BE}|$ controls collector current and other currents
- Scale current is an inherent parameter of a transistor
- I_S is typically in the order of 10^{-12} to 10^{-15} A

9

why??

this is also the drift current, from min carriers, right?

-never used this equation in assignments or quiz

where do these equations come from?

Do I just need to memorize as is?

9

Collector Current Examples

Example: A transistor gives 4 mA of collector current at $V_{BE} = 0.72 \text{ V}$. Determine scale current I_S of the transistor.

Soln: $I_S = (0.004) / e^{(0.72/0.025)}$
 $I_S = 1.24 \times 10^{-15} \text{ A}$

$$I_S = \frac{I_C}{e^{\frac{V_{BE}}{V_T}}}$$

I_S = drift current, saturation, scale

Example: The saturation current of a transistor is given $I_S = 2.1 \times 10^{-13} \text{ A}$. What base-emitter voltage is required to generate 2.5 mA of collector current?

Soln: $\ln\left(\frac{i_C}{I_S}\right) = \frac{V_{BE}}{V_T}$

or, $V_{BE} = V_T \ln\left(\frac{i_C}{I_S}\right) = 0.58 \text{ V}$

10

just rearranging of equation

10

Collector Current Example

Example: Given that a transistor with $\beta = 150$ has a base current of $15 \mu\text{A}$. Determine a) collector current i_C , b) emitter current i_E , and c) the common-base current gain α .

Soln:

a) We know, $i_C = \beta i_B = 150 \times 15 \times 10^{-6}$
or, $i_C = 2.25 \text{ mA}$

b) We know, $i_E = i_C + i_B$
or, $i_E = 2.25 \times 10^{-3} + 15 \times 10^{-6}$
or, $i_E = 2.265 \text{ mA}$

Also, $i_E = (\beta + 1)i_B$
or, $i_E = 151 \times 15 \times 10^{-6}$
or, $i_E = 2.265 \text{ mA}$

c) We know, $\alpha = \beta / (\beta + 1)$
or, $\alpha = 150/151$
or, $\alpha = 0.9934$

verify: $\beta = \alpha / (\alpha - 1)$
 $\beta = 150.5$ (0.3% error)
if we take $\alpha = 0.993$,
 $\beta = 141.9$ (5.4% error)

if we take $\alpha = 0.99$,
 $\beta = 99.0$ (51.5% error)

It is not just the math, you need to fully understand how your design is changing.

11

rearrange equations and plug numbers

-need to understand that if it's +ve or -ve, what it means in circuit

I don't quite understand this point

11

Transistor Characteristics: Base-Emitter


- This is the same as a diode
- Note the slope changes from infinite to almost zero
- What happens if the voltage is increased to 0.8 or higher? For this particular graph with $I_S = 5 \times 10^{-15} \text{ A}$ and $\beta = 150$, we'll have:

$$I_E = 24.7 \mu\text{A} \text{ at } V_{BE} = 0.8 \text{ V}$$

$$I_E = 0.135 \text{ A} \text{ at } V_{BE} = 0.9 \text{ V}$$

$$I_E = 7.356 \text{ A} \text{ at } V_{BE} = 1.0 \text{ V}$$

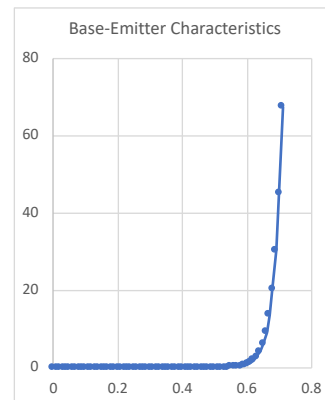- V_{BE} decreases by 2 mV for temperature rise of 1°C
- Consider $V_{BE(on)} = 0.7 \text{ V}$ throughout this course




exponential increase

12

12

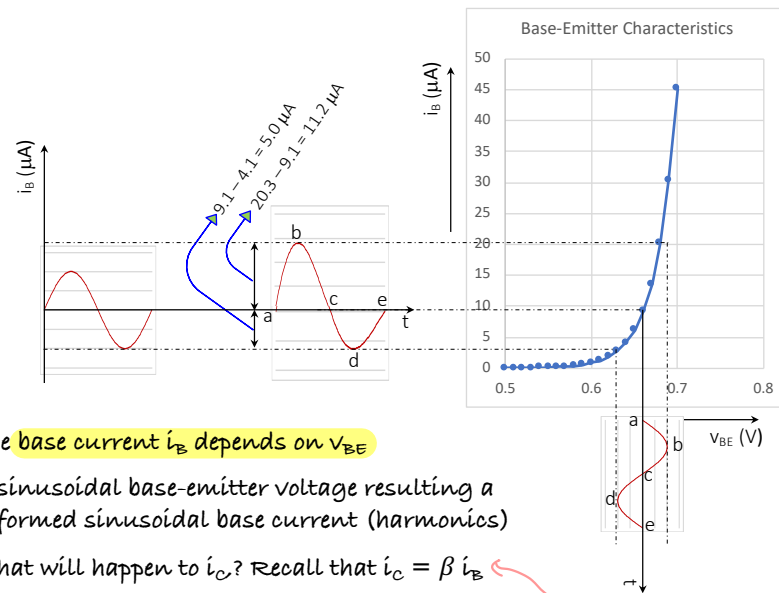Effect of Nonlinearity in Base-Emitter Characteristic



- The base current i_B depends on v_{BE}
- A sinusoidal base-emitter voltage resulting a deformed sinusoidal base current (harmonics)
- What will happen to i_C ? Recall that $i_C = \beta i_B$
- Select linear region by applying small signal


13

it will also exponentially increase

13

Transistor Characteristics: Collector-Emitter

- Ideally, all curves should be horizontal in the active region
- Why does the current increase so rapidly (\approx zero slope)? (homework)
- Why does the current become almost constant after a fraction of voltage (\approx infinite slope)? (homework)
- Notice that in practice the slope decreases with the increase of i_B
- How much current can you expect at $i_B = 0$? What is the source of the current at $i_B = 0$?
- What happens at very large $|v_{CE}|$?
- What is the effect of temperature?

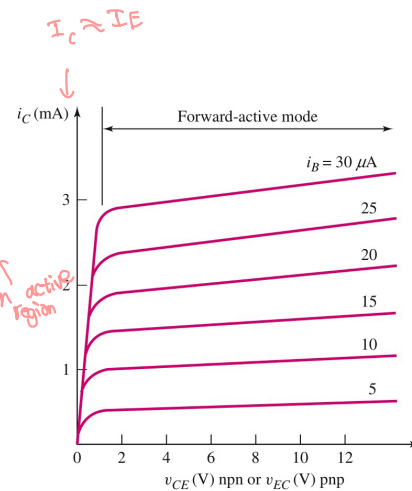

14

14