

Lab#4 – The Differential Amplifier

Student's Name: Omar Ahmed

The goal of this exercise is to analyze the differential amplifier circuit.

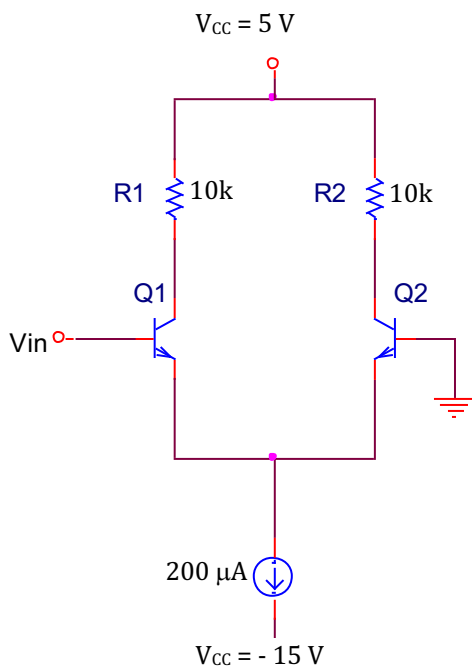


Figure 1(a)


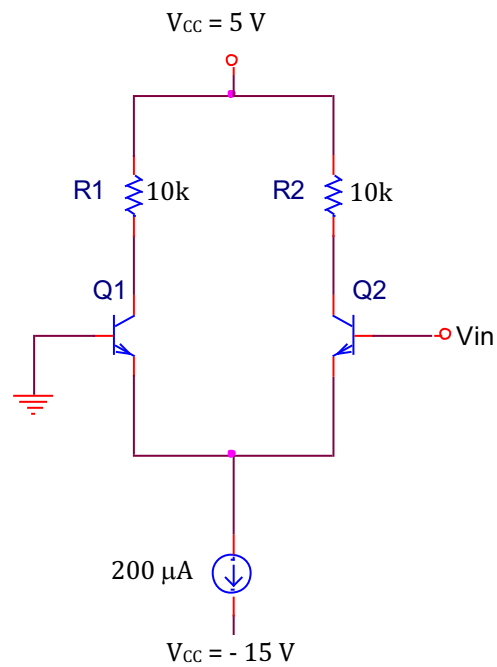


Figure 1(b)

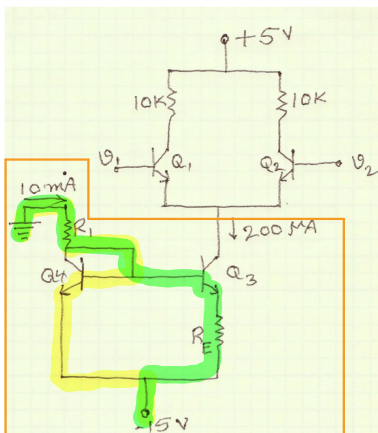

$$I_O R_E = V_T \ln \left(\frac{I_{REF}}{I_O} \right)$$

$$R_E = \frac{V_T \ln \left(\frac{I_{REF}}{I_O} \right)}{I_O}$$

$$R_E = \frac{25 \times 10^{-3} \ln \left(\frac{10 \text{ mA}}{200 \mu\text{A}} \right)}{200 \mu\text{A}}$$

$$R_E = 489 \Omega$$

widlar
current
source

$$0 - (10 \text{ mA} \cdot R_1) - 0.7 - (-15) = 0$$

$$10 \text{ mA} \cdot R_1 = 14.3$$

$$R_1 = \frac{14.3}{10 \text{ mA}} = 1430 \Omega$$

$$0 - (10 \text{ mA} \cdot R_1) - 0.7 - (-15) = 0$$

$$10 \text{ mA} \cdot R_1 = 14.3$$

$$R_1 = 1430 \Omega$$

Can't do KVL here

Part-1: Basic Operation of a Differential Pair

- a) Implement the circuit shown in figure 1(a). Implement the current source as shown in figure 4. Apply a dc voltage at the base of Q1. Measure currents and voltages as required in table-1. R1 and R2 must be measured by a meter (**NOT** the colour code value).

Table-1

	Measurement for Q1				Measurement for Q2				
V _{in} (V)	R ₁ (Ω) (Actual)	V _{R1} (V)	I _{C1} = V _{R1} /R ₁ (mA)	Status On/Off	R ₂ (Ω) (Actual)	V _{R2} (V)	I _{C2} = V _{R1} /R ₁ (mA)	Status On/Off	V _E (V)
0 (B1 grounded)									
0.1									
2.0									
- 2.0									

- b) Implement the circuit shown in figure 1(b). Apply a dc voltage at the base of Q2. Measure currents and voltages as required in table-2. R1 and R2 must be measured by a meter (**NOT** the colour code value).

Table-2

	Measurement for Q1				Measurement for Q2				
V _{in} (V)	R ₁ (Ω) (Actual)	V _{R1} (V)	I _{C1} = V _{R1} /R ₁ (mA)	Status On/Off	R ₂ (Ω) (Actual)	V _{R2} (V)	I _{C2} = V _{R1} /R ₁ (mA)	Status On/Off	V _E (V)
0 (B2 grounded)									
0.1									
2.0									
-2.0									

Part-2: Common Mode Voltage

- a) Implement the circuit shown in figure 2. Apply a common-mode (dc) voltage as shown in the circuit. Measure currents and voltages as required in table-3 and table-4. R1 and R2 must be measured by a meter (**NOT** the colour code value). Record the correct polarity of V_{CB} . Determine the biasing of the CB junction.

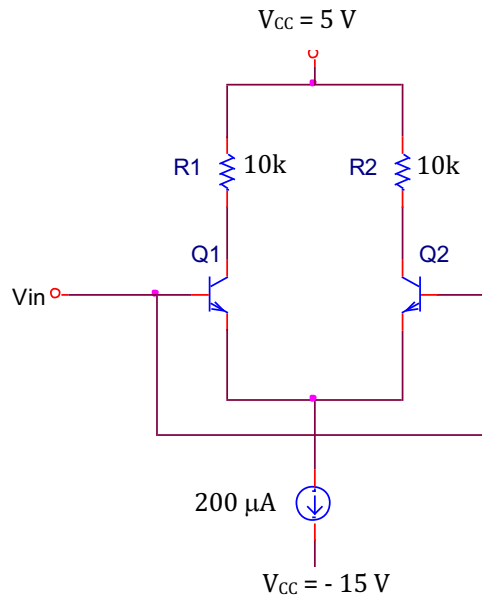


Figure 2

Table-3

V_{ICM} (V)	V_{C1} (V)	V_{C2} (V)	$V_0 =$ $V_{C1} - V_{C2}$ (V)	$I_{C1} =$ V_{R1}/R_1 (mA)	$I_{C2} =$ V_{R2}/R_2 (mA)	V_{CB1} (V)	V_{CB2} (V)
0							
1							
3							
4							
5							
6							

Table-4

V_{ICM} (V)	V_{C1} (V)	V_{C2} (V)	$V_0 =$ $V_{C1} - V_{C2}$ (V)	$I_{C1} =$ V_{R1}/R_1 (mA)	$I_{C2} =$ V_{R2}/R_2 (mA)	V_{CB1} (V)	V_{CB2} (V)
-2							
-4							
-6							
-8							
-12							
-14							
-15							

Determine the theoretical limits of the common-mode input voltage of this circuit.

Part-3: Differential Input Resistance

a) Implement the circuit shown in figure 3. Apply a differential input voltage of 150 mV (peak), as shown in the circuit. Measure the differential input resistance, and compare it with the calculated value of R_{id} .

b) Calculated R_{id} :

$$R_{id} = 2(\beta + 1)(r_e + R_e)$$

$$\text{Here, } r_e = (V_T)/(I_E)$$

$$R_e = 100 \Omega$$

Assume $\beta = 165$ (for 3904)

Calculation (using formula):

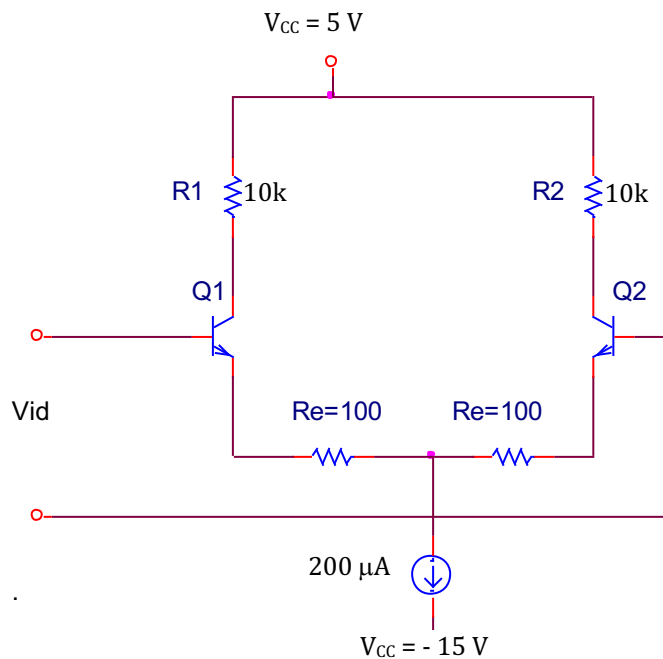


Figure 3

c) **Determination of R_{id} :**

$$R_{id} = v_{id}/i_{in}$$

Apply a signal voltage of $v_{id} = 20$ mV and $v_{id} = 400$ mV. Here, i_{in} can be measured by measuring the **AC voltage drop** across R_e and dividing the voltage by R_e (**Not** the colour code value).

The experimentally measured value of R_{id} :

For $v_{id} = 20$ mV

$v_{id} = 400$ mV

Implement the following circuit and repeat Table 1. Identify the differences.

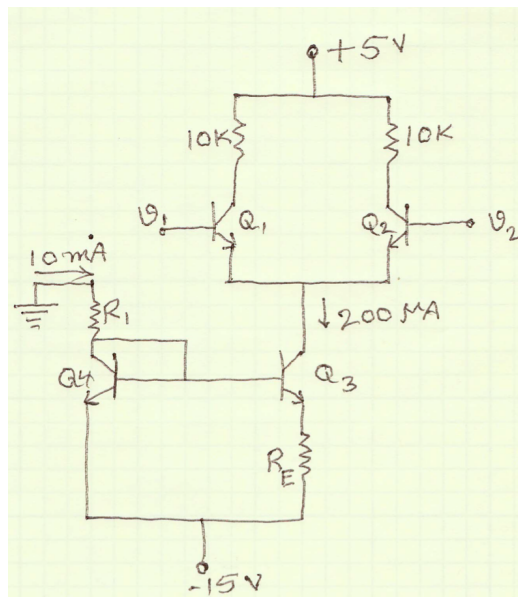


Figure 4