
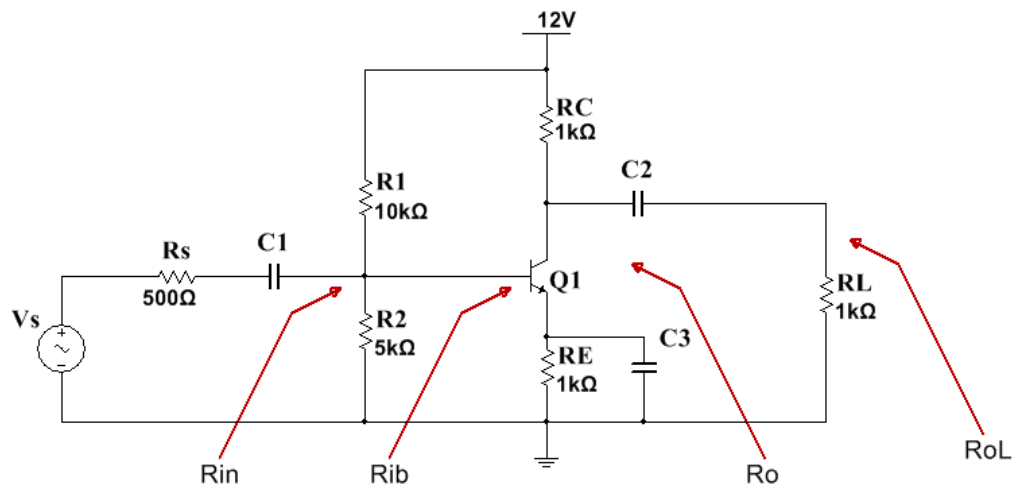


Assignment #2: Amplifier Circuits
ENEL469: Analog Electronics

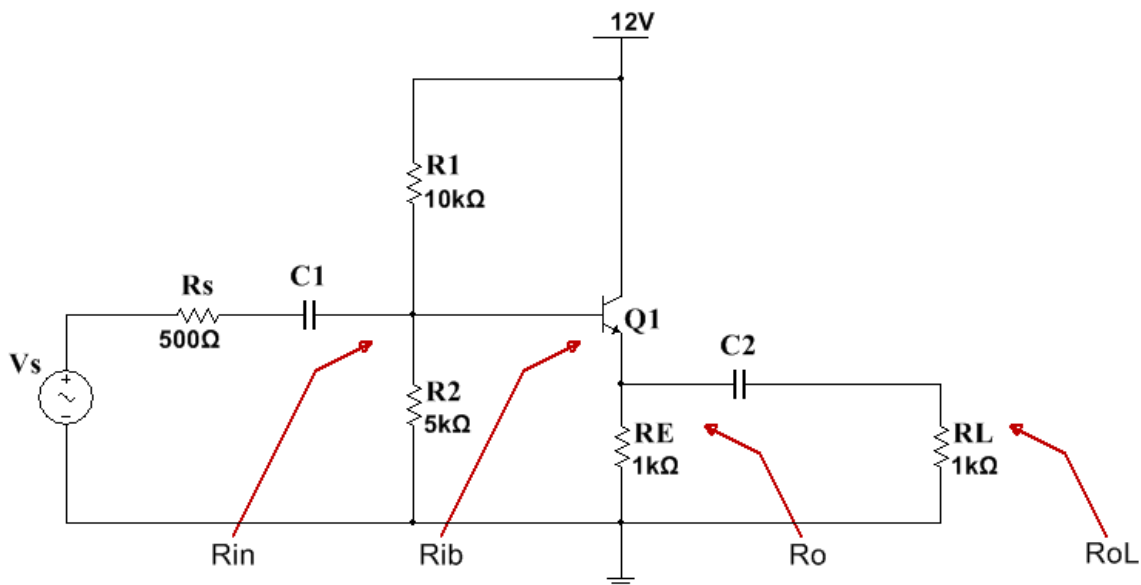
1. Consider the following common emitter amplifier circuit where $\beta = 70$, $V_{BE(ON)} = 0.7$ V, $V_A = 100$ V, $v_s = 10$ mV and $V_{CE(Sat)} = 0.2$ V. Determine: small-signal parameters (r_π , r_e , r_o and g_m), R_{in} , R_{ib} , R_o , R_{oL} , signal current in collector (i_c), signal voltage at collector (v_c). Use π model and do not ignore output resistance r_o . Assume that the capacitors are large enough for the signal frequency.



2. Consider the following common collector amplifier circuit where $\beta = 70$, $V_{BE(ON)} = 0.7$ V, $V_A = 100$ V, $v_s = 10$ mV and $V_{CE(Sat)} = 0.2$ V. Determine: the small-signal parameters (r_π , r_e , r_o and g_m), R_{in} , R_{ib} , R_o , R_{oL} , voltage across the load R_L . Use T model and do not ignore output resistance r_o . Assume that the capacitors are large enough for the signal frequency.



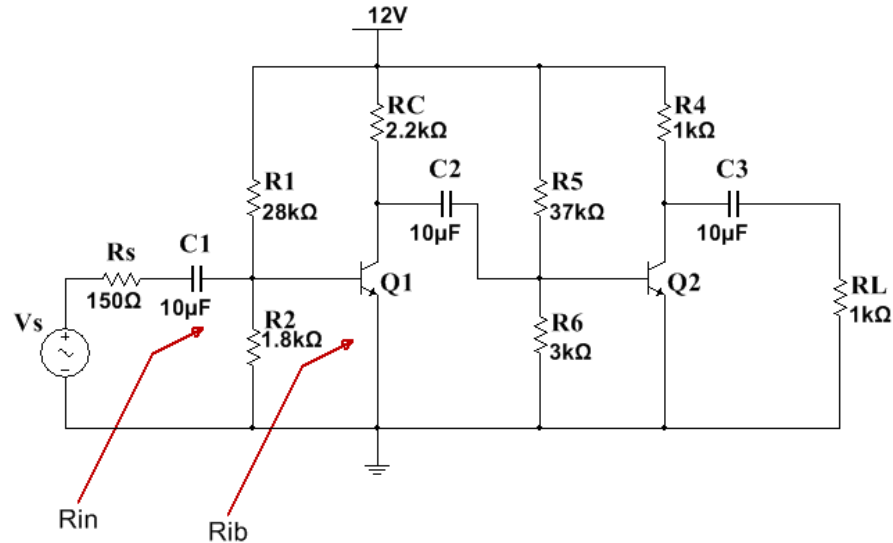3. Consider the following two-stage common emitter amplifier circuit where the transistors are identical. Given that $\beta = 70$, $V_{BE(ON)} = 0.7 \text{ V}$, $V_A = 100 \text{ V}$, $v_s = 10 \text{ mV}$ and $V_{CE(Sat)} = 0.2 \text{ V}$. Determine: small-signal parameters ($r_{\pi 1}$, $r_{\pi 2}$, r_{e1} , r_{e2} , r_{o1} , r_{o2} and g_{m1} , g_{m2}), R_{in} , R_{ib} , signal currents flowing in both collectors (i_{c1} , i_{c2}) signal voltage at both collectors (v_{c1} , v_{c2}). Do not ignore output resistance r_o . Assume that the capacitors are large enough for the signal frequency.



4. Consider the following two-stage amplifier circuit where the transistors are identical. Given that $\beta = 70$, $V_{BE(ON)} = 0.7 \text{ V}$, $V_A = 100 \text{ V}$, $v_s = 10 \text{ mV}$ and $V_{CE(Sat)} = 0.2 \text{ V}$. Determine: the voltage across load resistor R_L and output resistance R_{OL} as indicated in the circuit below. Do not ignore output resistance r_o . Assume that the capacitors are large enough for the signal frequency.

