
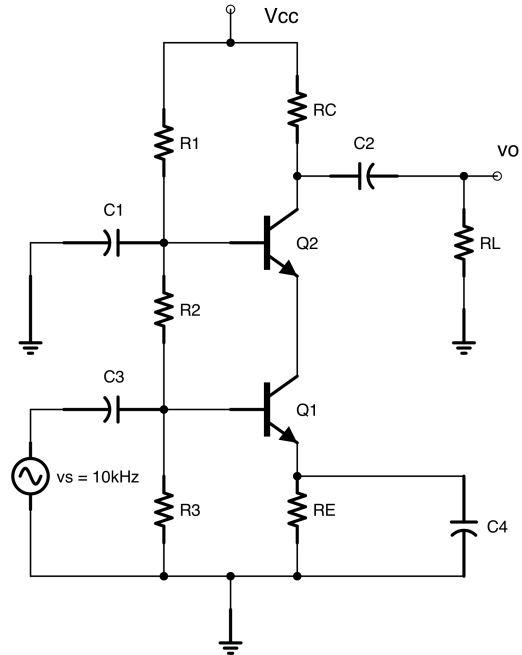


Practice Problem Set #4
 Small-signal equivalent circuit
 ENEL469: Analog Electronics

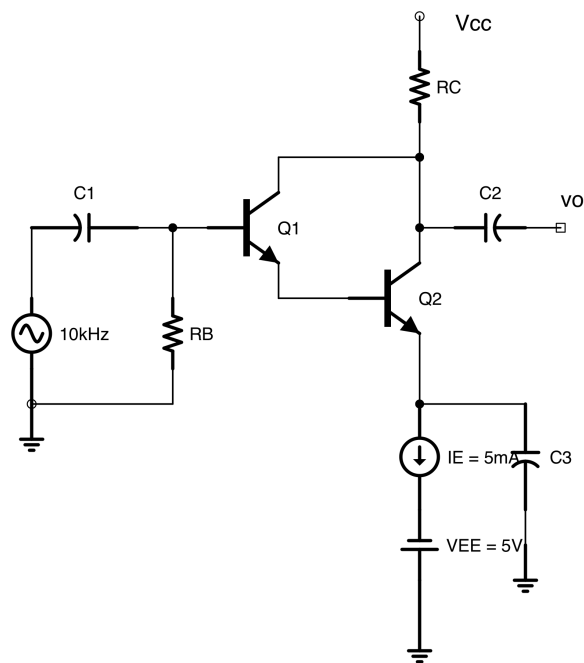1. Draw the small-signal π model of the following circuit.



2. Draw the small-signal π model of the following circuit.



3. Try to draw the small-signal T models for both circuits on your own. Solution to this part is not available