

ENEL 469: Analog Electronic Circuits

Quiz-1, Fall 2023

Total marks: 28; Time: 11:00 am – 12:30 pm

ID (Optional)	First Name (PRINT)	Last Name (PRINT)


1. [Total 10] Circle True or False for the following statements.

- a) [2] The following temperature relationship satisfies the given IV characteristic curves.

$$T_2 > T_1 > T_0$$

Answer: True

False

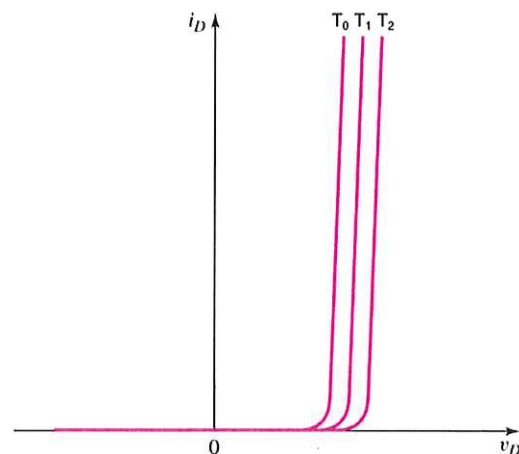

- b) [2] The direction of the electric field due to the depletion region changes when the biasing across the diode junction changes from forward to reverse or vice versa.


Answer: True

False

- c) [2] For the transistor biasing shown below, the E-B junction is forward-biased, and the C-B junction is reverse-biased.

Answer: True

False

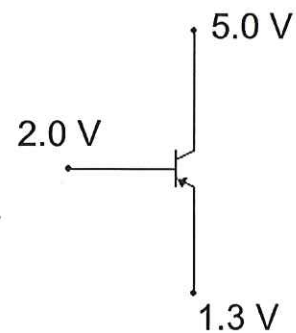

- d) [2] For an npn transistor, the holes in the base region can easily cross the collector-base (C-B) junction despite the reverse bias applied to the C-B junction.

Answer: True

False

- e) [2] For a pnp transistor, the collector current is slightly higher than the emitter current.

Answer: True

False

2. [3] The base-emitter junction of a pnp transistor is reversed biased by 2.0 V, and the common-emitter current gain β of the transistor is 80. Determine the collector current I_C of the transistor in mA. Ignore all leakage currents in your calculation.

Ans: $I_C = 0$ mA

3. [Total 5] Consider the following circuit, where $V_{CC} = 12\text{ V}$, $V_{CE} = 6\text{ V}$, $R_C = 1.5\text{ k}\Omega$, $\beta = 110$, $V_{BE(\text{on})} = 0.7\text{ V}$, $V_{SE(\text{Sat})} = 0.2\text{ V}$ and $I_2 = 80\text{ }\mu\text{A}$. Determine the value of the resistor R_1 in $\text{k}\Omega$.

Soln:

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$


$$I_C = 4\text{ mA}$$

$$I_B = \frac{I_C}{\beta} = 36.4\text{ }\mu\text{A}$$

Thus, $I_1 = I_B + I_2 = 116.4\text{ }\mu\text{A}$

$$R_1 = \frac{V_{CC} - 0.7}{I_1}$$


$$\boxed{R_1 = 97.1\text{ k}\Omega}$$

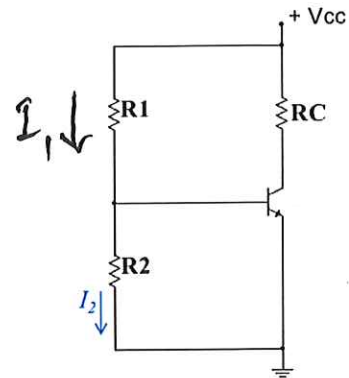

Ans: $R_1 = 97.1\text{ k}\Omega$

4. [Total 10] Consider the given circuit. Given, $V_{BE(on)} = 0.7V$, $\beta = 52$, $V_{CC} = 14V$, $R_C = 2\text{ k}\Omega$, and $R_B = 175\text{ k}\Omega$.

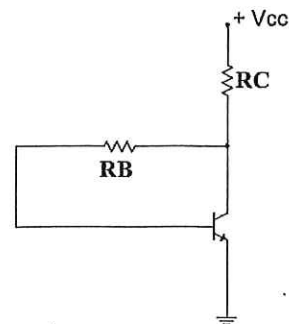a) [4] Determine the collector current I_C in mA for the given circuit. Do not consider $I_C = I_E$



$$V_{CC} = I_E R_C + I_B R_B + V_{BE(on)}$$

$$\text{or, } I_B = \frac{V_{CC} - 0.7}{R_B + (\beta + 1)R_C}$$

$$I_B = 47.3\text{ }\mu\text{A}$$

$$\text{Thus, } I_C = 2.46\text{ mA}$$

$$\text{Ans: } I_C = 2.46\text{ mA}$$

b) [3] The collector-emitter voltage V_{CE} .

$$\begin{aligned} V_{CE} &= V_{CC} - I_E R_C \\ &= 8.99\text{ V} \end{aligned}$$

$$\text{Ans: } V_{CE} = 8.99\text{ V}$$

c) [2] The collector-base voltage V_{CB} .

$$V_{CB} = V_{CE} - 0.7$$

$$\text{Ans: } V_{CB} = 8.29\text{ V}$$