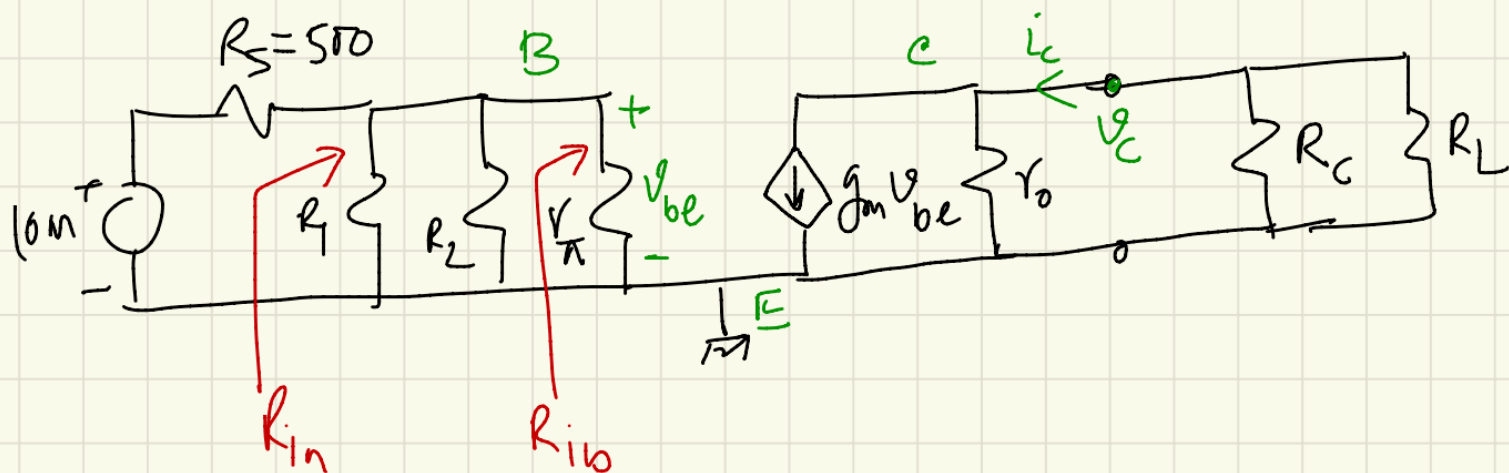


# Problem 1

DC analysis will be same as problem 5.

## Small Signal Model:



$$\text{Now, } r_{ib} = r_{\pi} = 5631 \Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel r_{\pi} \\ = 481.6 \Omega$$

$$r_o = \frac{V_A}{I_C} = 32.15 \text{ k}\Omega$$

$$g_m = I_C / V_T = 129.4 \text{ mA/V}$$

$$\therefore v_{be} = V_s R_{in} / (R_s + R_{in}) = 4.91 \text{ mV}$$


$$\therefore v_c = -g_m v_{be} (r_o \parallel R_C \parallel R_L)$$

$$= -129.4 \times 10^{-3} \times 4.91 \times 10^{-3} \times 492.34$$


$$v_c = -300.7 \text{ mV}$$

$$i_c = v_c / (R_C \parallel R_L) = 601.4 \mu\text{A}$$

## Problem 2

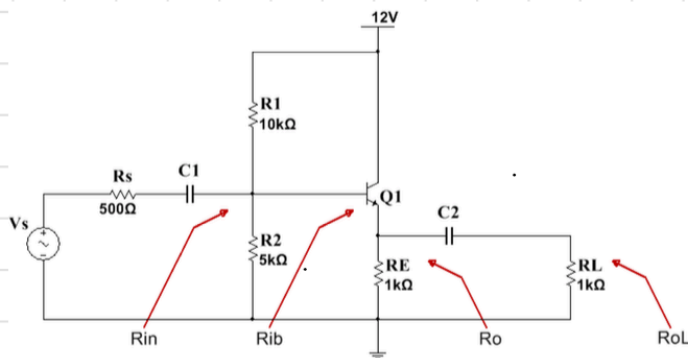

DC Equivalent Circuit:

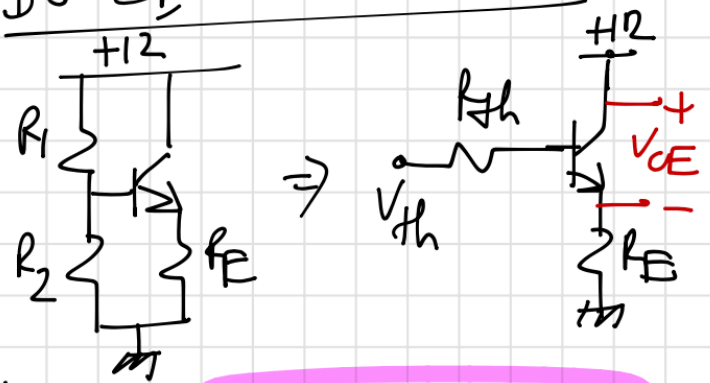

$$R_{th} = R_1 \parallel R_2 = 3.33k$$

$$V_{th} = \frac{R_2}{R_1 + R_2} V = 4V$$

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$\Rightarrow I_E = 3.1522 \text{ mA}$$

$$\therefore I_C = \frac{\beta}{\beta + 1} I_E = 3.1078 \text{ mA}$$


$$V_{CE} = 12 - I_E R_E = 8.8478 \text{ V}$$

$$g_m = \frac{I_C}{V_T} \approx 124.312 \text{ mA/V}$$


$$r_e = \frac{V_T}{I_E} \approx 7.981 \Omega$$

$$r_{\pi} = \frac{V_T}{I_B} \approx 563 \Omega$$


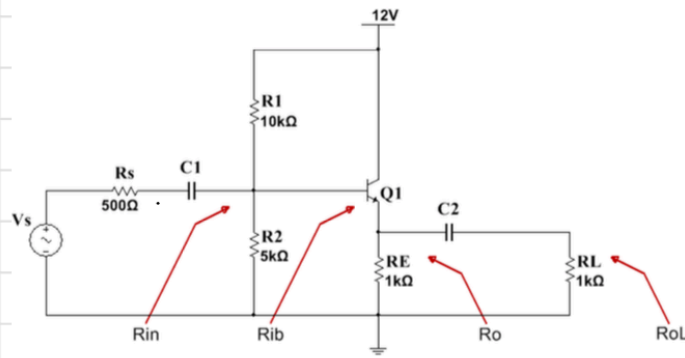
$$r_o = \frac{V_A}{I_C} \approx 32.18 \Omega$$



AC Equivalent circuit:

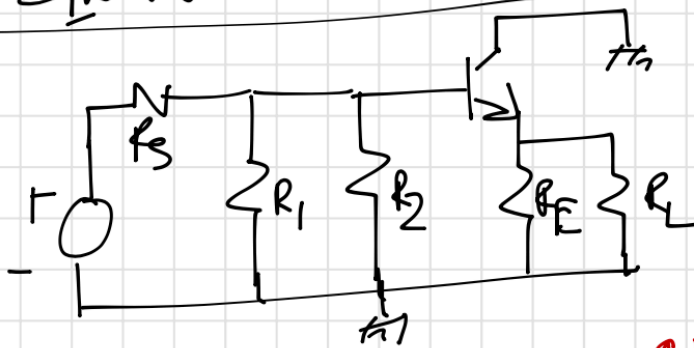

⇒

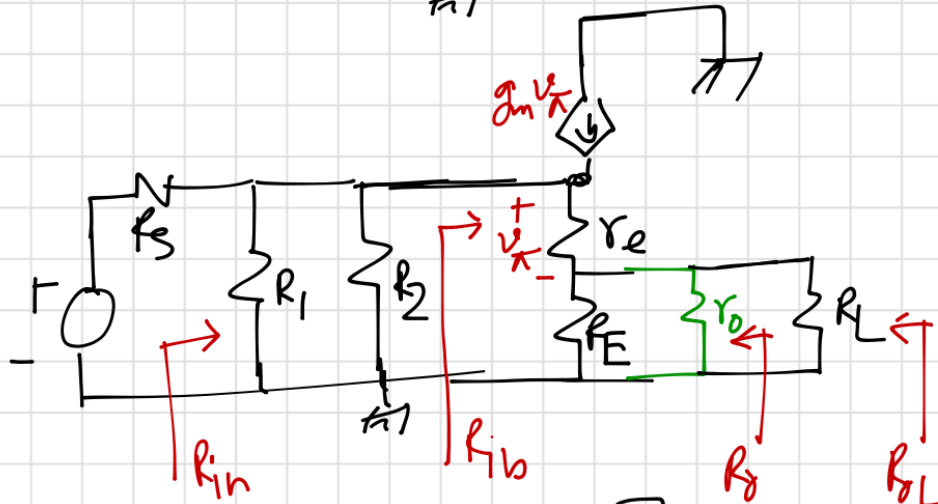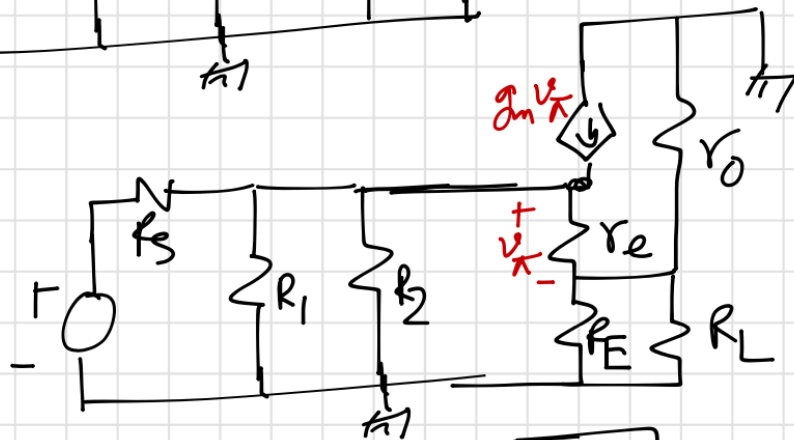


⇒

$$R_{ib} = (\beta + 1) [r_e + (R_E \parallel r_o \parallel R_L)]$$

$$\approx 36 \text{ k}\Omega$$
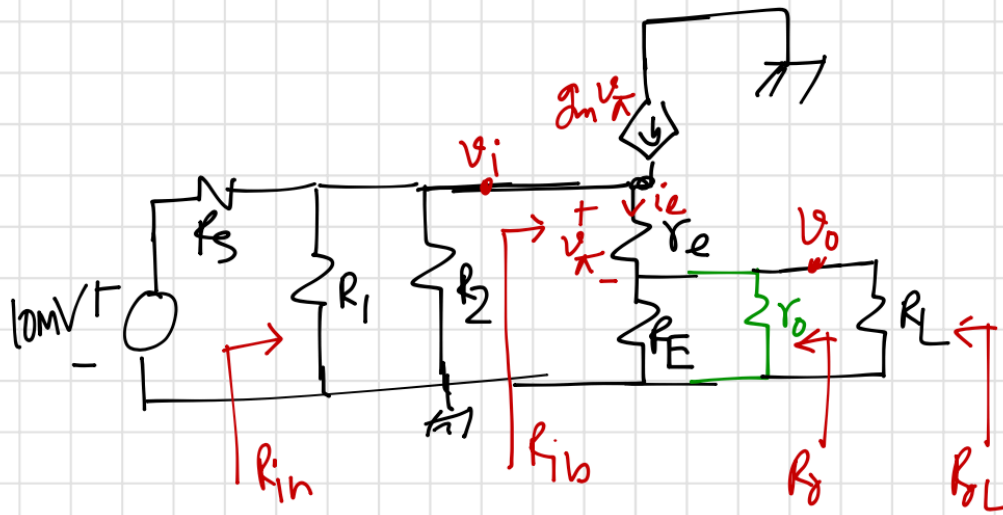
$$R_{in} = R_1 \parallel R_2 \parallel R_{ib} = 3.0738 \text{ k}\Omega$$



$$R_o = r_o \parallel R_E \parallel \left[ r_e + \frac{(R_1 \parallel R_2 \parallel R_3)}{(\beta + 1)} \right]$$

$$\approx r_e + \frac{(R_1 \parallel R_2 \parallel R_3)}{(\beta + 1)}$$

$$\approx 14 \Omega$$

$$R_{oL} = R_o \parallel R_L = 13.8 \Omega$$

$$v_i = v_{sig} \frac{R_{in}}{R_{sig} + R_{in}} = 8.6945 \text{ mV}$$


$$i_e = \frac{v_i}{r_e + R_E \parallel R_o \parallel R_L} = 17.38 \mu\text{A}$$

$$v_o = i_e (R_E \parallel R_o \parallel R_L) = 8.55 \text{ mV}$$

### Problem 3

For the first stage, DC analysis and small signal parameters are same as before.

# For the second stage:

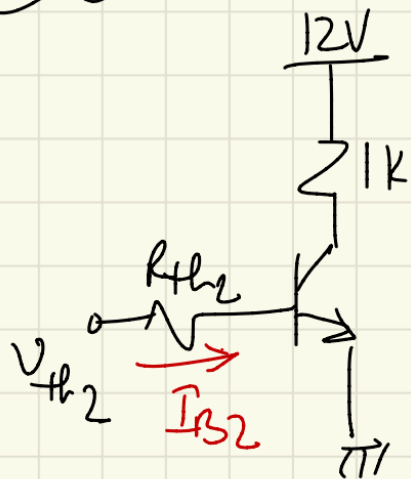

$$R_{th2} = R_5 \parallel R_6 = 2.775 k\Omega$$

$$V_{th2} = \frac{R_6}{R_5 + R_6} \cdot 12 = 0.9V$$

$$\therefore I_{B2} = \frac{0.9 - 0.7}{R_{th2}} = 72.1 \mu A$$

$$I_{C2} = 5.047 mA$$

$$I_{E2} = 5.12 mA$$


$$g_{m2} = \frac{I_{C2}}{V_T} = 201.88 mA/V$$

$$r_{e2} = \frac{V_T}{I_{E2}} = 4.88 \Omega$$

$$r_{\pi 2} = \frac{V_T}{I_{B2}} = 346.741 \Omega$$

$$r_{o2} = V_A / I_C = 19.81 k\Omega$$

# Small signal Model:

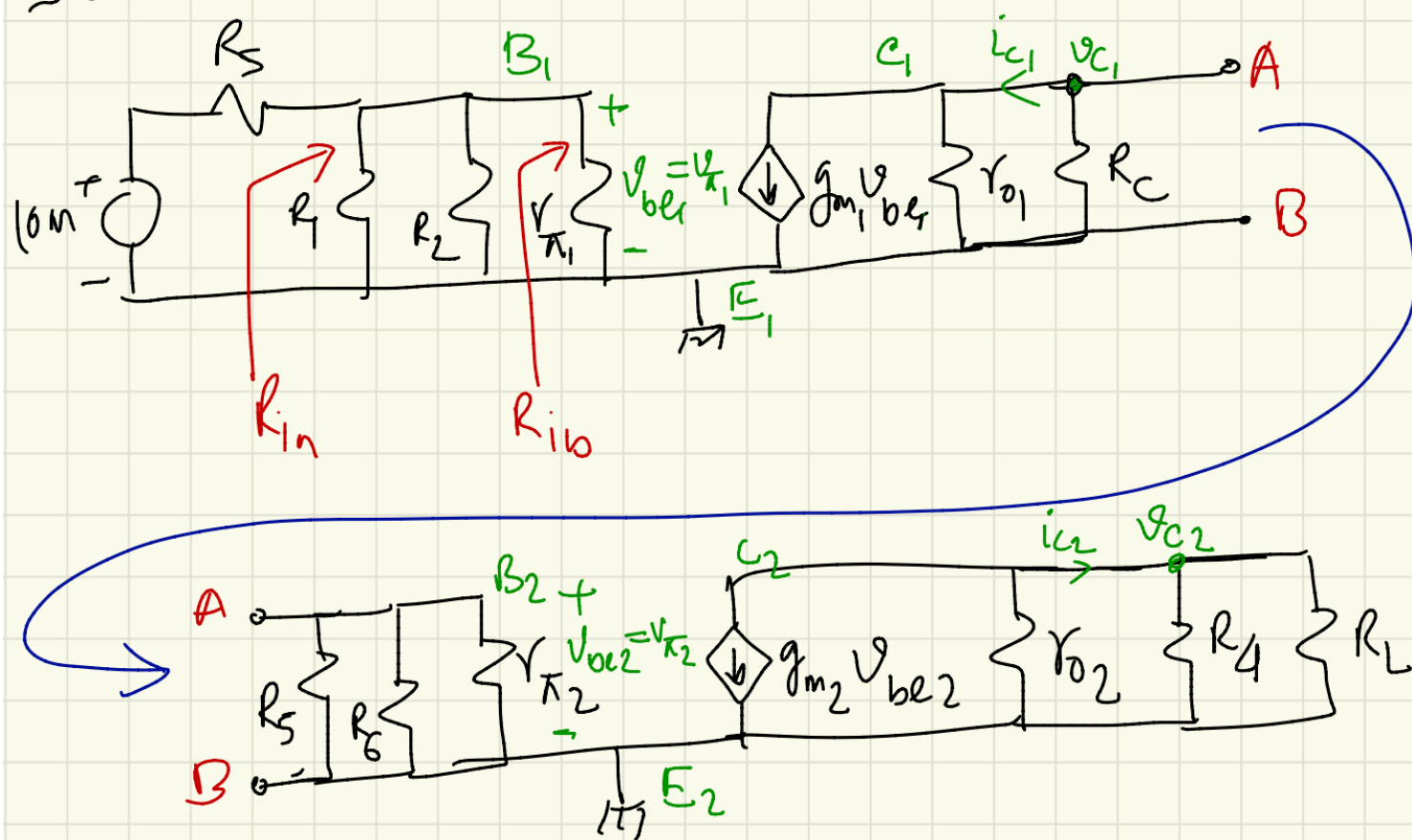

$$\therefore V_{c1} = -g_{m1} V_{be1} (R_{o1} \parallel R_C \parallel R_5 \parallel R_6 \parallel r_{\pi 2})$$

$$R_{o1} \parallel R_C \parallel R_5 \parallel R_6 \parallel r_{\pi 2} = 269.76 \Omega$$

$$V_{c1} = -41.1 \times 10^{-3} \times 8.5 \times 10^{-3} \times 269.76$$

$$= -94.2 \text{ mV}$$

$$R_C \parallel R_5 \parallel R_6 \parallel r_{\pi 2} = 270.51$$

$$\therefore i_{c1} = V_{c1} / (R_C \parallel R_5 \parallel R_6 \parallel r_{\pi 2})$$

$$= 348.2 \mu\text{A}$$

Now,  $v_{be2} = v_{c1} = -94.2 \text{ mV}$

$$\therefore v_{c2} = g_{m2} v_{be2} (r_{o2} \parallel R_4 \parallel R_L)$$

$$r_{o2} \parallel R_4 \parallel R_L = 487.7 \Omega$$

$$= 201.88 \times 10^{-3} \times 94.2 \times 10^{-3} \times 487.7$$

$$= 9.275 \text{ V} \rightarrow \text{see that it's a positive value.}$$

$$i_{c2} = v_{c2} / (R_4 \parallel R_L)$$

$$= 9.275 / 500$$


$$= 18.6 \text{ mA}$$

→ look at the considered direction of  $i_{c2}$  in the circuit.

→ If opposite direction is considered,  $i_{c2}$  will be negative.

# Problem 4
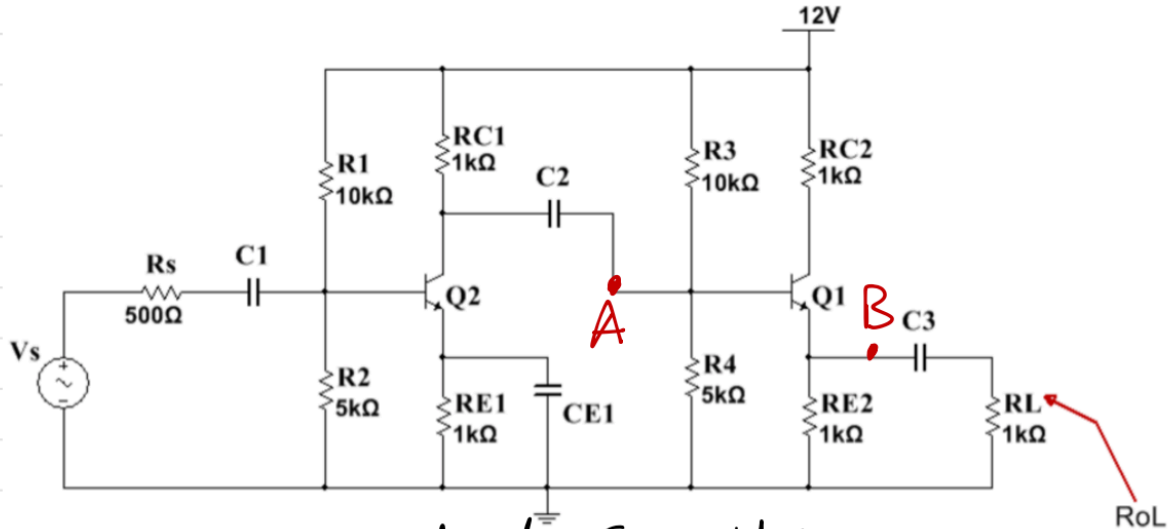
# Biasing and small signal parameters are as same as Problem 5 for both first and second stages



Small Signal Equivalent Circuit:

